


BUCK CONVERTER

PART 2

DESIGN

Calculations

Simulations

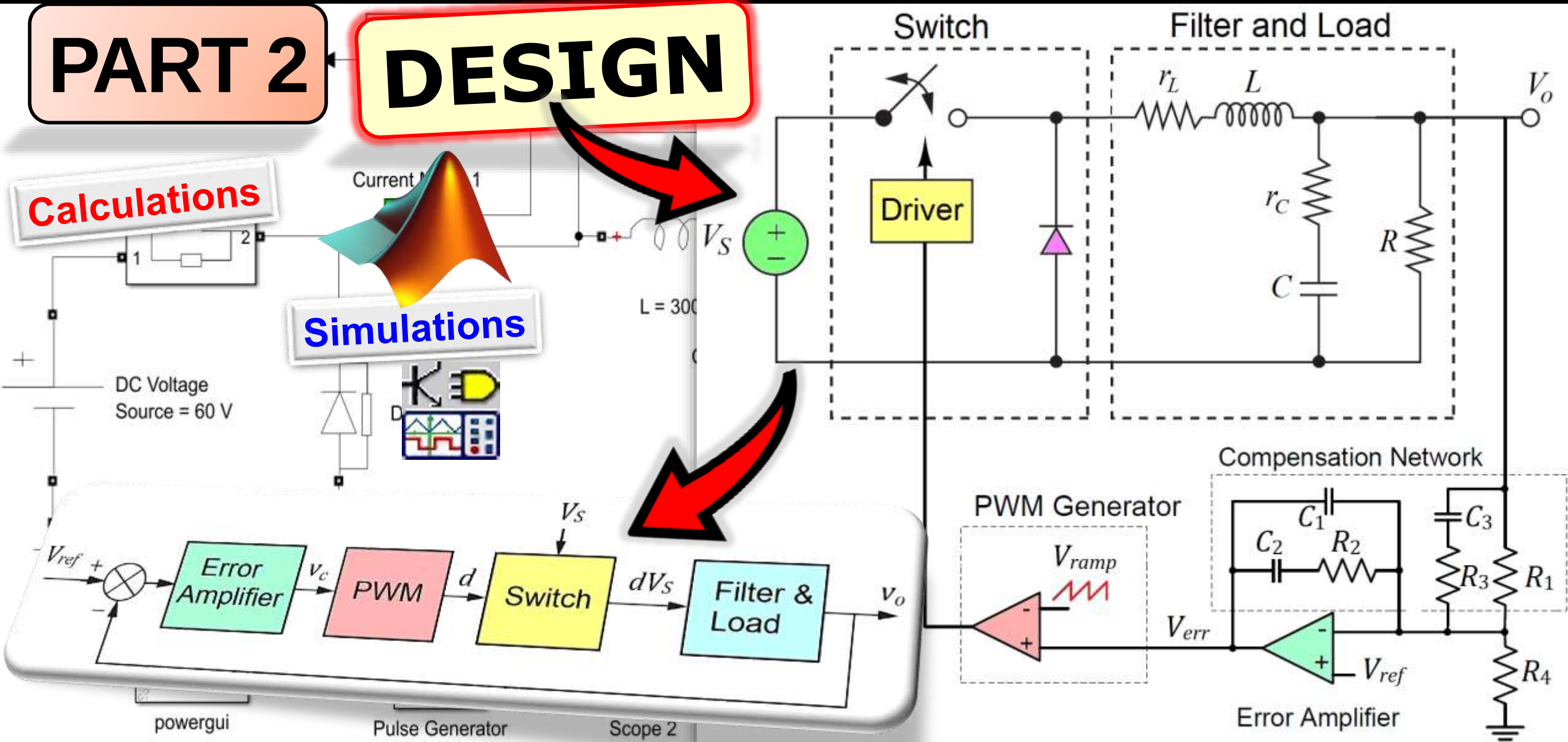

Outline

❖ **PART 1A: Open-Loop – Calculations**

1. Buck Converter Circuit
2. Specifications
3. Component Values
4. Component Ratings

❖ **PART 1B: Open-Loop – Simulations**

1. Simulations
 - a. TINA-TI Spice
 - b. MATLAB/Simulink
2. Fine Tuning

❖ **PART 2A: Control Theory**

1. Time Response Analysis
2. Frequency Response Analysis
3. Root Locus Analysis
4. Controller Circuits

❖ **PART 2B: Controller Design – Calculations**

1. Specifications
2. Buck Controller IC (LM5146)
3. Compensator Values - *Pole Placement Method*
4. Total Loop Transfer Function

❖ **PART 2C: Controller Design – Simulations**

1. Simulations
 - a. TINA-TI Spice
 - b. MATLAB/Simulink
2. Fine Tuning

PART 2A:

Theory

1. Time Response Analysis

❖ Unit-Step Response (Second-Order System)

$$y(t) = 1 - e^{-\omega_n \zeta t} \left(\cos(\omega_n \sqrt{1 - \zeta^2} t) + \frac{\zeta}{\sqrt{1 - \zeta^2}} \sin(\omega_n \sqrt{1 - \zeta^2} t) \right)$$

$$y(t) = 1 - \frac{\zeta}{\sqrt{1 - \zeta^2}} e^{-\omega_n \zeta t} \cos(\omega_n \sqrt{1 - \zeta^2} t - \phi)$$

$$y(t) = 1 - \frac{\zeta}{\sqrt{1 - \zeta^2}} e^{-\omega_n \zeta t} \cos(\omega_d t - \phi)$$

with $\phi = \arctan\left(\frac{\zeta}{\sqrt{1 - \zeta^2}}\right)$ and $\omega_d = \omega_n \sqrt{1 - \zeta^2}$

▪ General Second-Order System Model

$$H(s) = \frac{K_{DC} \omega_n^2}{s^2 + 2\zeta \omega_n s + \omega_n^2}$$


▪ Natural Frequency: ω_n

Frequency of **oscillation** of the system **without damping**

▪ Damping Ratio: ζ $\zeta = \frac{\text{Exponential decay frequency}}{\text{Natural frequency}}$

▪ DC Gain: K_{DC}

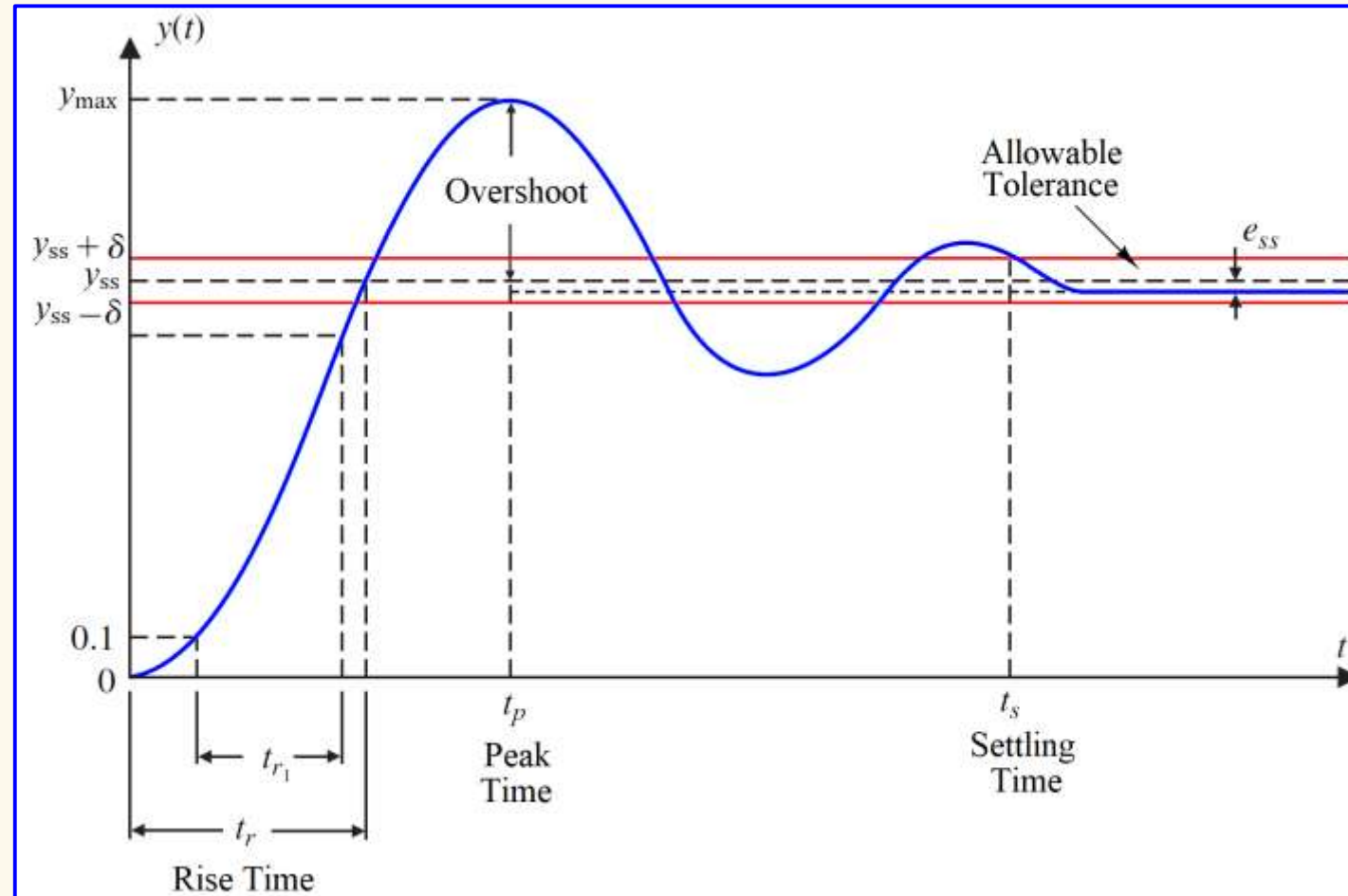Steady-state value (DC gain) of the system



NOTE: this model only holds for an **all-pole second-order system**, thus **without additional poles, zeros, delays or limitations**. If the system is **not a pure all-pole second-order system**, the response can **deviate** from the **calculated response**. However, we can use this second-order model to **estimate** the performance of other and **higher order systems**.

1. Time Response Analysis

- **Peak Time:** time required to reach the first peak value. Peak time is denoted as t_p . The peak time is found by differentiating $y(t)$ and setting $dy(t)/dt$ equal to zero.

$$t_p = \frac{\pi}{\omega_n \sqrt{1 - \zeta^2}} = \frac{\pi}{\omega_d}$$

- **Overshoot:** The amount that the waveform overshoots the steady-state value (final value) at the peak time. Overshoot is denoted as M_p .

$$M_p = \frac{y_{\max} - y_{ss}}{y_{ss}} \quad y_{\max} = y(t_p) = 1 + e^{-\pi\zeta/\sqrt{1-\zeta^2}}$$

For unit step input, $y_{ss} = 1$

Then, we get $M_p = \frac{1 + e^{-\pi\zeta/\sqrt{1-\zeta^2}} - 1}{1} = e^{-\pi\zeta/\sqrt{1-\zeta^2}}$ or $\zeta = \sqrt{\frac{\ln^2(M_p)}{\ln^2(M_p) + \pi^2}}$


- **Rise Time:** The time for the waveform to go from 0% to 100% of its final value.

Exact expression: $t_r = \frac{\arctan(\sqrt{1-\zeta^2}/\zeta)}{\omega_n \sqrt{1-\zeta^2}}$

Approximated expression: $t_r = \frac{2.16\zeta + 0.6}{\omega_n}$

- **Settling Time:** Time for the response to reach and stay within a specific percentage of the steady-state value.

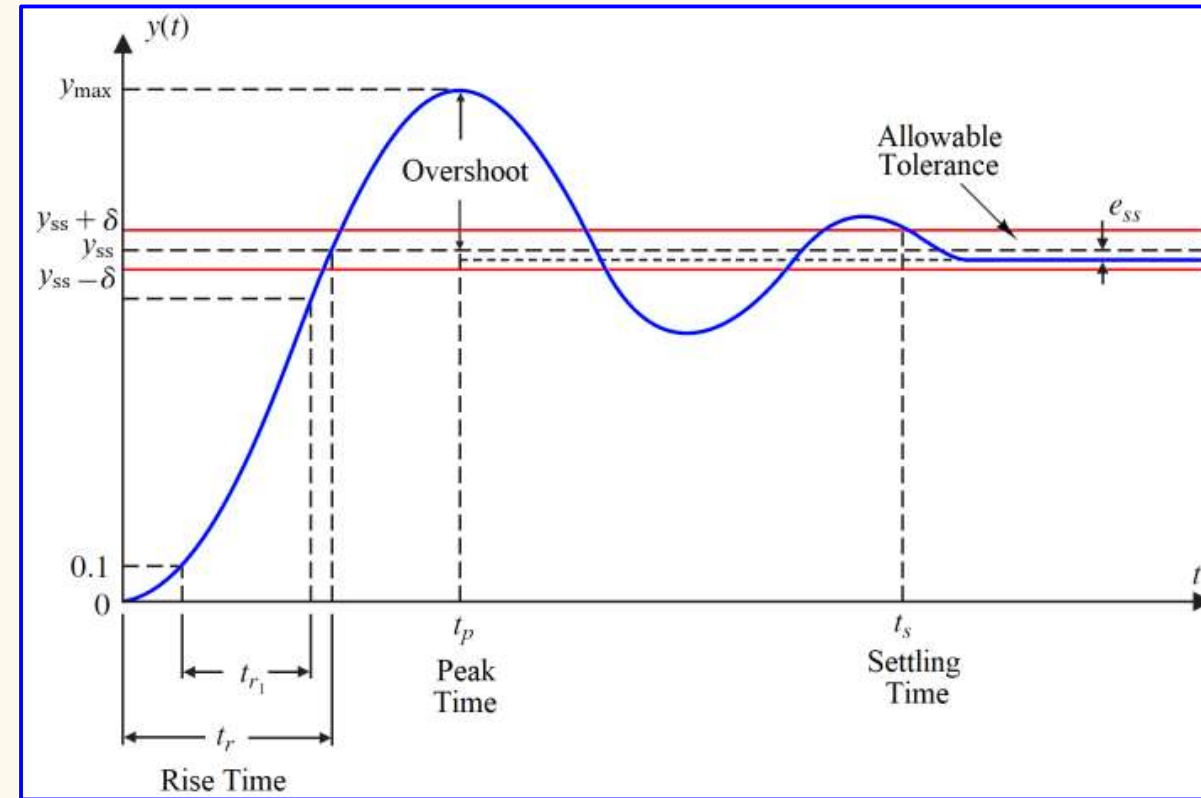- Settling time with **±2% criterion** is called **indication time** and is denoted as $t_s(2\%)$
- Settling time with **±5% criterion** is called **response time** and is denoted as $t_s(5\%)$



Indication time: $M_p = e^{-\pi\zeta t/\sqrt{1-\zeta^2}} = 0.02 \rightarrow t = -\frac{\ln(0.02\sqrt{1-\zeta^2})}{\zeta\omega_n} \equiv t_s(2\%)$

Approximately: $t_s(2\%) = \frac{4}{\zeta\omega_n}$

Response time: $M_p = e^{-\pi\zeta t/\sqrt{1-\zeta^2}} = 0.05 \rightarrow t = -\frac{\ln(0.05\sqrt{1-\zeta^2})}{\zeta\omega_n} \equiv t_s(5\%)$

Approximately: $t_s(5\%) = \frac{3}{\zeta\omega_n}$

2. Frequency Response Analysis

❖ Stability Margins

▪ Gain Margin:

1. Find the **frequency** where the **loop phase** is -180° . This frequency is called ω_{gm} .
2. Determine the **loop gain** at ω_{gm} .
3. The **gain margin (GM)** is the gain required to **raise** the **magnitude curve** to 0 dB.

▪ Phase Margin:

1. Find the **frequency** where the **loop gain** is 0 dB. This frequency is called ω_{pm} .
2. The **phase margin (PM)** is the **difference** between the **loop phase** at ω_{pm} and -180° .

Example:

Loop transfer function: $L(j\omega) = \frac{1000}{(j\omega + 4)(j\omega + 8)(j\omega + 10)}$

Phase Margin: $|L(j\omega)| = 1 \Rightarrow \frac{1000}{\sqrt{\omega^2 + 4^2}\sqrt{\omega^2 + 8^2}\sqrt{\omega^2 + 10^2}} = 1$

$$\arg(\omega_{pm}) = -\arctan\left(\frac{\omega_{pm}}{4}\right) - \arctan\left(\frac{\omega_{pm}}{8}\right) - \arctan\left(\frac{\omega_{pm}}{10}\right) = -134^\circ$$

$$PM = 180 + \arg(\omega_{pm}) = 46^\circ$$

Gain Margin: $\arg(\omega) = -\arctan\left(\frac{\omega}{4}\right) - \arctan\left(\frac{\omega}{8}\right) - \arctan\left(\frac{\omega}{10}\right) = -180^\circ$

$$|L(j\omega_{gm})| = \frac{1000}{\sqrt{\omega_{gm}^2 + 4^2}\sqrt{\omega_{gm}^2 + 8^2}\sqrt{\omega_{gm}^2 + 10^2}} = 0.3307 \text{ } (-9.61 \text{ dB})$$

Determine:

- Phase margin (PM)
- Gain margin (GM)


Solving:

$$\omega = 6.79 \text{ rad/s} \equiv \omega_{pm}$$

Solving:

$$\omega = 12.33 \text{ rad/s} \equiv \omega_{gm}$$

$$GM = \frac{1}{|L(j\omega_{gm})|} = 3.024 \text{ } (9.61 \text{ dB})$$

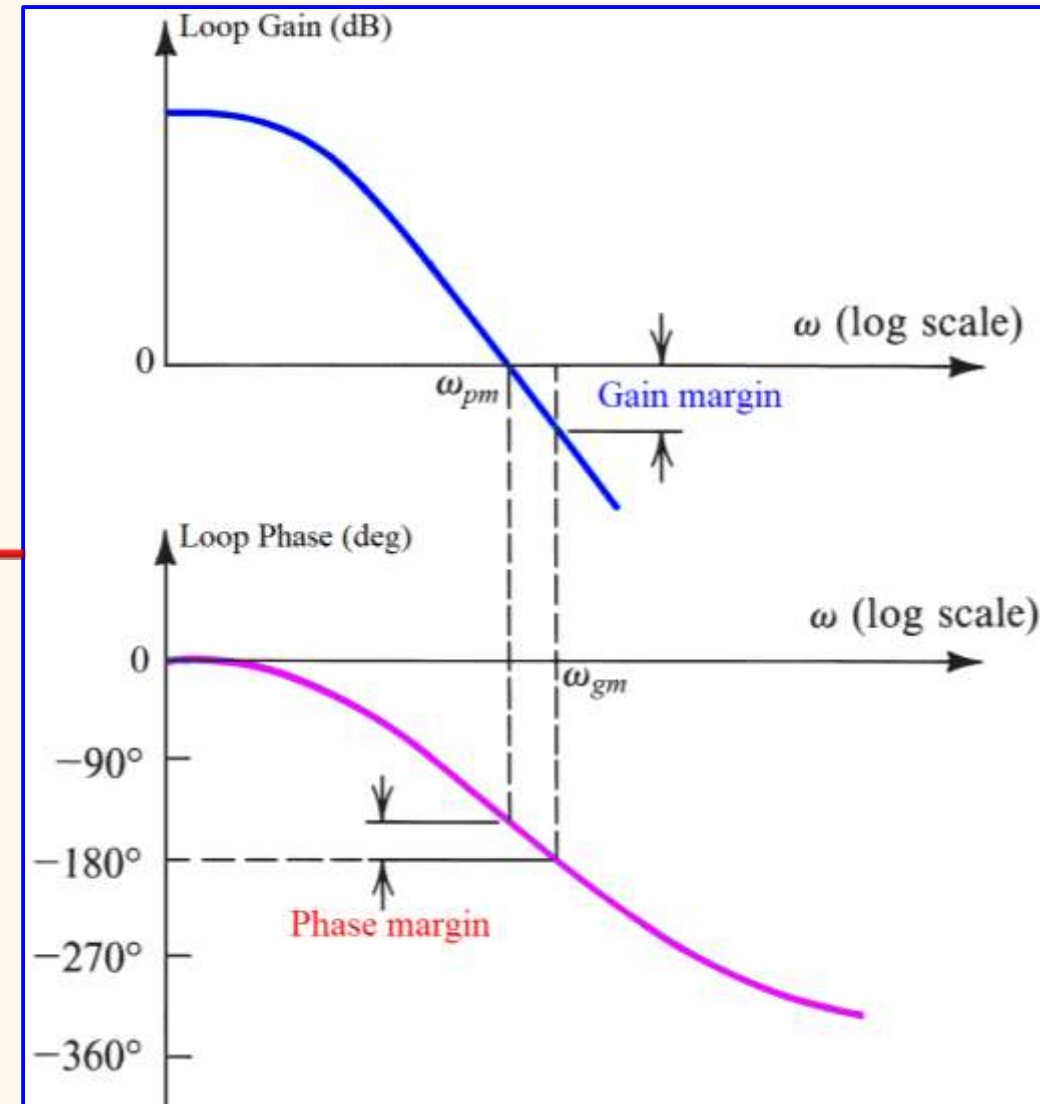

2. Frequency Response Analysis



Example:

Loop transfer function: $L(j\omega) = \frac{1000}{(j\omega + 4)(j\omega + 8)(j\omega + 10)}$

Determine:


- Phase margin (PM)
- Gain margin (GM)

Simulation Results:

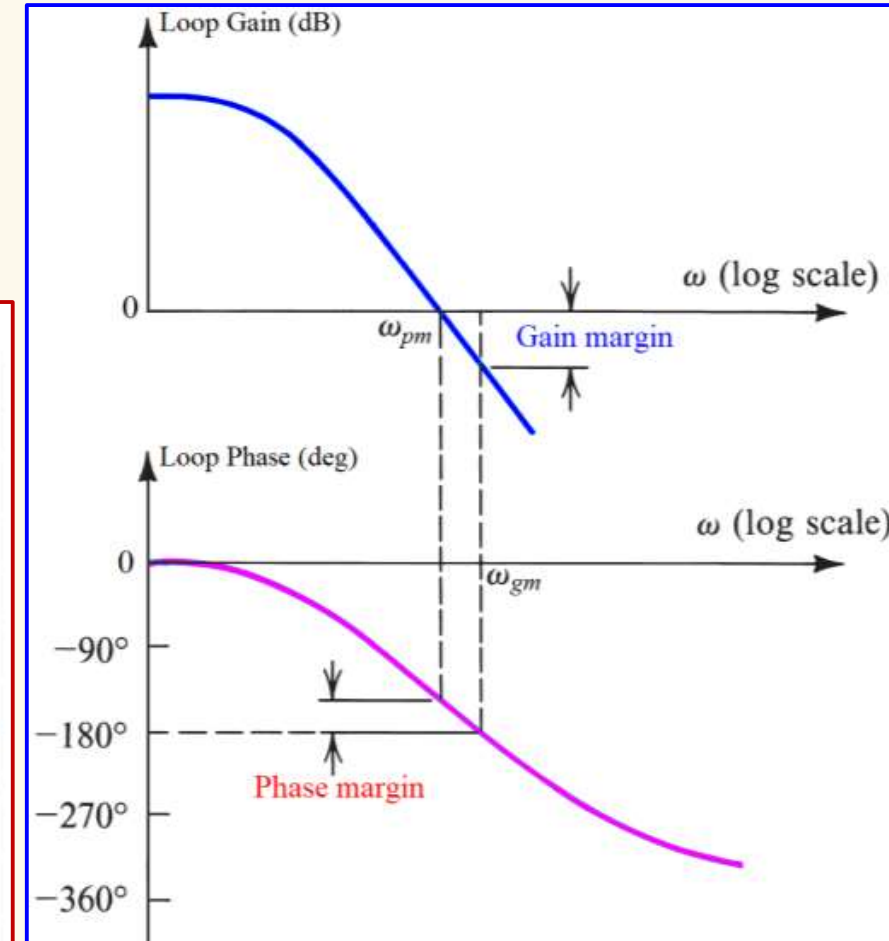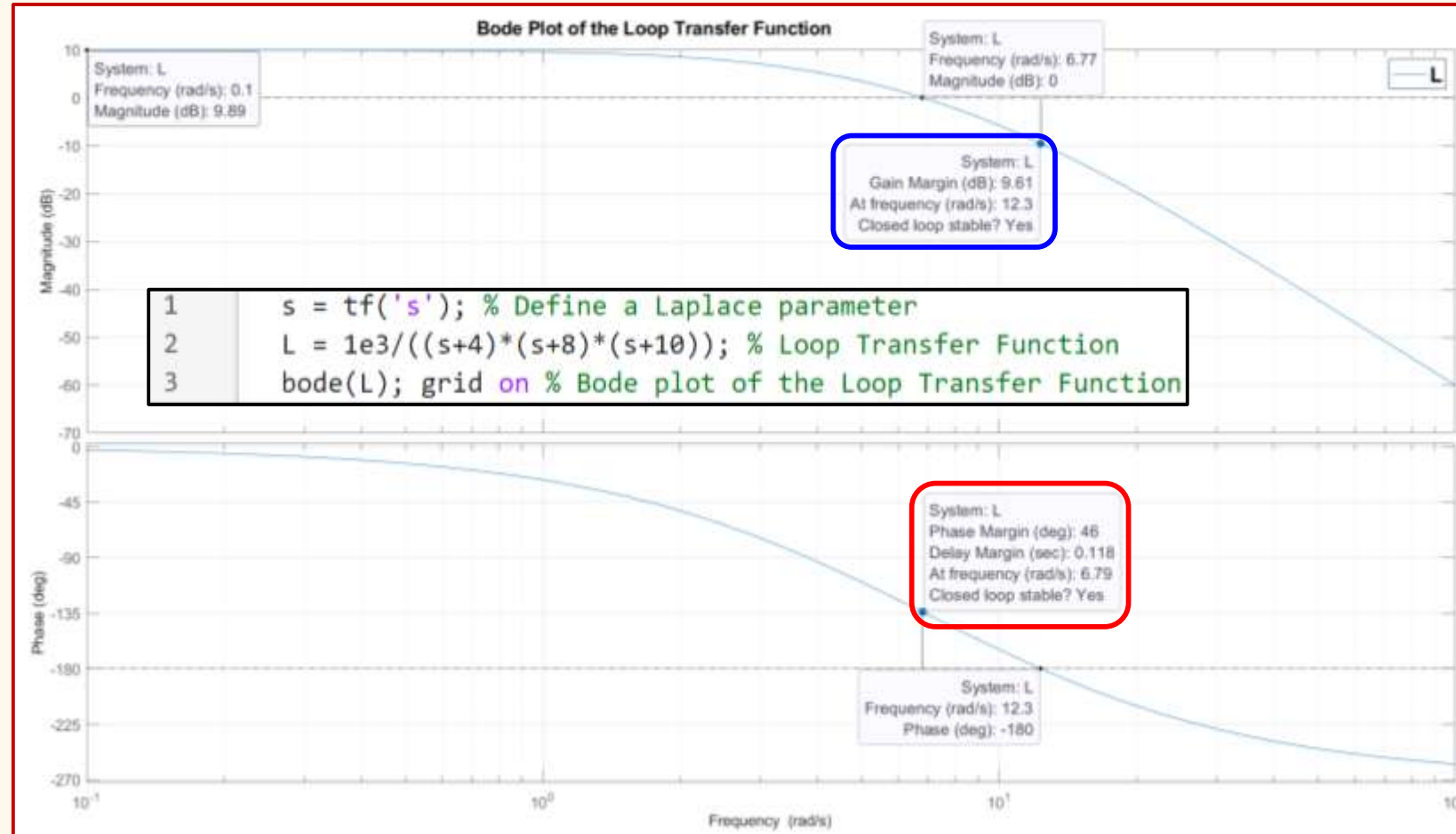

$$\omega_{pm} = 6.79 \text{ rad/s} \quad PM = 180 + \arg(\omega_{pm}) = 46^\circ$$

$$\omega_{gm} = 12.33 \text{ rad/s} \quad GM = \frac{1}{|L(j\omega_{gm})|} = 3.024 \text{ (9.61 dB)}$$

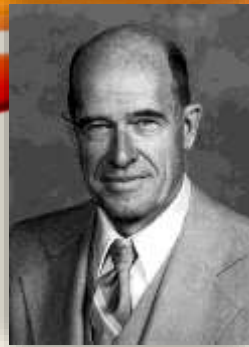


3. Root Locus Analysis

❖ Root Locus Method

- Analysis and design for **stability** and **transient response** (W.R. Evans, 1948).
- Graphical presentation** of the **closed-loop poles** as a function of a **system parameter**.
- Display the effects on **overshoot**, **settling time**, **rise time** and **peak time**.

Example:

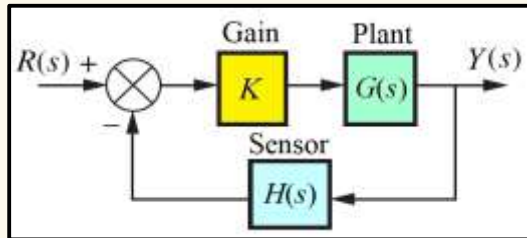

$$G(s) = \frac{2}{s-1} \quad H(s) = \frac{1}{s+3}$$

Determine the range of stability.

Root Locus Equation: $1 + L(s) = 0$

$$1 + KG(s)H(s) = 0 \Rightarrow 1 + \frac{2K}{(s-1)(s+3)} = 0$$

$$(s-1)(s+3) + 2K = 0$$


$$s^2 + 2s - 3 + 2K = 0$$

When $-3 + 2K = 0$, we have: $s^2 + 2s = 0$

$$s(s+2) = 0$$


$$-3 + 2K \geq 0 \Rightarrow K \geq 1.5$$

Stability
Range

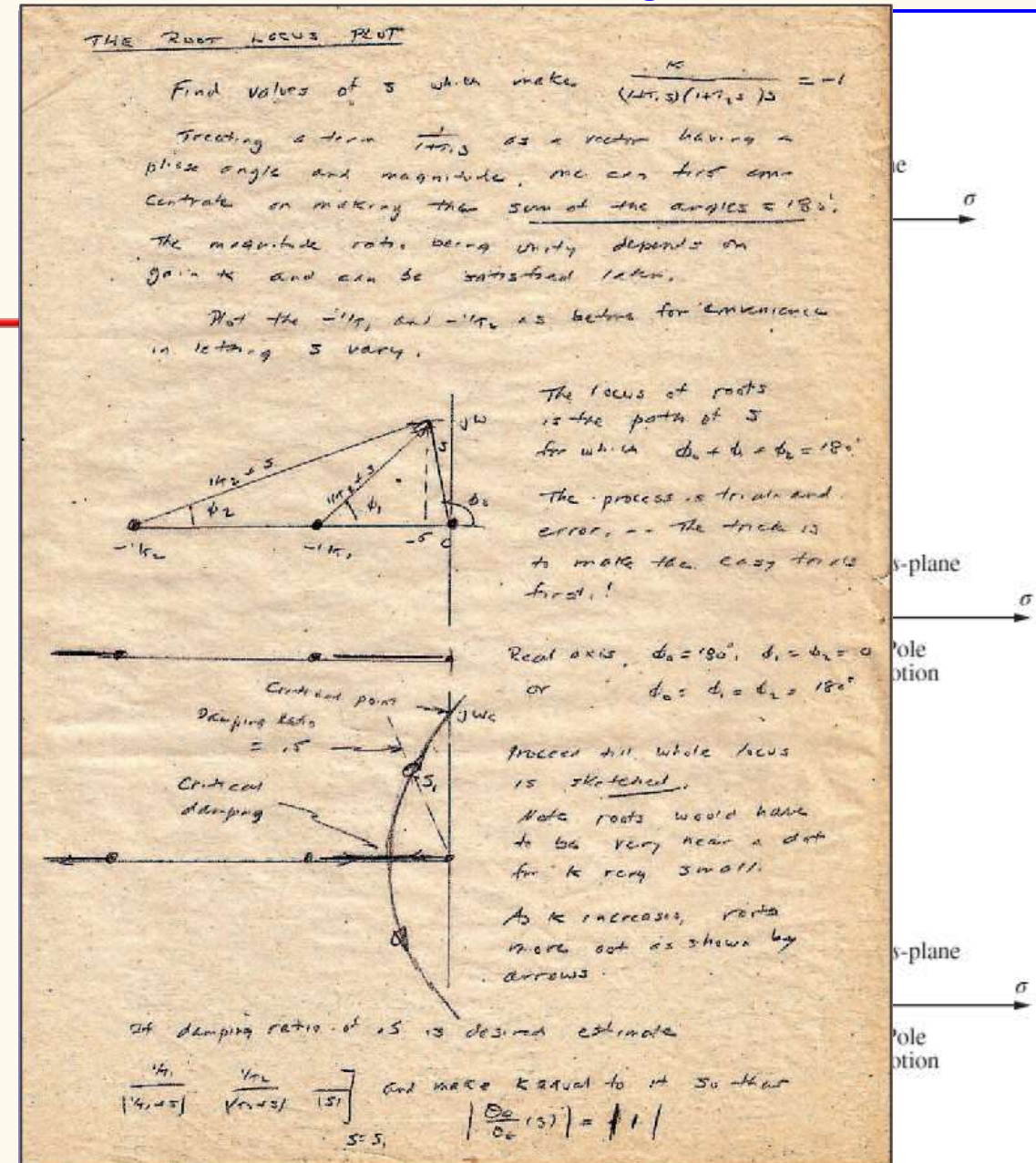

3. Root Locus Analysis

Example:

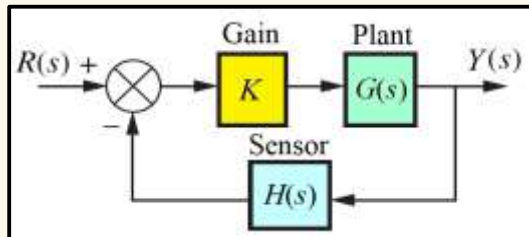


$$G(s) = \frac{2}{s-1} \quad H(s) = \frac{1}{s+3}$$

Determine the range of stability.


$$s^2 + 2s - 3 + 2K = 0 \quad K \geq 1.5$$

Stability Range


Simulation Results:

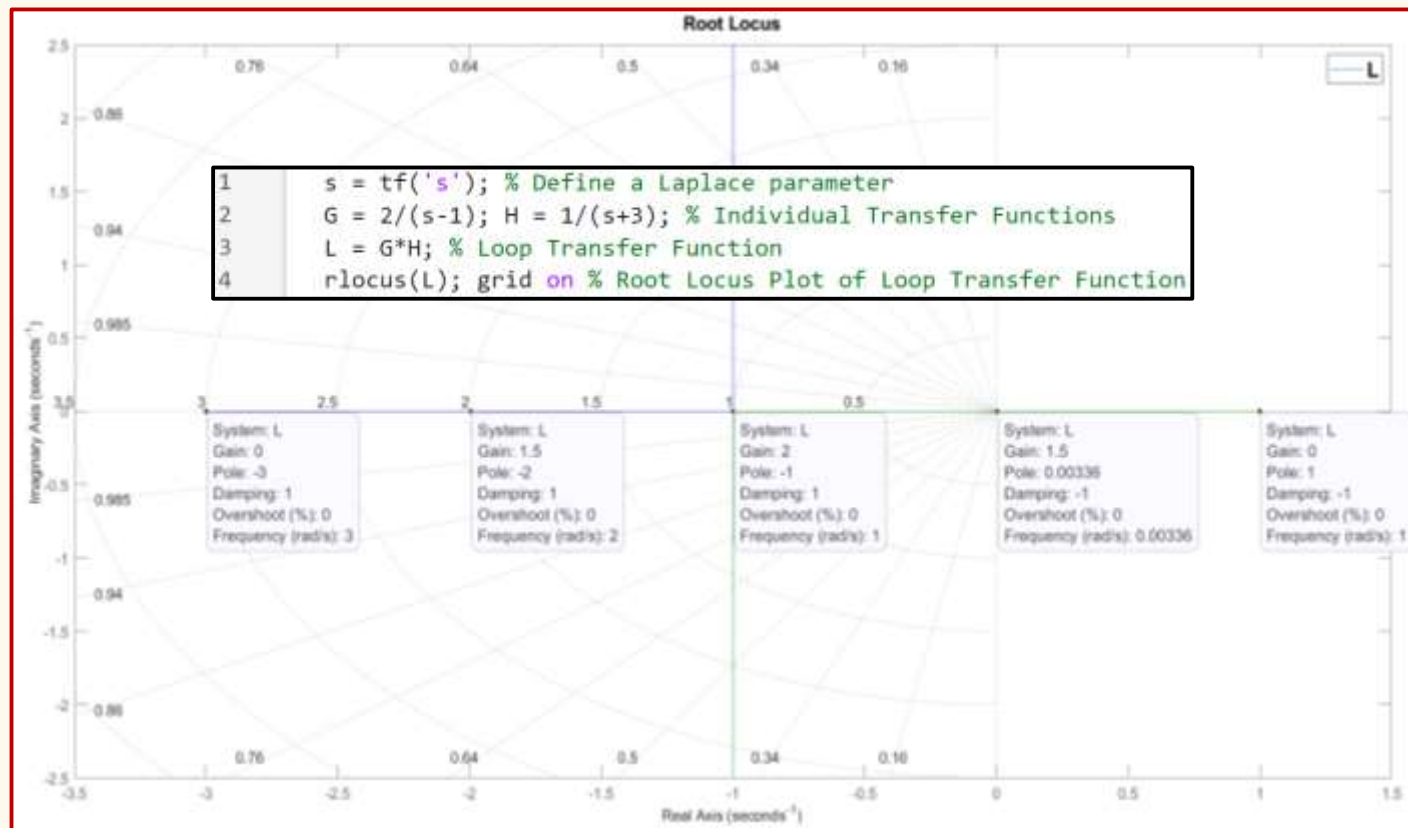


Settling Time

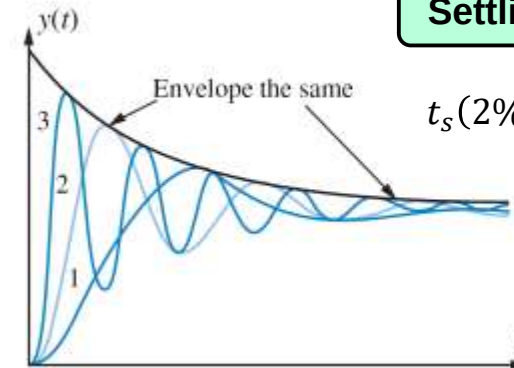


$$t_s(2\%) = \frac{4}{\zeta \omega_n}$$

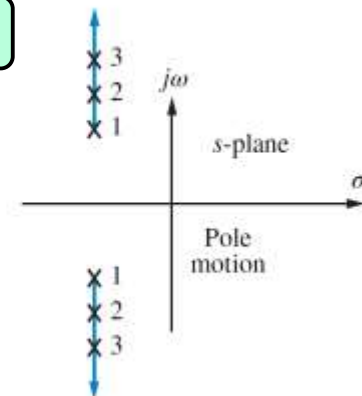


Peak Time

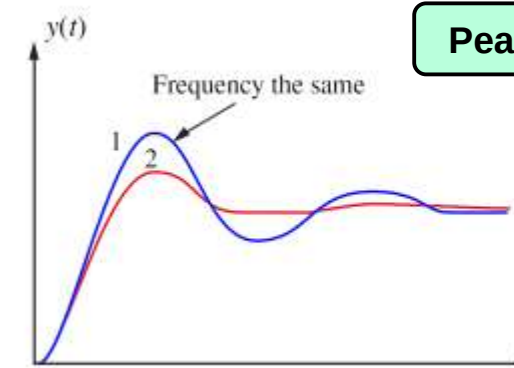


$$t_p = \frac{\pi}{\omega_d}$$

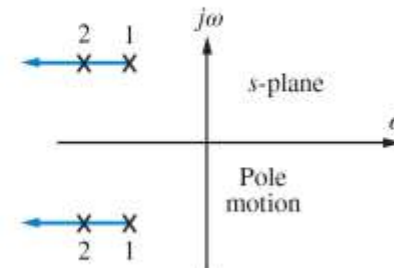

Overshoot


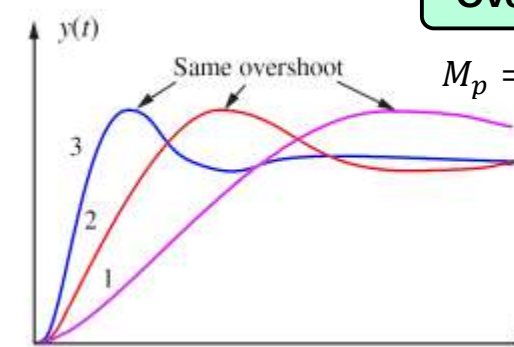

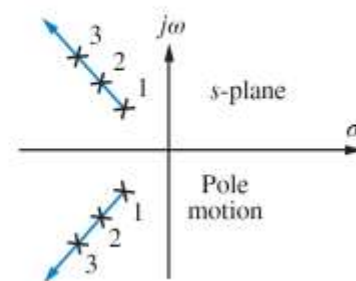
$$M_p = e^{-\pi \zeta / \sqrt{1-\zeta^2}}$$





4. Controller Circuits

❖ Type 2 Compensated Error Amplifier

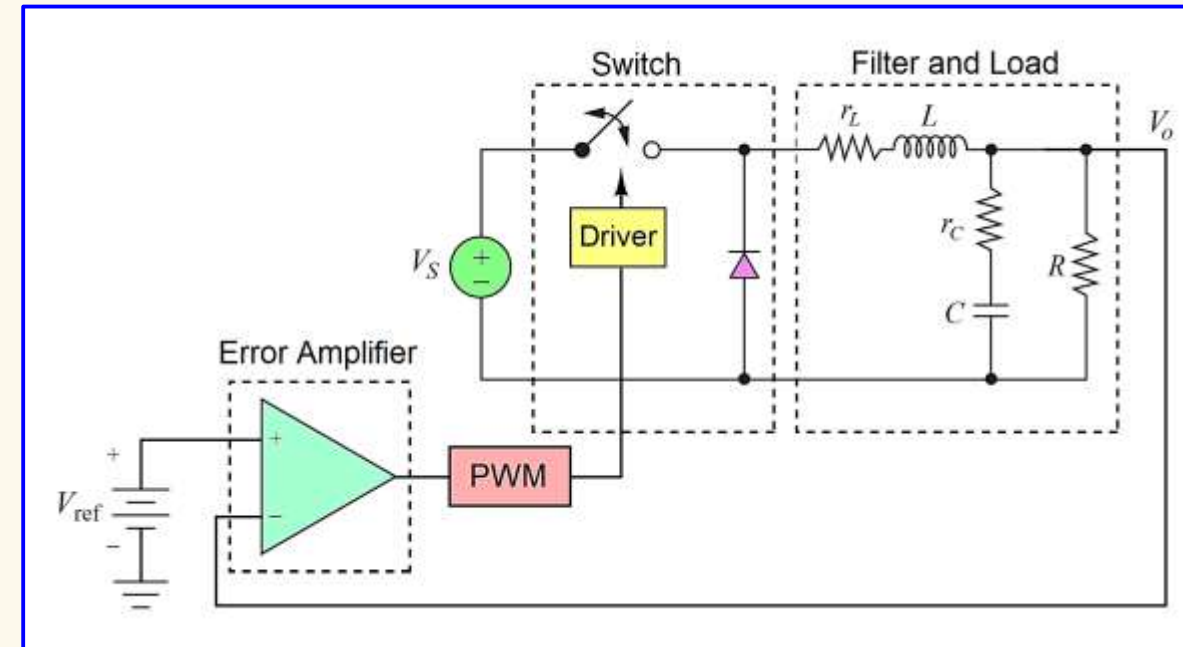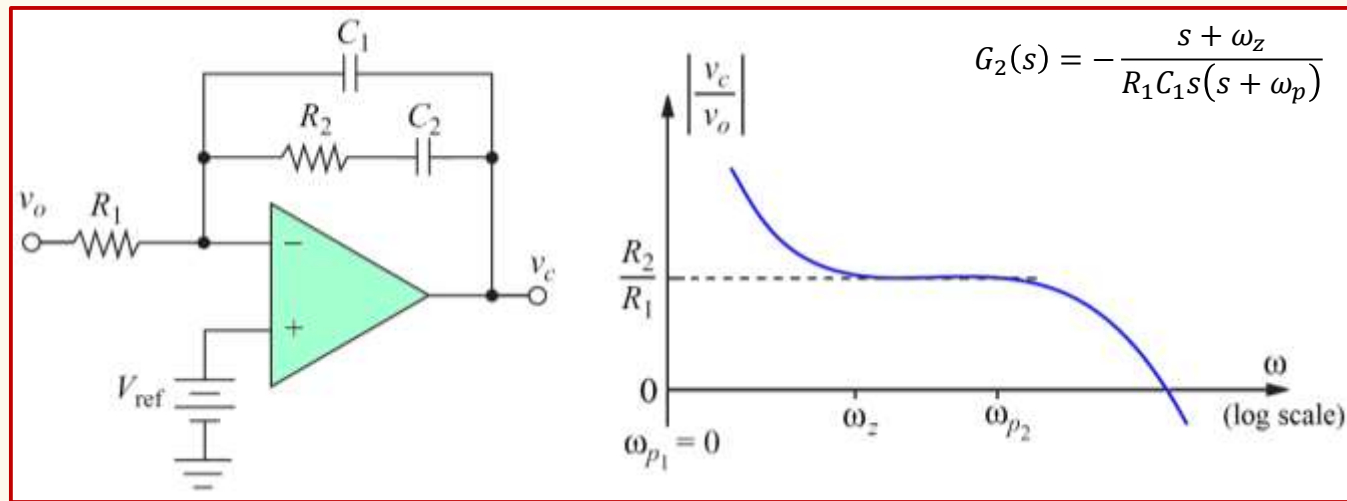


❖ Type 3 Compensated Error Amplifier

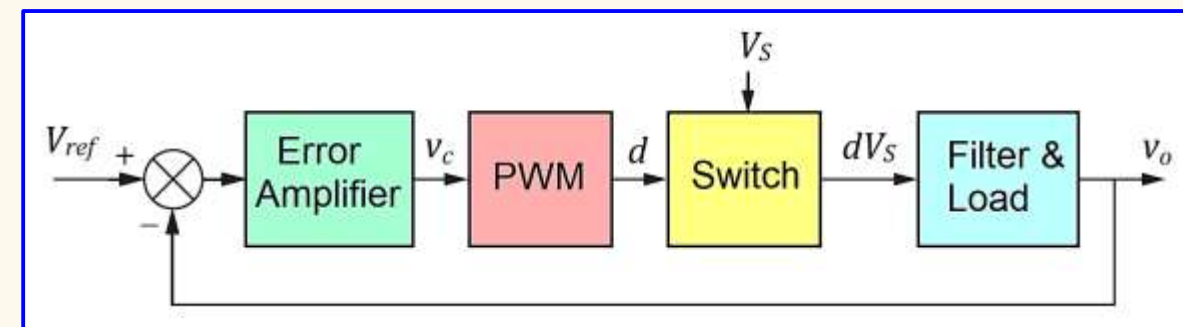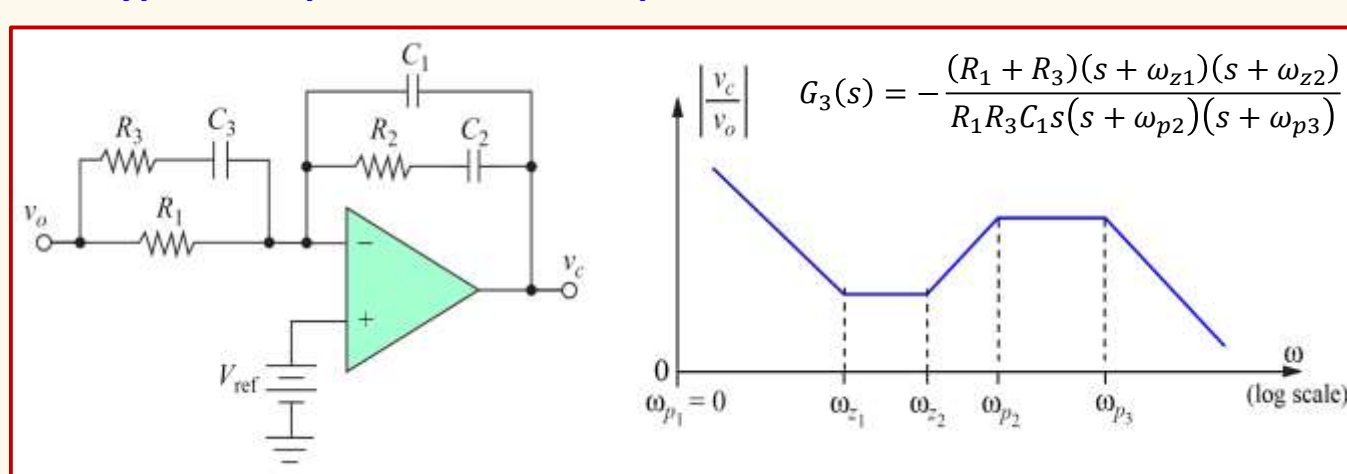

4. Controller Circuits

❖ Modulator:

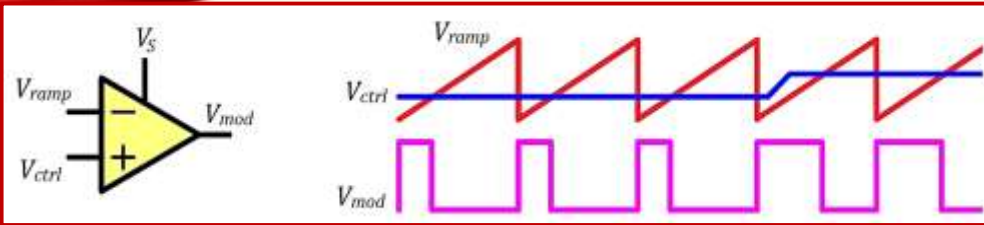

Modulator Average Output Voltage: $V_{mod} = \frac{1}{T} \int_0^T v_{mod}(t) dt = \frac{1}{T} \int_0^{t_{on}} V_s dt$

Modulator Transfer Function: $M(s) = \frac{\Delta V_{mod}}{\Delta V_{ctrl}}$

$$M(s) = \frac{dV_{mod}}{dV_{ctrl}} = \frac{d}{dV_{ctrl}} \left(V_s \frac{V_{ctrl}}{V_{ramp}} \right) \quad \boxed{M(s) = \frac{V_s}{V_{ramp}}}$$

❖ Filter & Load:



Filter & Load Transfer Function: $F(s) = \frac{V_o}{V_D} = \frac{1 + r_c C s}{1 + \frac{r_L}{R} + \left(\frac{L}{R} + (r_L + r_c) C + \frac{r_L r_c C}{R} \right) s + \left(1 + \frac{r_c}{R} \right) L C s^2}$

❖ Compensator:

Compensator Transfer Function: $G(s) = \frac{V_c}{V_o} = \frac{A_{OL}(s)}{1 + A_{OL}(s)\beta(s)} \approx \frac{A_{OL}(s)}{A_{OL}(s)\beta(s)} \approx \frac{1}{\beta(s)}$

Error Amplifier Open-Loop Transfer Function: $A_{OL}(s) = \frac{A_{DC}}{1 + \frac{s}{\omega_{pe}}} \quad A_{OL}(s)\beta(s) \gg 1$

Feedback Transfer Function: $\beta(s)$

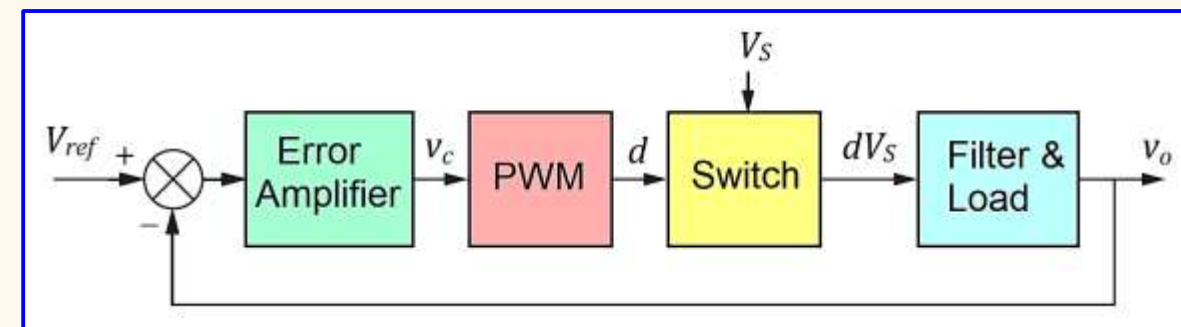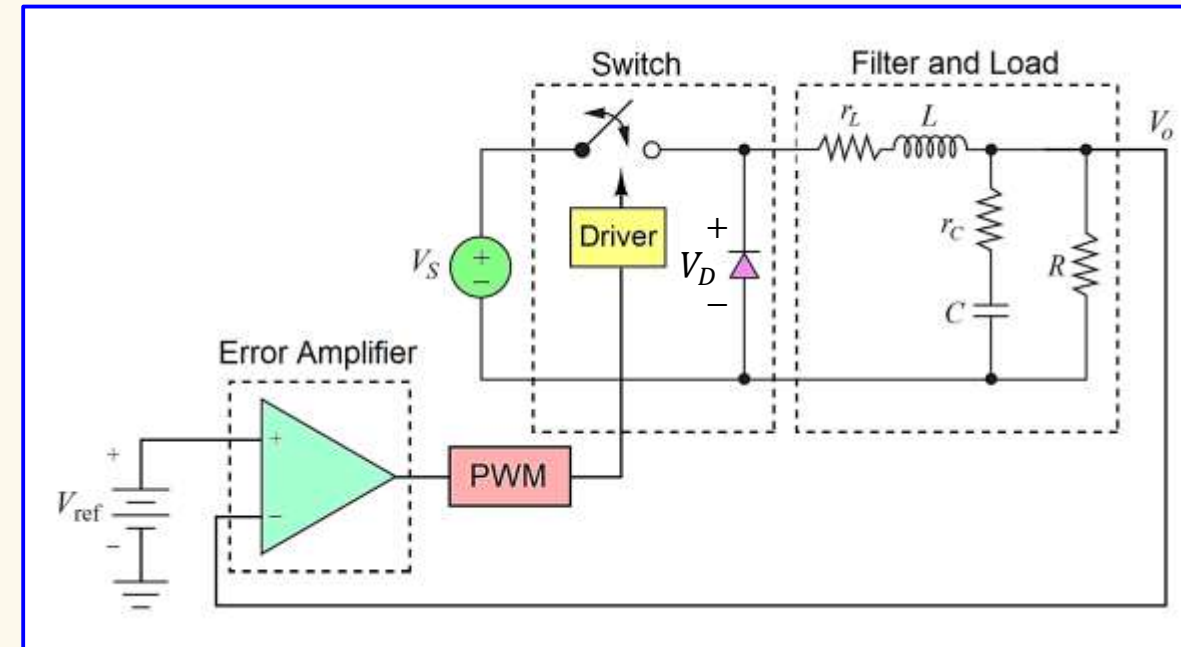

PART 2B:

CALCULATIONS

❖ Specifications:

Objective: Design a buck converter circuit with:

- DC input voltage $V_S = 60\text{ V}$
- Average output voltage $V_o = 15\text{ V}$
- Average output current $I_o = 2\text{ A}$
- Maximum percentage peak-peak output ripple voltage $\Delta V_o/V_o = 0.01\text{ (1\%)}$

❖ Buck Converter Component Values & Selections:



PART 1

$L = 300\text{ }\mu\text{H}$ $r_L = 0.025\text{ }\Omega$ $R = 7.5\text{ }\Omega$
 $C = 20\text{ }\mu\text{F}$ $r_C = 0.400\text{ }\Omega$ $f_s = 100\text{ kHz (selected)}$

❖ Buck Controller IC (LM5146):

- Input Voltage Range: 5.5 V to 100 V
- Maximum Output Current: 20 A
- Control Mode: Voltage Mode
- Operating Temperature Range: $-40\text{ }^\circ\text{C}$ to $125\text{ }^\circ\text{C}$
- Reference Voltage: $V_{ref} = 0.8\text{ V}$
- PWM Ramp Amplitude: $V_{ramp} = \frac{V_S}{15} = \frac{60}{15} = 4\text{ V}$
- Error Amplifier Open-Loop DC Voltage Gain: $A_{OL} = 94\text{ dB (50118 V/V)}$
- Gain Bandwidth Product: $GBW = 6.5\text{ MHz}$
- Error Amplifier Open-Loop Compensation Pole: $f_{pe} = 129.7\text{ Hz}$

PARAMETER		TEST CONDITIONS	MIN	TYP	MAX	UNIT
PWM CONTROL						
DC _{100kHz}	Maximum duty cycle	$F_{SW} = 100\text{ kHz}, 6\text{ V} \leq V_{VIN} \leq 60\text{ V}$	98	99		%
DC _{400kHz}		$F_{SW} = 400\text{ kHz}, 6\text{ V} \leq V_{VIN} \leq 60\text{ V}$	90	94		%
V _{RAMP(min)}	RAMP valley voltage (COMP at 0% duty cycle)			300		mV
k _{FF}	PWM feedforward gain (V_{IN} / V_{RAMP})	$6\text{ V} \leq V_{VIN} \leq 100\text{ V}$		15		V/V
ERROR AMPLIFIER						
V _{REF}	FB reference Voltage	FB connected to COMP	792	800	808	mV
AVOL	DC gain			94		dB
GBW	Unity gain bandwidth			6.5		MHz

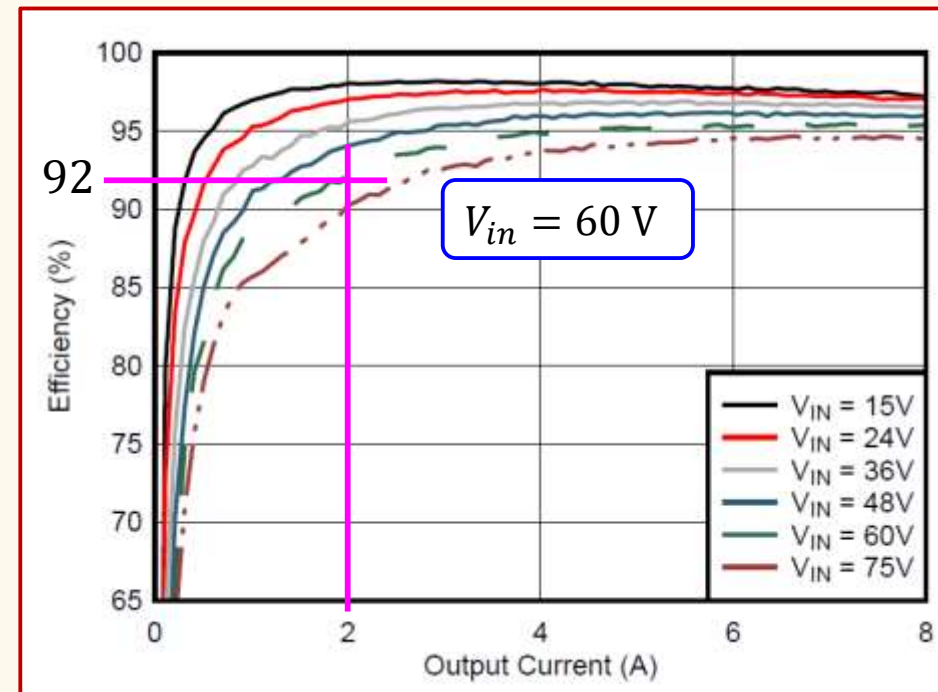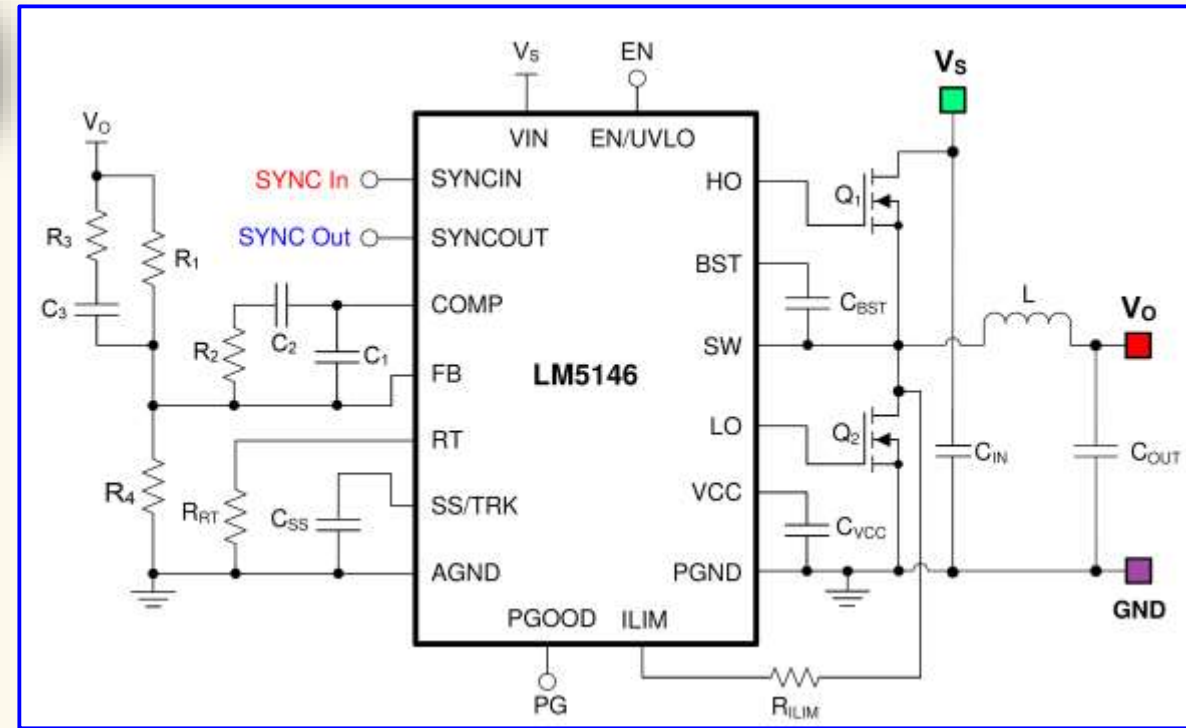

❖ Specifications:

Objective: Design a buck converter circuit with:

- DC input voltage $V_S = 60\text{ V}$
- Average output voltage $V_o = 15\text{ V}$
- Average output current $I_o = 2\text{ A}$
- Maximum percentage peak-peak output ripple voltage $\Delta V_o/V_o = 0.01\text{ (1\%)}$

❖ Buck Converter Component Values & Selections:

PART 1

$$L = 300\text{ }\mu\text{H} \quad r_L = 0.025\text{ }\Omega \quad R = 7.5\text{ }\Omega$$

$$C = 20\text{ }\mu\text{F} \quad r_C = 0.400\text{ }\Omega \quad f_s = 100\text{ kHz (selected)}$$

❖ Buck Controller IC (LM5146):

- Reference Voltage: $V_{ref} = 0.8\text{ V}$
- PWM Ramp Amplitude: $V_{ramp} = \frac{V_S}{15} = \frac{60}{15} = 4\text{ V}$
- Error Amplifier Open-Loop DC Voltage Gain: $A_{OL} = 94\text{ dB (50118 V/V)}$
- Gain Bandwidth Product: $GBW = 6.5\text{ MHz}$
- Error Amplifier Open-Loop Compensation Pole: $f_{pe} = 129.7\text{ Hz}$

❖ Compensator Values – Pole Placement Method:

- Step 1: Resistor Divider Values** Select $R_4 = 10\text{ k}\Omega$

$$V_{ref} = \frac{R_4}{R_1 + R_4} V_o \Rightarrow R_1 = \left(\frac{V_o}{V_{ref}} - 1 \right) R_4 = \left(\frac{15}{0.8} - 1 \right) \cdot 10^4$$

$$R_1 = 177.5\text{ k}\Omega$$

- Step 2: Resonant Frequency of the Filter**

$$f_{LC} = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi\sqrt{300 \cdot 10^{-6} \cdot 20 \cdot 10^{-6}}} = 2055\text{ Hz}$$


- Step 3: First Zero Frequency**

Slightly smaller than f_{LC}

$$f_{z1} = 0.9f_{LC} = 0.9 \cdot 2055 = 1850\text{ Hz}$$

$$f_{z1} = \frac{1}{2\pi R_1 C_3} \Rightarrow C_3 = \frac{1}{2\pi R_1 f_{z1}} = \frac{1}{2\pi \cdot 177.5 \cdot 10^3 \cdot 1850}$$

$$C_3 = 484.7\text{ pF}$$

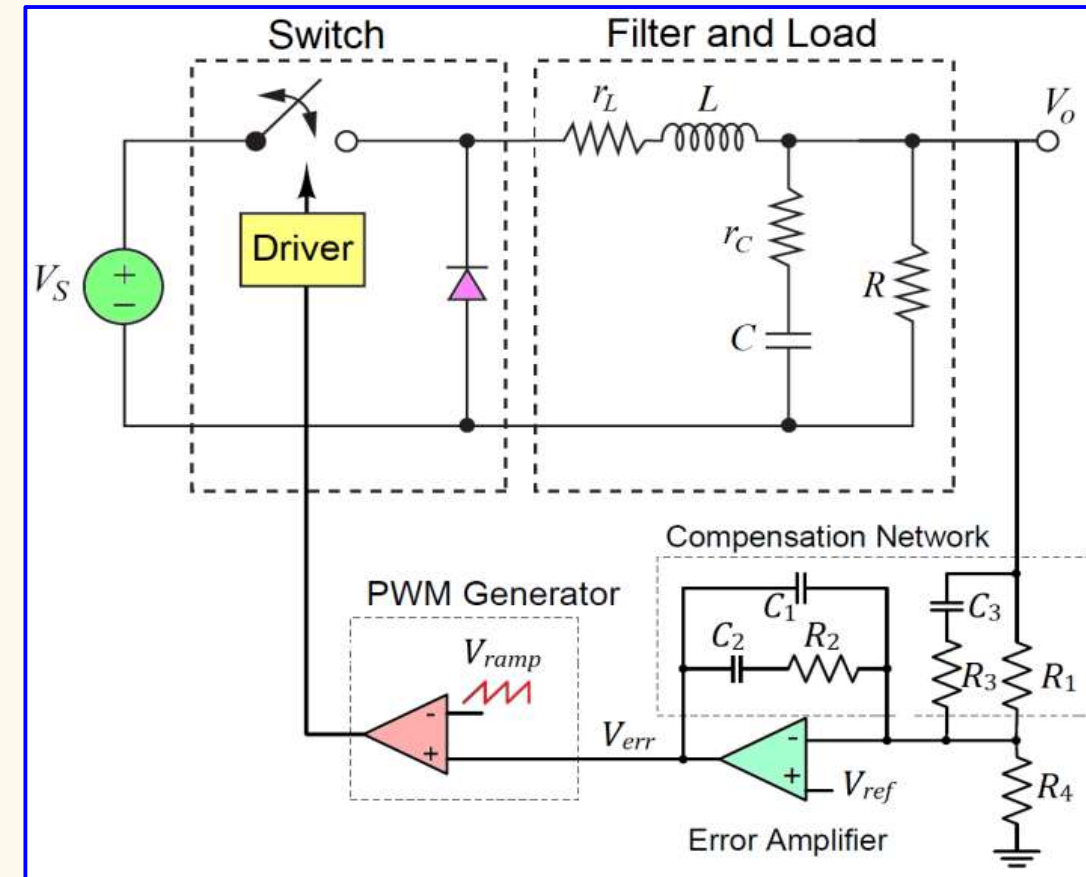

Type 3 Compensated Error Amplifier:

$$G_3(s) = -\frac{(R_1 + R_3)(s + \omega_{z1})(s + \omega_{z2})}{R_1 R_3 C_1 s (s + \omega_{p2})(s + \omega_{p3})}$$

$$G_3(s) = -\frac{R_1 + R_3}{R_1 R_3 C_1} \cdot \frac{\left(s + \frac{1}{(R_1 + R_3)C_3}\right) \left(s + \frac{1}{R_2 C_2}\right)}{s \left(s + \frac{1}{R_3 C_3}\right) \left(s + \frac{C_1 + C_2}{C_1 C_2 R_2}\right)}$$

Assuming:

$$R_1 \gg R_3$$

$$C_2 \gg C_1$$

$$G_3(s) \approx -\frac{1}{R_3 C_1} \cdot \frac{\left(s + \frac{1}{R_1 C_3}\right) \left(s + \frac{1}{R_2 C_2}\right)}{s \left(s + \frac{1}{R_3 C_3}\right) \left(s + \frac{1}{R_2 C_1}\right)}$$

❖ Compensator Values – Pole Placement Method:

- **Step 1: Resistor Divider Values** Select $R_4 = 10 \text{ k}\Omega$

$$V_{ref} = \frac{R_4}{R_1 + R_4} V_o \Rightarrow R_1 = \left(\frac{V_o}{V_{ref}} - 1 \right) R_4 = \left(\frac{15}{0.8} - 1 \right) \cdot 10^4 \quad \boxed{R_1 = 177.5 \text{ k}\Omega}$$

- **Step 2: Resonant Frequency of the Filter**

$$f_{LC} = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi\sqrt{300 \cdot 10^{-6} \cdot 20 \cdot 10^{-6}}} = 2055 \text{ Hz}$$

- **Step 3: First Zero Frequency**

$$f_{z1} = \frac{1}{2\pi R_1 C_3} \Rightarrow C_3 = \frac{1}{2\pi R_1 f_{z1}} = \frac{1}{2\pi \cdot 177.5 \cdot 10^3 \cdot 1850}$$

Slightly smaller than f_{LC}

$$f_{z1} = 0.9 f_{LC} = 0.9 \cdot 2055 = 1850 \text{ Hz}$$

$$\boxed{C_3 = 484.7 \text{ pF}}$$

- **Step 4: Second Pole Frequency**

Select the crossover frequency at $f_t = 10 \text{ kHz}$ (**one decade below** $f_s = 100 \text{ kHz}$)

Set $f_{p2} = f_t = 10 \text{ kHz}$

$$f_{p2} = \frac{1}{2\pi R_3 C_3} \Rightarrow R_3 = \frac{1}{2\pi C_3 f_{p2}} = \frac{1}{2\pi \cdot 484.7 \cdot 10^{-12} \cdot 10^4}$$

$$\boxed{R_3 = 32.84 \text{ k}\Omega}$$

- **Step 5: Required Compensator Gain at the Crossover Frequency**


$$\text{Modulator gain: } M = \frac{V_s}{V_{ramp}} = \frac{60}{4} = 15 \text{ (23.52 dB)}$$

$$\text{Filter gain: } F(s) = \frac{1 + r_c C s}{1 + \frac{r_L}{R} + \left(\frac{L}{R} + (r_L + r_c) C + \frac{r_L r_c C}{R} \right) s + \left(1 + \frac{r_c}{R} \right) L C s^2}$$

$$F(j\omega) = \frac{1 + j\omega r_c C}{1 + \frac{r_L}{R} - \left(1 + \frac{r_c}{R} \right) L C \omega^2 + j\omega \left(\frac{L}{R} + (r_L + r_c) C + \frac{r_L r_c C}{R} \right)}$$

$$|F(j\omega)| = \frac{\sqrt{1 + (\omega r_c C)^2}}{\sqrt{\left(1 + \frac{r_L}{R} - \left(1 + \frac{r_c}{R} \right) L C \omega^2 \right)^2 + \left(\omega \left(\frac{L}{R} + (r_L + r_c) C + \frac{r_L r_c C}{R} \right) \right)^2}}$$

$$|F(j\omega_t)| = 0.04636 \text{ (-26.68 dB)}$$

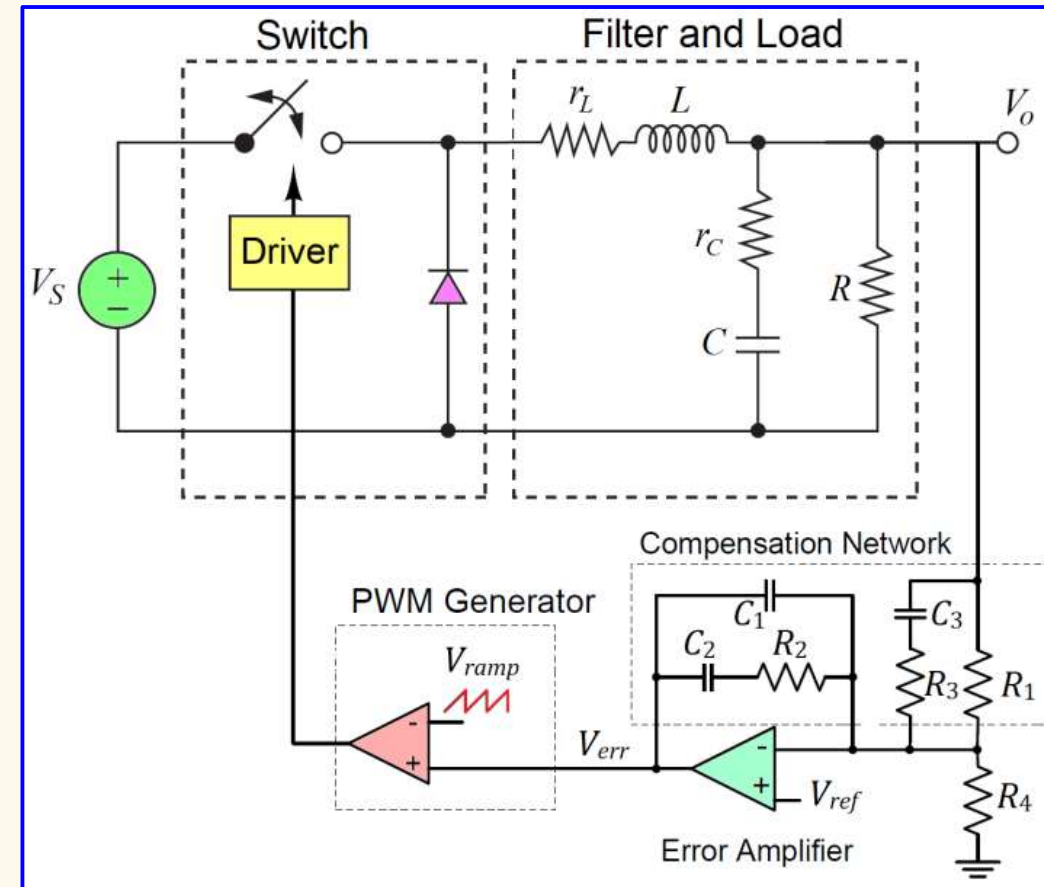

Type 3 Compensated Error Amplifier:

$$G_3(s) \approx -\frac{1}{R_3 C_1} \cdot \frac{\left(s + \frac{1}{R_1 C_3} \right) \left(s + \frac{1}{R_2 C_2} \right)}{s \left(s + \frac{1}{R_3 C_3} \right) \left(s + \frac{1}{R_2 C_1} \right)}$$

Loop gain at f_t must be unity:

$$K_{comp} \cdot M \cdot |F(j\omega_t)| = 1$$

$$K_{comp} = \frac{1}{M \cdot |F(j\omega_t)|}$$

$$K_{comp} = \frac{1}{15 \cdot 0.04636}$$

$$K_{comp} = 1.438 \text{ (3.155 dB)}$$

❖ Compensator Values – Pole Placement Method:

- Step 1: Resistor Divider Values** Select $R_4 = 10 \text{ k}\Omega$ $R_1 = 177.5 \text{ k}\Omega$
- Step 2: Resonant Frequency of the Filter**

$$f_{LC} = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi\sqrt{300 \cdot 10^{-6} \cdot 20 \cdot 10^{-6}}} = 2055 \text{ Hz}$$
- Step 3: First Zero Frequency**
 Slightly smaller than f_{LC} $f_{z1} = 0.9f_{LC} = 0.9 \cdot 2055 = 1850 \text{ Hz}$ $C_3 = 484.7 \text{ pF}$
- Step 4: Second Pole Frequency**
 Select the crossover frequency at $f_t = 10 \text{ kHz}$ (**one decade below** $f_s = 100 \text{ kHz}$) Set $f_{p2} = f_t = 10 \text{ kHz}$

$$f_{p2} = \frac{1}{2\pi R_3 C_3} \Rightarrow R_3 = \frac{1}{2\pi C_3 f_{p2}} = \frac{1}{2\pi \cdot 484.7 \cdot 10^{-12} \cdot 10^4}$$
 $R_3 = 32.84 \text{ k}\Omega$
- Step 5: Required Compensator Gain at the Crossover Frequency**
 $K_{comp} = 1.438 \text{ (3.155 dB)}$
- Step 6: Compensator Gain Setting**

$$K_{comp} = \frac{R_2}{(R_1 || R_3)} \Rightarrow R_2 = K_{comp}(R_1 || R_3) = 1.438 \cdot \left(\frac{177.5 \cdot 10^3 \cdot 32.84 \cdot 10^3}{177.5 \cdot 10^3 + 32.84 \cdot 10^3} \right)$$
 $R_2 = 39.85 \text{ k}\Omega$
- Step 7: Second Zero Frequency**
 Slightly smaller than f_{LC}
 $f_{z2} = 0.9f_{LC} = 0.9 \cdot 2055 = 1850 \text{ Hz}$


$$f_{z2} = \frac{1}{2\pi R_2 C_2} \Rightarrow C_2 = \frac{1}{2\pi R_2 f_{z2}} = \frac{1}{2\pi \cdot 39.85 \cdot 10^3 \cdot 1850}$$
 $C_2 = 2.159 \text{ nF}$
- Step 8: Third Pole Frequency**
 About one decade above $f_t = 10 \text{ kHz}$
 $f_{p3} = 10f_t = 10 \cdot 10^4 = 100 \text{ kHz}$

$$f_{p3} = \frac{1}{2\pi R_2 C_1} \Rightarrow C_1 = \frac{1}{2\pi R_2 f_{p3}} = \frac{1}{2\pi \cdot 39.85 \cdot 10^3 \cdot 10^5}$$
 $C_1 = 39.94 \text{ pF}$

❖ Total Loop Transfer Function:

$$L(s) = M(s)F(s)G_3(s)$$
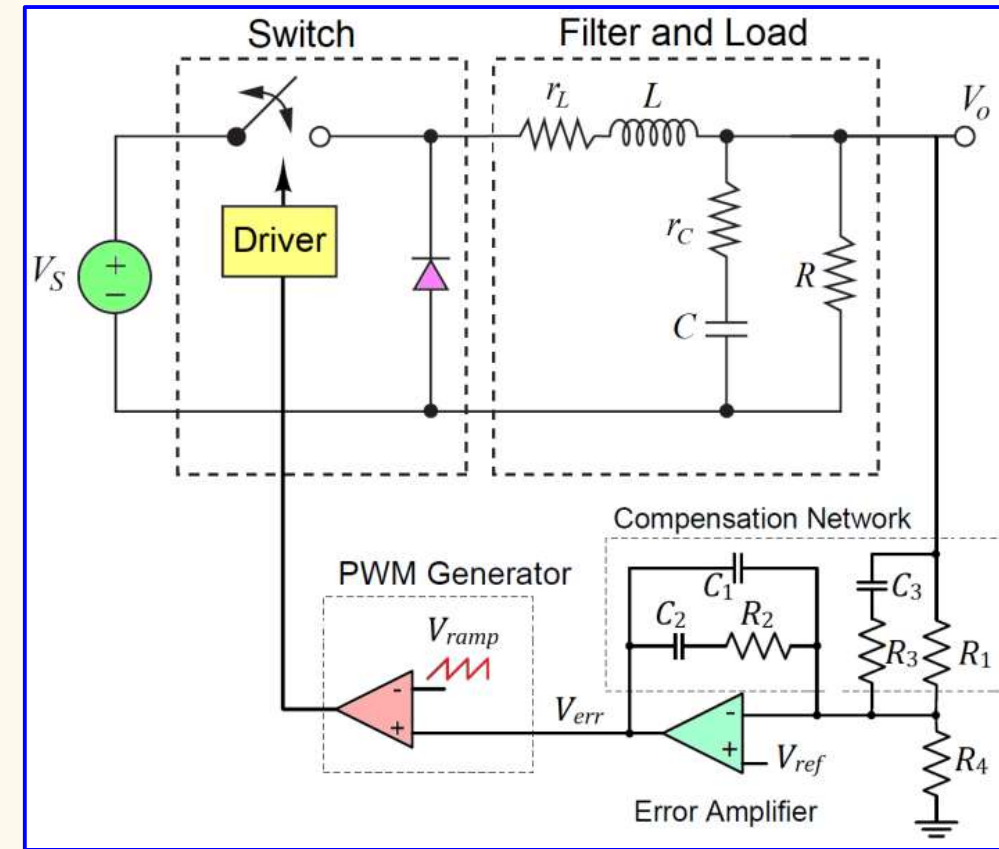
$$L(s) = \frac{V_S}{V_{ramp}} \cdot \frac{1 + r_C s}{1 + \frac{r_L}{R} + \left(\frac{L}{R} + (r_L + r_C)C + \frac{r_L r_C C}{R} \right) s + \left(1 + \frac{r_C}{R} \right) LC s^2} \cdot \frac{1}{R_3 C_1} \cdot \frac{\left(s + \frac{1}{R_1 C_3} \right) \left(s + \frac{1}{R_2 C_2} \right)}{s \left(s + \frac{1}{R_3 C_3} \right) \left(s + \frac{1}{R_2 C_1} \right)}$$



Type 3 Compensated Error Amplifier:


$$G_3(s) \approx -\frac{1}{R_3 C_1} \cdot \frac{\left(s + \frac{1}{R_1 C_3} \right) \left(s + \frac{1}{R_2 C_2} \right)}{s \left(s + \frac{1}{R_3 C_3} \right) \left(s + \frac{1}{R_2 C_1} \right)}$$

Summary: $V_S = 60 \text{ V}$	$R = 7.5 \text{ }\Omega$	$R_1 = 177.5 \text{ k}\Omega$	$C_1 = 39.94 \text{ pF}$
$V_{ramp} = 4 \text{ V}$	$L = 300 \text{ }\mu\text{H}$	$R_2 = 39.85 \text{ k}\Omega$	$C_2 = 2.159 \text{ nF}$
	$C = 20 \text{ }\mu\text{F}$	$R_3 = 32.84 \text{ k}\Omega$	$C_3 = 484.7 \text{ pF}$
	$r_L = 0.025 \text{ }\Omega$	$R_4 = 10 \text{ k}\Omega$	
	$r_C = 0.400 \text{ }\Omega$		

PART 2C:

Simulations

MATLAB/Simulink

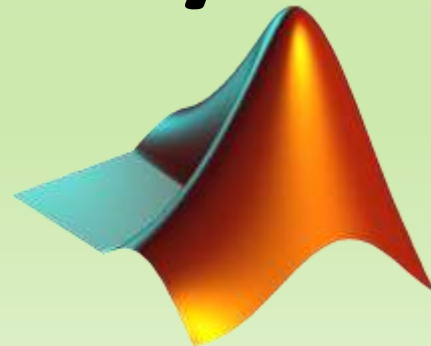

Objective: Design a buck converter circuit with:

- DC input voltage $V_S = 60$ V
- Average output voltage $V_o = 15$ V
- Average output current $I_o = 2$ A

Solution: ☐ Simulations – MATLAB Script

Transfer Functions:

- Modulator: $M(s) = \frac{V_S}{V_{ramp}}$
- Filter & Load: $F(s) = \frac{1 + r_c C s}{1 + \frac{r_L}{R} + \left(\frac{L}{R} + (r_L + r_c)C + \frac{r_L r_c C}{R}\right)s + \left(1 + \frac{r_c}{R}\right)LCs^2}$
- Compensator: $G_3(s) = \frac{1}{R_3 C_1} \cdot \frac{\left(s + \frac{1}{R_1 C_3}\right)\left(s + \frac{1}{R_2 C_2}\right)}{s\left(s + \frac{1}{R_3 C_3}\right)\left(s + \frac{1}{R_2 C_1}\right)}$
- Loop: $L(s) = M(s)F(s)G_3(s)$

```

1  s = tf('s'); % Define a Laplace parameter
2
3  %**SPECIFICATIONS**
4  Vs = 60; Vo = 15; % Input and output DC voltage values
5
6  %**SELECTIONS**
7  f_s = 1e5; % Switching frequency
8
9  %**BUCK CONTROLLER IC: LM5146**
10 Vref = 0.8; % Reference voltage from Buck Controller LM5146
11 Vramp = Vs/15; %Ramp voltage amplitude from Buck Controller LM5146
12 A_DC = 50119; % Error amplifier open-loop DC gain
13 f_pe = 129.7; % Error amplifier open-loop pole
14
15 %**COMPONENTS**
16 R = 7.5; L = 300e-6; C = 20e-6; % Buck converter output filter values
17 r_C = 0.400; % ESR of the capacitor C
18 r_L = 0.025; % ESR of the inductor L
19
20 %**TRANSFER FUNCTIONS**
21 M = Vs/Vramp; % PWM modulator transfer function
22 F = (1+r_C*C*s)/(1+r_L/L + (L/R+(r_C+r_L)*C+r_C*r_L*C/R)*s + (1+r_C/R)*L*C*s^2); % Filter and Load
23
24 %**BREAK FREQUENCIES**
25 f_LC = 1/(2*pi*sqrt(L*C)); % Filter's resonant frequency
26 f_z1 = 0.9*f_LC; % First zero frequency slightly lower than f_LC
27 f_t = 0.1*f_s; % Crossover frequency (selected value one decade below f_s)
28
29 %**CONTROLLER COMPONENT VALUES**
30 R4 = 1e4; % Bottom resistor for reference voltage divider (selected)
31 R1 = (Vo/Vref - 1)*R4; % Top resistor for reference voltage divider
32 C3 = 1/(2*pi*f_z1*R1);
33 R3 = 1/(2*pi*f_t*C3);
34
35 G_MF = M*F; % Loop transfer function Modulator + Filter
36 K_comp = 1.438; % Required compensator gain at the crossover frequency
37
38 R2 = K_comp*(R1^-1+R3^-1)^-1;
39 C2 = 1/(2*pi*0.9*f_LC*R2);
40 C1 = 1/(2*pi*10*f_t*R2);
41
42 %**COMPENSATOR TRANSFER FUNCTION**
43 G_OL = -A_DC/(1+s/(2*pi*f_pe)); % Error amplifier transfer
44 beta = (R1*R3*C1*s*(s+(C1+C2)/(C1*C2*R2))*(s+1/(R3*C3)))/((R1+R3)*(s+1/(R2*C2))*(s+1/((R1+R3)*C3)));
45 G_comp = G_OL/(1+G_OL*beta); % Compensator transfer
46 G_loop = M*F*G_comp;



```

Objective: Design a buck converter circuit with:

- DC input voltage $V_S = 60\text{ V}$
- Average output voltage $V_o = 15\text{ V}$
- Average output current $I_o = 2\text{ A}$

Summary: $V_S = 60\text{ V}$ $R = 7.5\ \Omega$ $R_1 = 177.5\text{ k}\Omega$ $C_1 = 39.94\text{ pF}$
 $V_{ramp} = 4\text{ V}$ $L = 300\ \mu\text{H}$ $R_2 = 39.85\text{ k}\Omega$ $C_2 = 2.159\text{ nF}$
 $C = 20\ \mu\text{F}$ $R_3 = 32.84\text{ k}\Omega$ $C_3 = 484.7\text{ pF}$
 $r_L = 0.025\ \Omega$ $R_4 = 10\text{ k}\Omega$
 $r_C = 0.400\ \Omega$

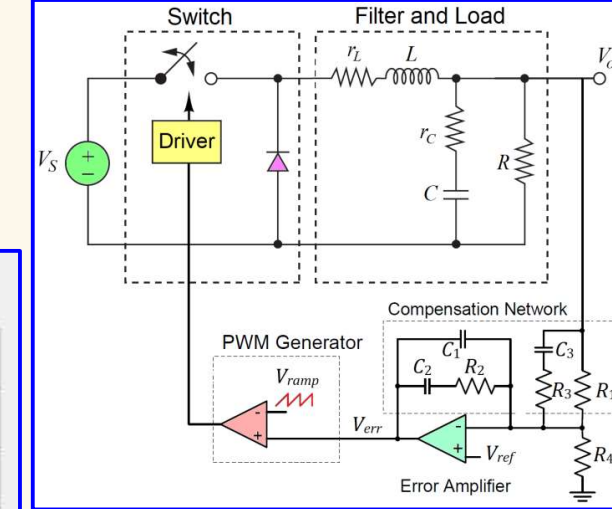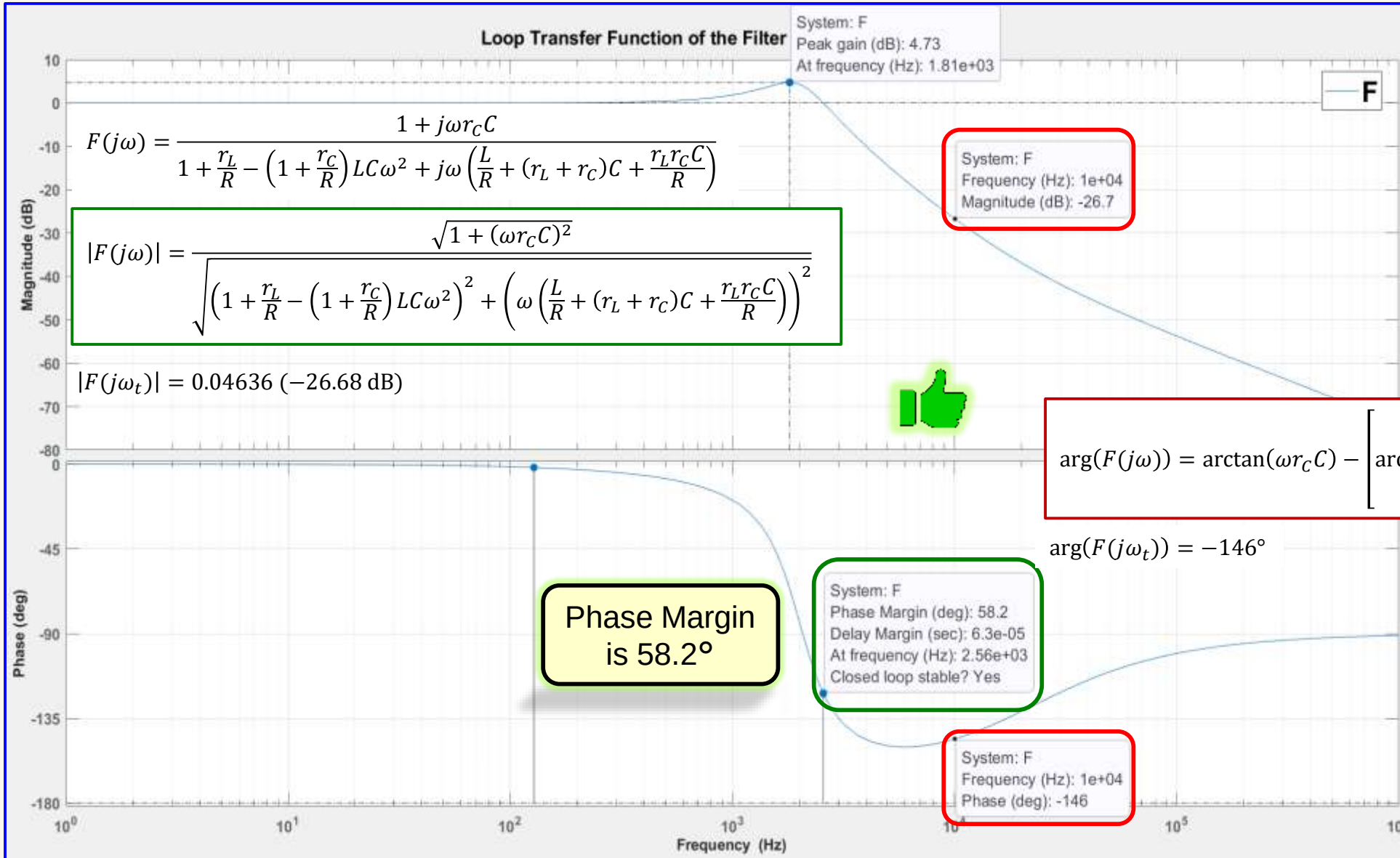Solution: ☐ Simulations – Loop Transfer Function of the Filter





Objective: Design a buck converter circuit with:

- DC input voltage $V_S = 60\text{ V}$
- Average output voltage $V_o = 15\text{ V}$
- Average output current $I_o = 2\text{ A}$

Summary: $V_S = 60\text{ V}$ $R = 7.5\ \Omega$ $R_1 = 177.5\text{ k}\Omega$ $C_1 = 39.94\text{ pF}$
 $V_{ramp} = 4\text{ V}$ $L = 300\ \mu\text{H}$ $R_2 = 39.85\text{ k}\Omega$ $C_2 = 2.159\text{ nF}$
 $C = 20\ \mu\text{F}$ $R_3 = 32.84\text{ k}\Omega$ $C_3 = 484.7\text{ pF}$
 $r_L = 0.025\ \Omega$ $R_4 = 10\text{ k}\Omega$
 $r_C = 0.400\ \Omega$

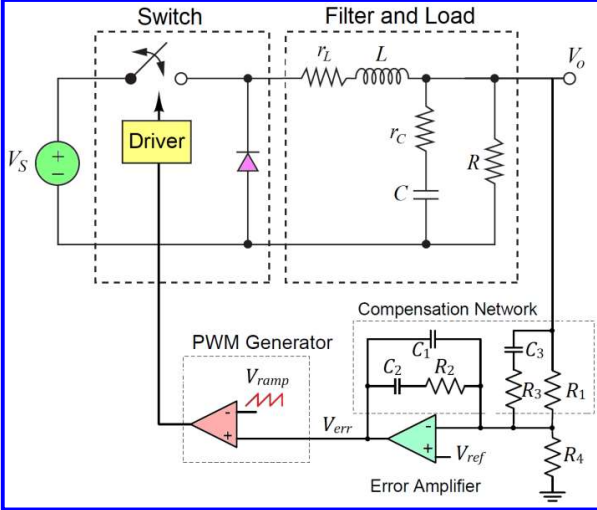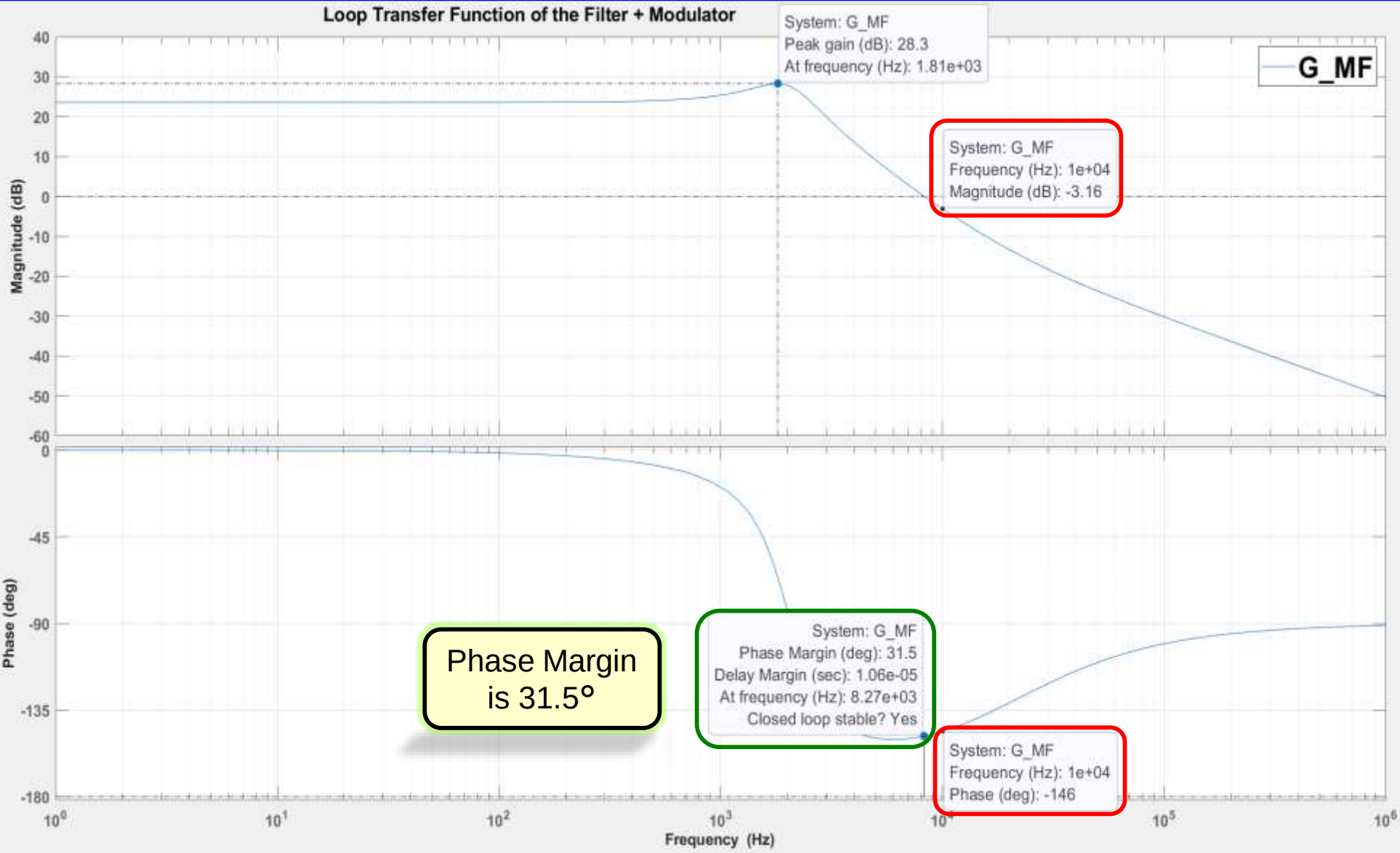Solution: ☐ Simulations – Loop Transfer Function of the Filter + Modulator





Objective: Design a buck converter circuit with:

- DC input voltage $V_S = 60\text{ V}$
- Average output voltage $V_o = 15\text{ V}$
- Average output current $I_o = 2\text{ A}$

Summary: $V_S = 60\text{ V}$ $R = 7.5\ \Omega$ $R_1 = 177.5\text{ k}\Omega$ $C_1 = 39.94\text{ pF}$
 $V_{ramp} = 4\text{ V}$ $L = 300\ \mu\text{H}$ $R_2 = 39.85\text{ k}\Omega$ $C_2 = 2.159\text{ nF}$
 $C = 20\ \mu\text{F}$ $R_3 = 32.84\text{ k}\Omega$ $C_3 = 484.7\text{ pF}$
 $r_L = 0.025\ \Omega$ $R_4 = 10\text{ k}\Omega$
 $r_C = 0.400\ \Omega$

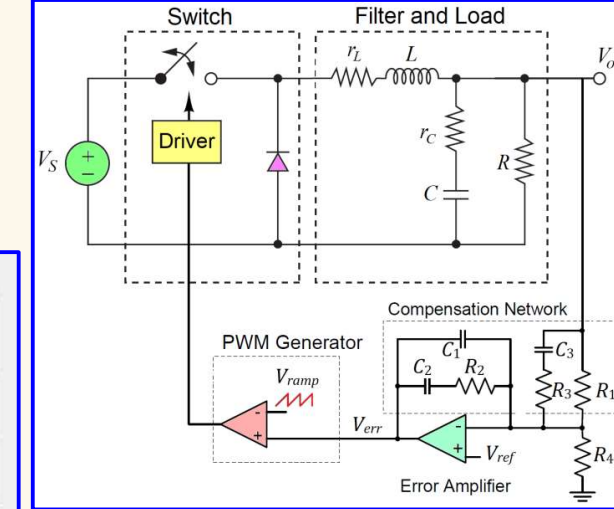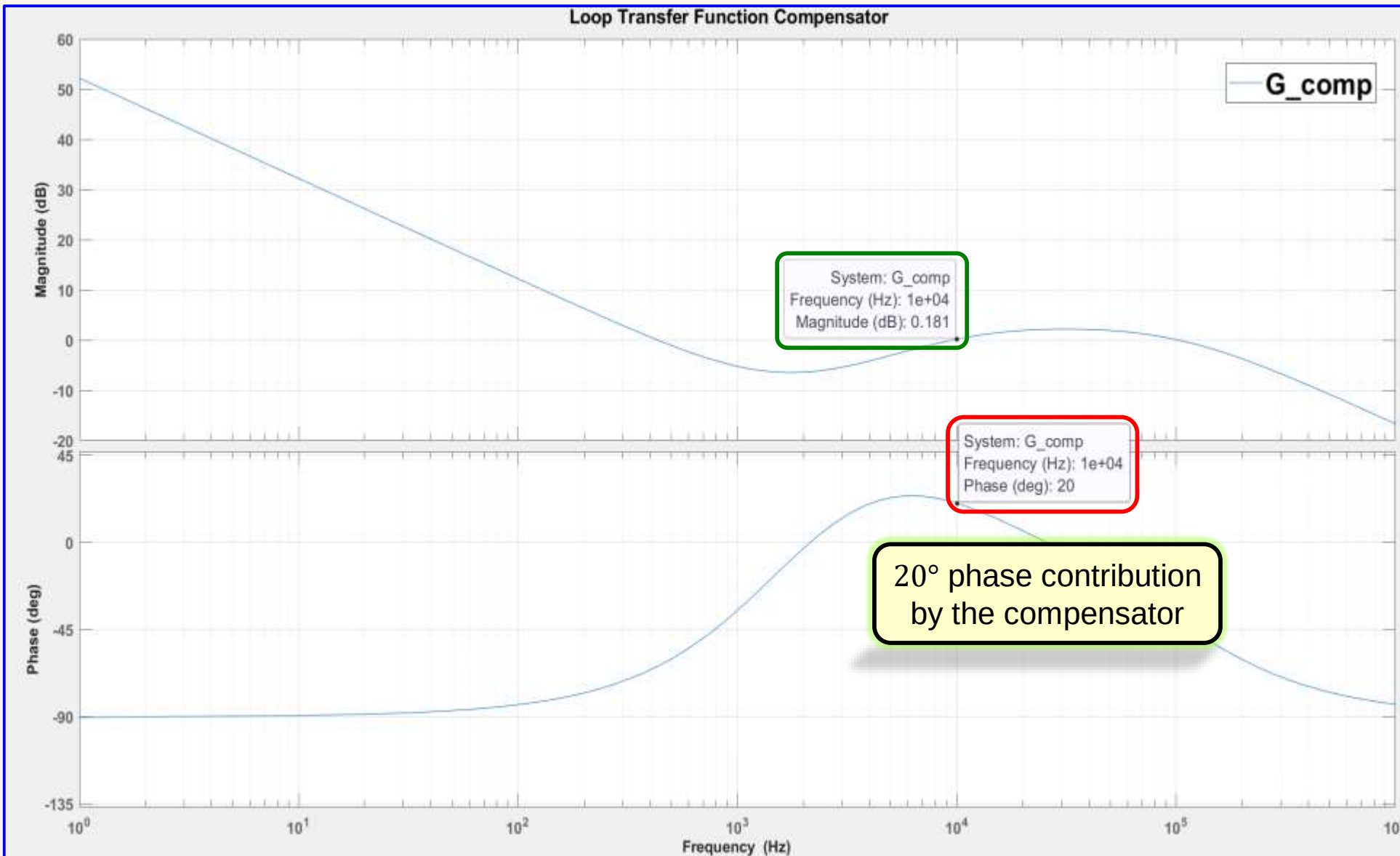Solution: ☐ Simulations – Loop Transfer Function Compensator





Objective: Design a buck converter circuit with:

- DC input voltage $V_S = 60\text{ V}$
- Average output voltage $V_o = 15\text{ V}$
- Average output current $I_o = 2\text{ A}$

Summary: $V_S = 60\text{ V}$ $R = 7.5\ \Omega$ $R_1 = 177.5\text{ k}\Omega$ $C_1 = 39.94\text{ pF}$
 $V_{ramp} = 4\text{ V}$ $L = 300\ \mu\text{H}$ $R_2 = 39.85\text{ k}\Omega$ $C_2 = 2.159\text{ nF}$
 $C = 20\ \mu\text{F}$ $R_3 = 32.84\text{ k}\Omega$ $C_3 = 484.7\text{ pF}$
 $r_L = 0.025\ \Omega$ $R_4 = 10\text{ k}\Omega$
 $r_C = 0.400\ \Omega$

Solution: ☐ Simulations – Loop Transfer Function Filter + Modulator + Compensator

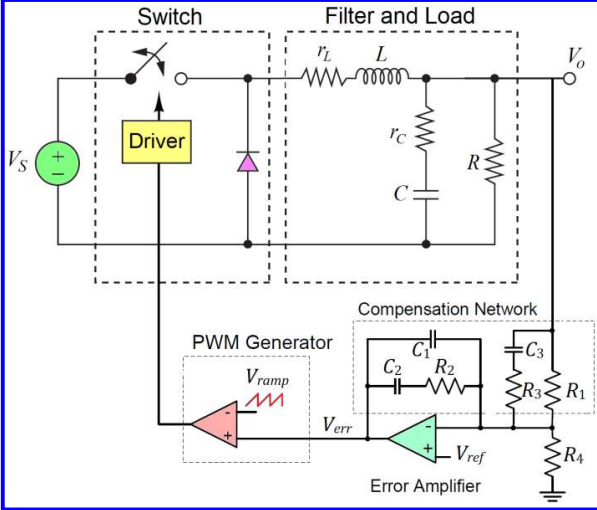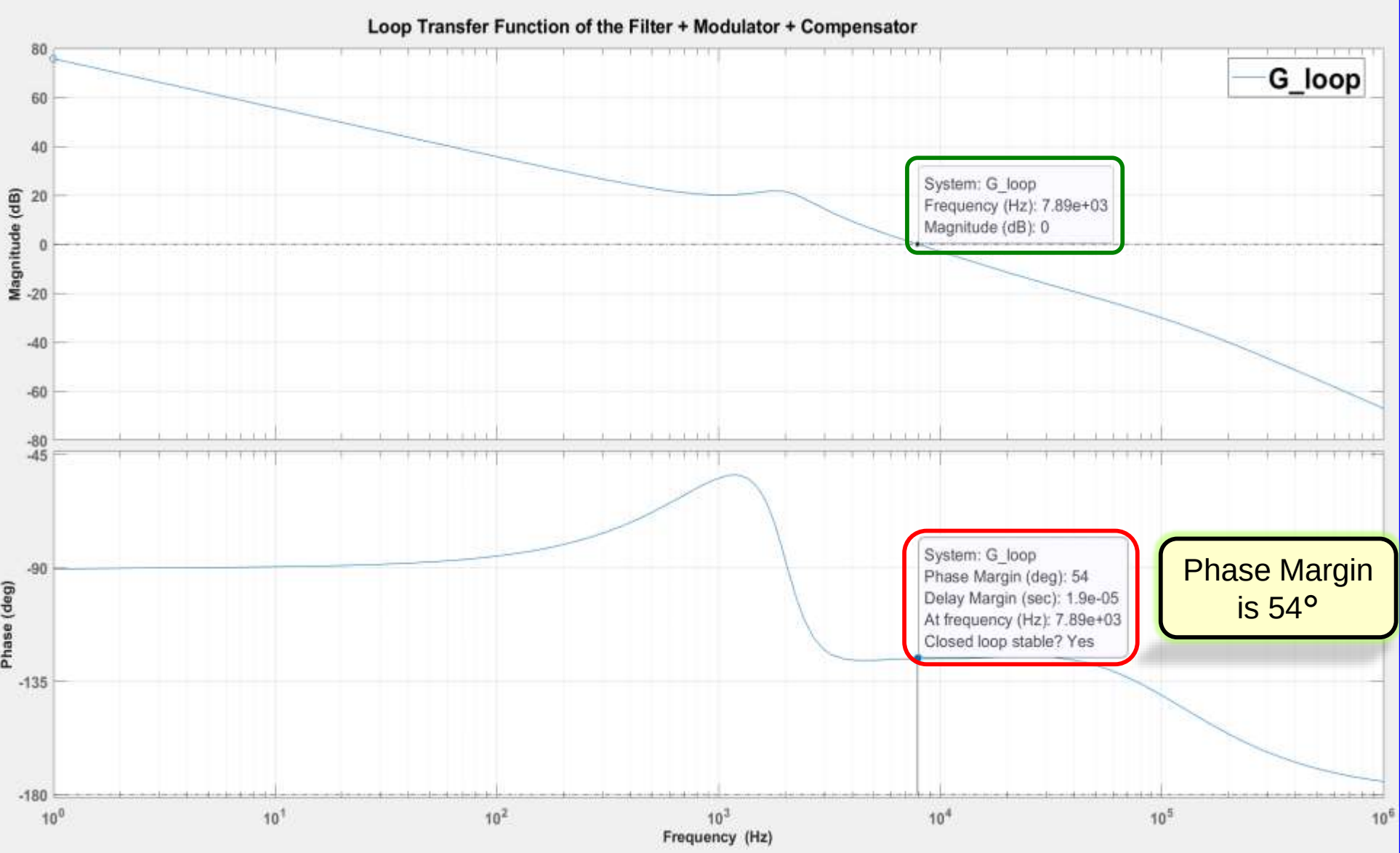

PART 2C:

Simulations

TINA-TI SPICE





Objective: Design a buck converter circuit with:


- DC input voltage $V_S = 60\text{ V}$
- Average output voltage $V_o = 15\text{ V}$
- Average output current $I_o = 2\text{ A}$

Solution:  *Simulations – Circuits*

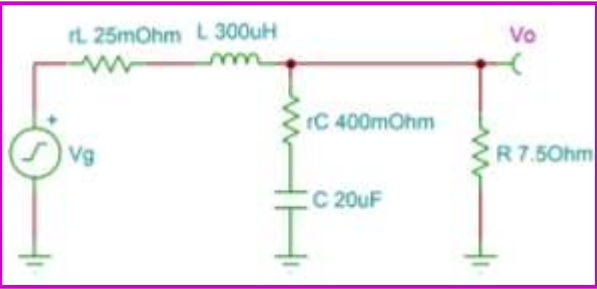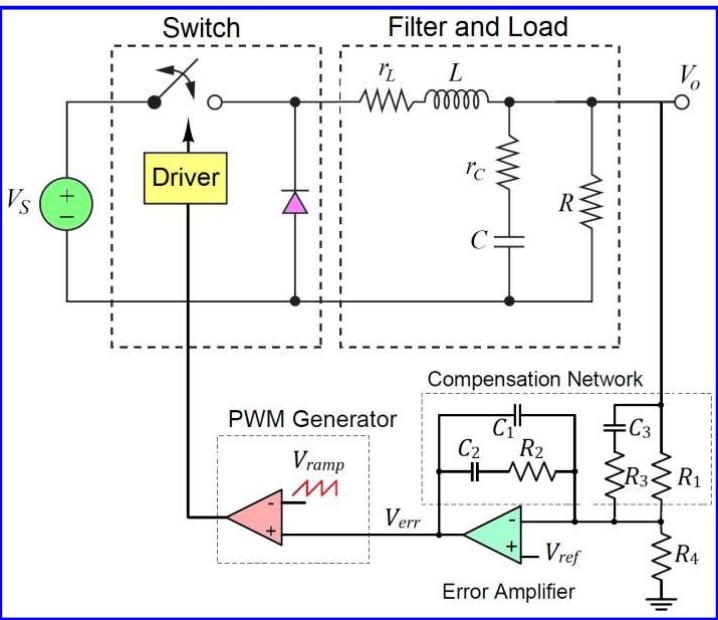
Summary: $V_S = 60\text{ V}$ $R = 7.5\ \Omega$ $R_1 = 177.5\text{ k}\Omega$ $C_1 = 39.94\text{ pF}$
 $V_{ramp} = 4\text{ V}$ $L = 300\ \mu\text{H}$ $R_2 = 39.85\text{ k}\Omega$ $C_2 = 2.159\text{ nF}$
 $C = 20\ \mu\text{F}$ $R_3 = 32.84\text{ k}\Omega$ $C_3 = 484.7\text{ pF}$
 $r_L = 0.025\ \Omega$ $R_4 = 10\text{ k}\Omega$
 $r_C = 0.400\ \Omega$




Filter

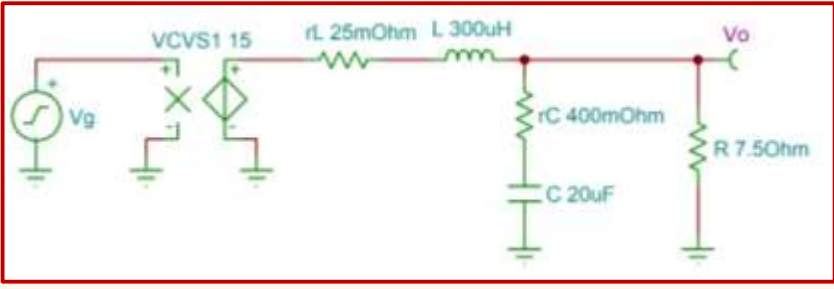

Filter & Modulator

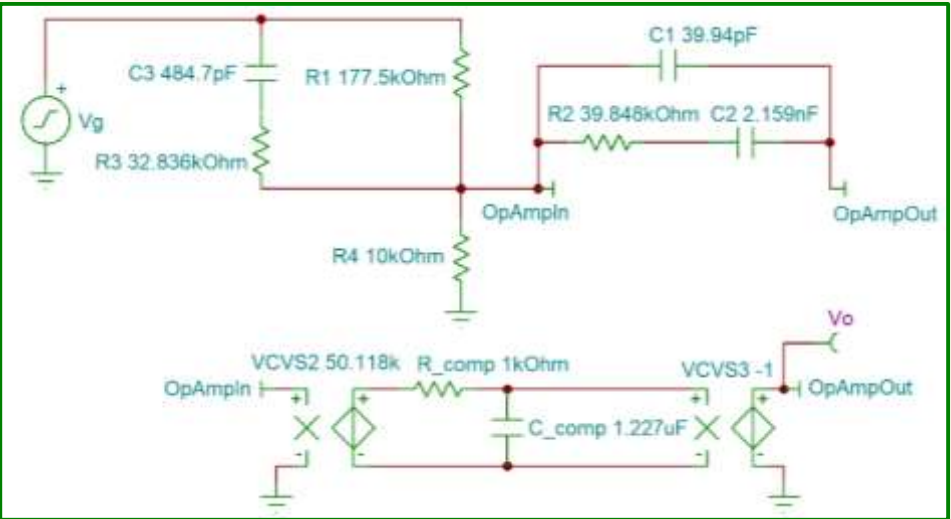

Compensator

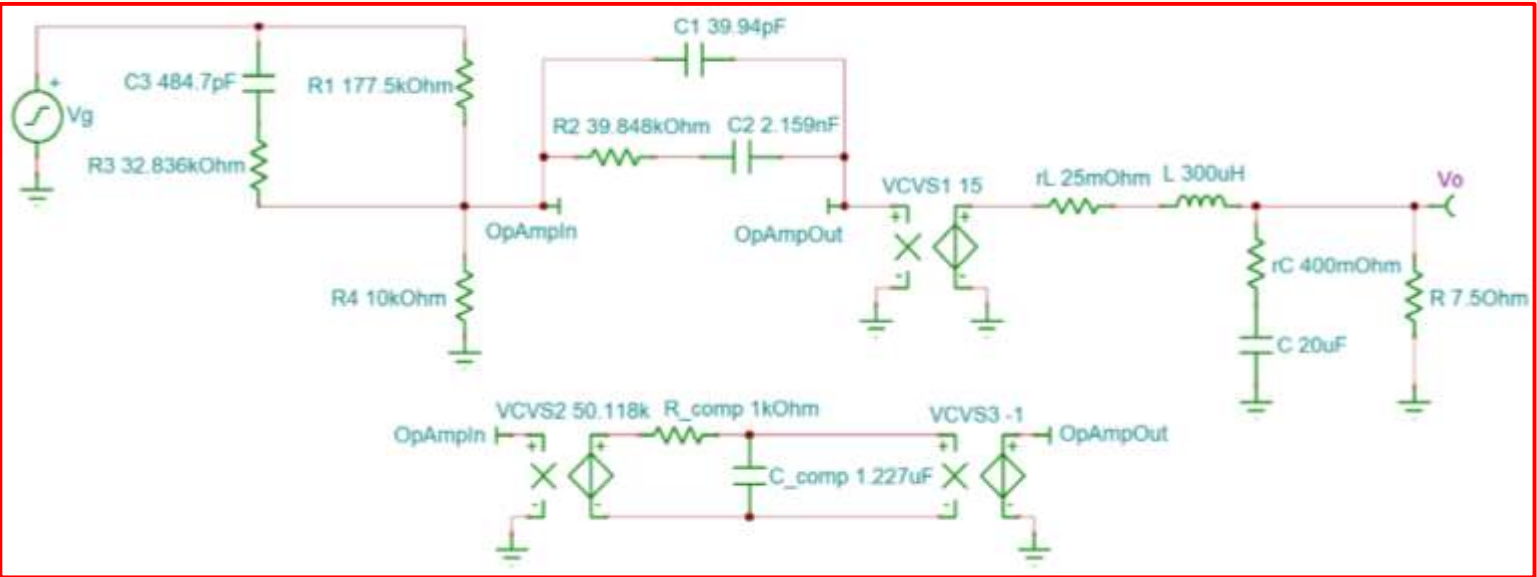



Filter & Modulator & Compensator

- Error Amplifier Open-Loop DC Voltage Gain: $A_{OL} = 94\text{ dB}$ (50118 V/V)
- Error Amplifier Open-Loop Compensation Pole: $f_{pe} = 129.7\text{ Hz}$

Objective: Design a buck converter circuit with:

- DC input voltage $V_S = 60\text{ V}$
- Average output voltage $V_o = 15\text{ V}$
- Average output current $I_o = 2\text{ A}$

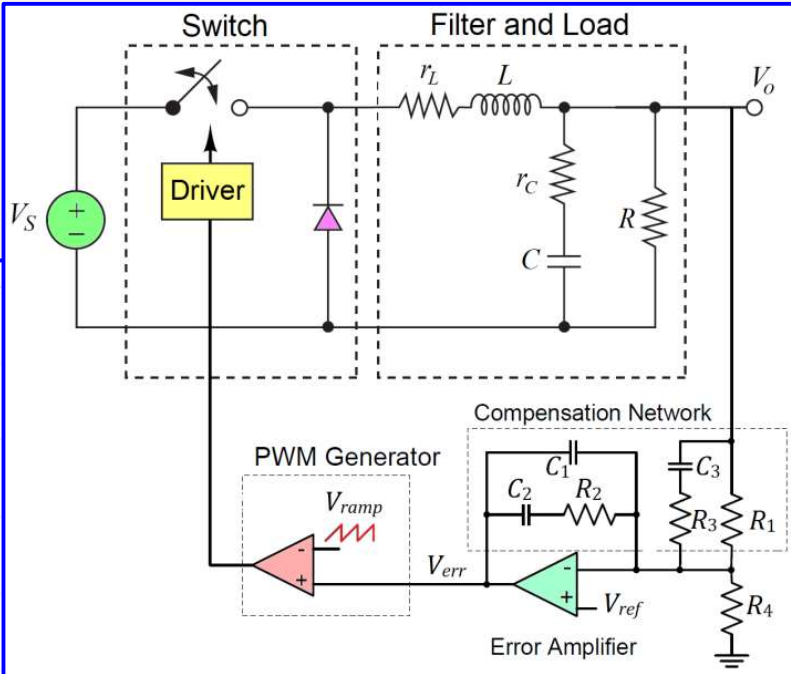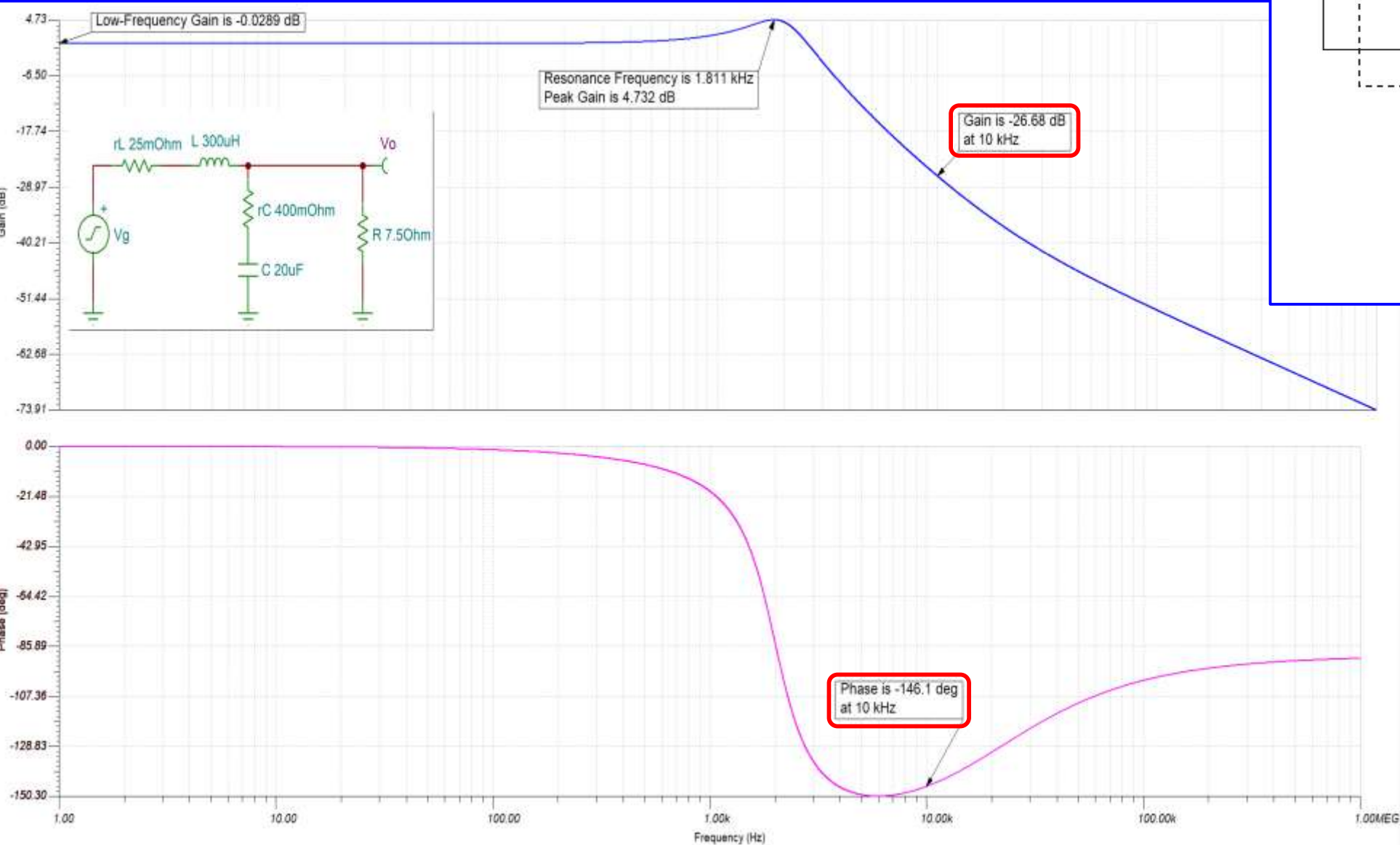Solution: ☐ Simulations – Loop Transfer Function of the Filter



Summary:



$V_S = 60\text{ V}$ $R = 7.5\ \Omega$
 $V_{ramp} = 4\text{ V}$ $L = 300\ \mu\text{H}$
 $C = 20\ \mu\text{F}$
 $r_L = 0.025\ \Omega$
 $r_C = 0.400\ \Omega$

$R_1 = 177.5\text{ k}\Omega$ $C_1 = 39.94\text{ pF}$
 $R_2 = 39.85\text{ k}\Omega$ $C_2 = 2.159\text{ nF}$
 $R_3 = 32.84\text{ k}\Omega$ $C_3 = 484.7\text{ pF}$
 $R_4 = 10\text{ k}\Omega$

Objective: Design a buck converter circuit with:

- DC input voltage $V_S = 60\text{ V}$
- Average output voltage $V_o = 15\text{ V}$
- Average output current $I_o = 2\text{ A}$

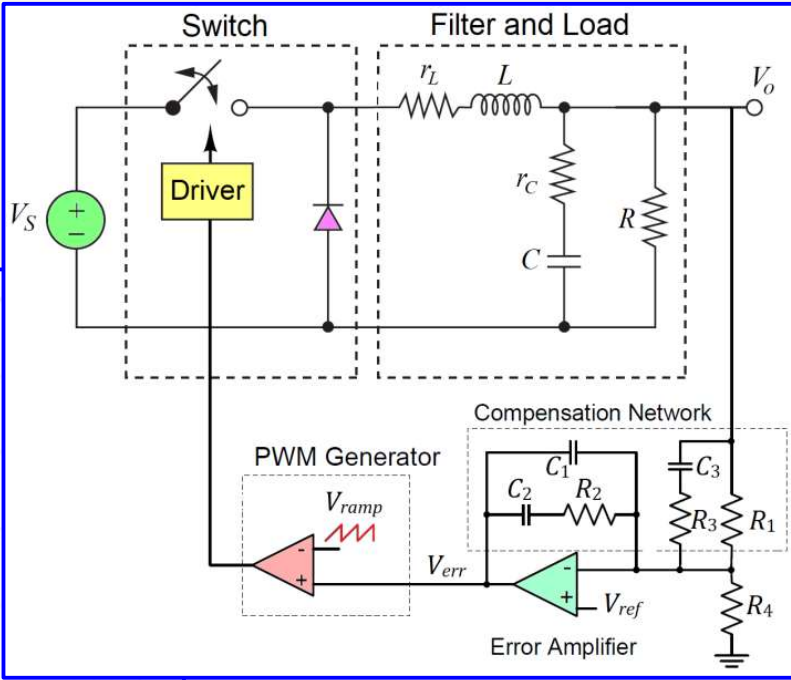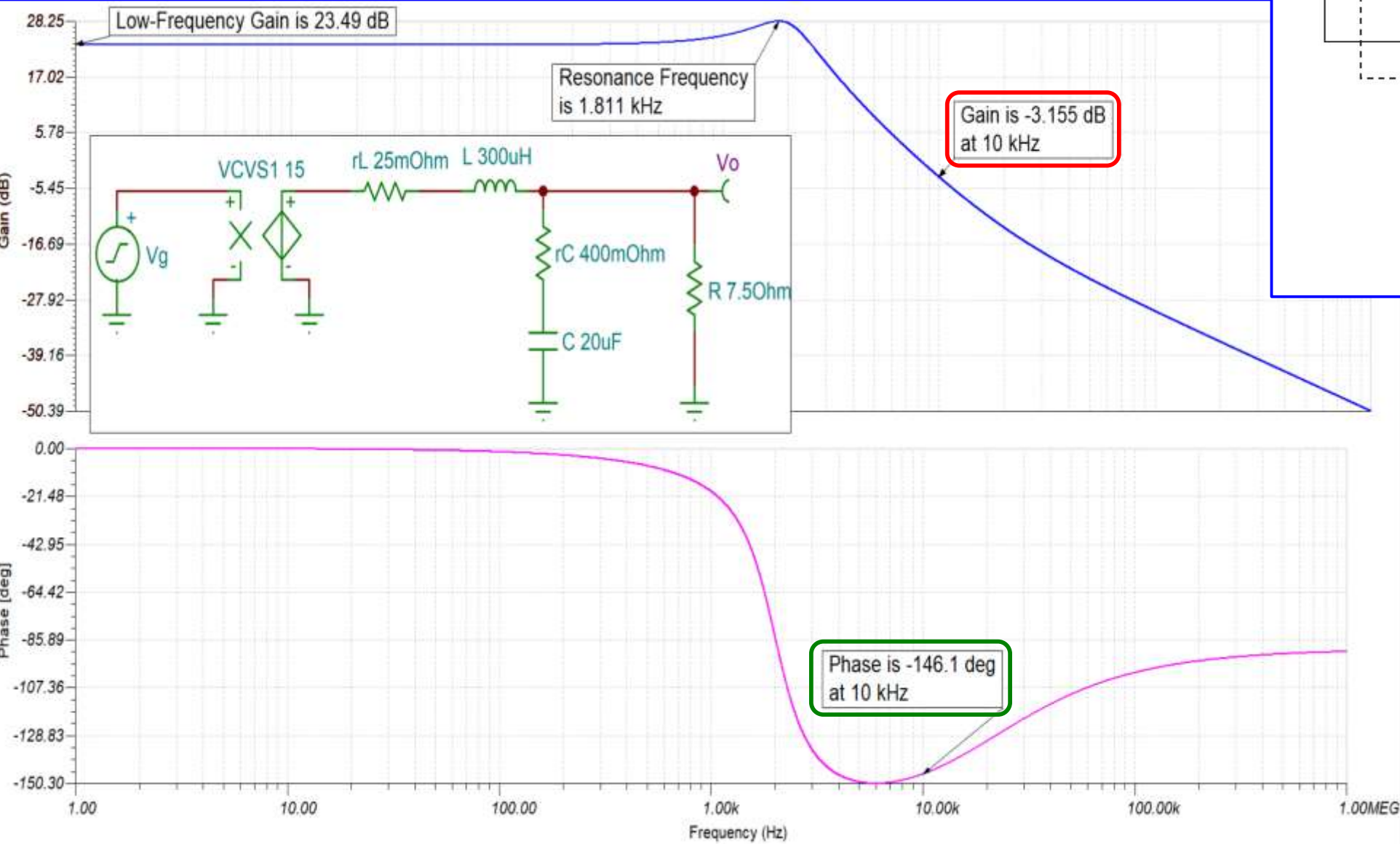Solution: ☐ Simulations – Loop Transfer Function of the Filter + Modulator



Summary:



$V_S = 60\text{ V}$ $R = 7.5\ \Omega$
 $V_{ramp} = 4\text{ V}$ $L = 300\ \mu\text{H}$
 $C = 20\ \mu\text{F}$
 $r_L = 0.025\ \Omega$
 $r_C = 0.400\ \Omega$

$R_1 = 177.5\text{ k}\Omega$ $C_1 = 39.94\text{ pF}$
 $R_2 = 39.85\text{ k}\Omega$ $C_2 = 2.159\text{ nF}$
 $R_3 = 32.84\text{ k}\Omega$ $C_3 = 484.7\text{ pF}$
 $R_4 = 10\text{ k}\Omega$

Objective: Design a buck converter circuit with:

- DC input voltage $V_S = 60\text{ V}$
- Average output voltage $V_o = 15\text{ V}$
- Average output current $I_o = 2\text{ A}$

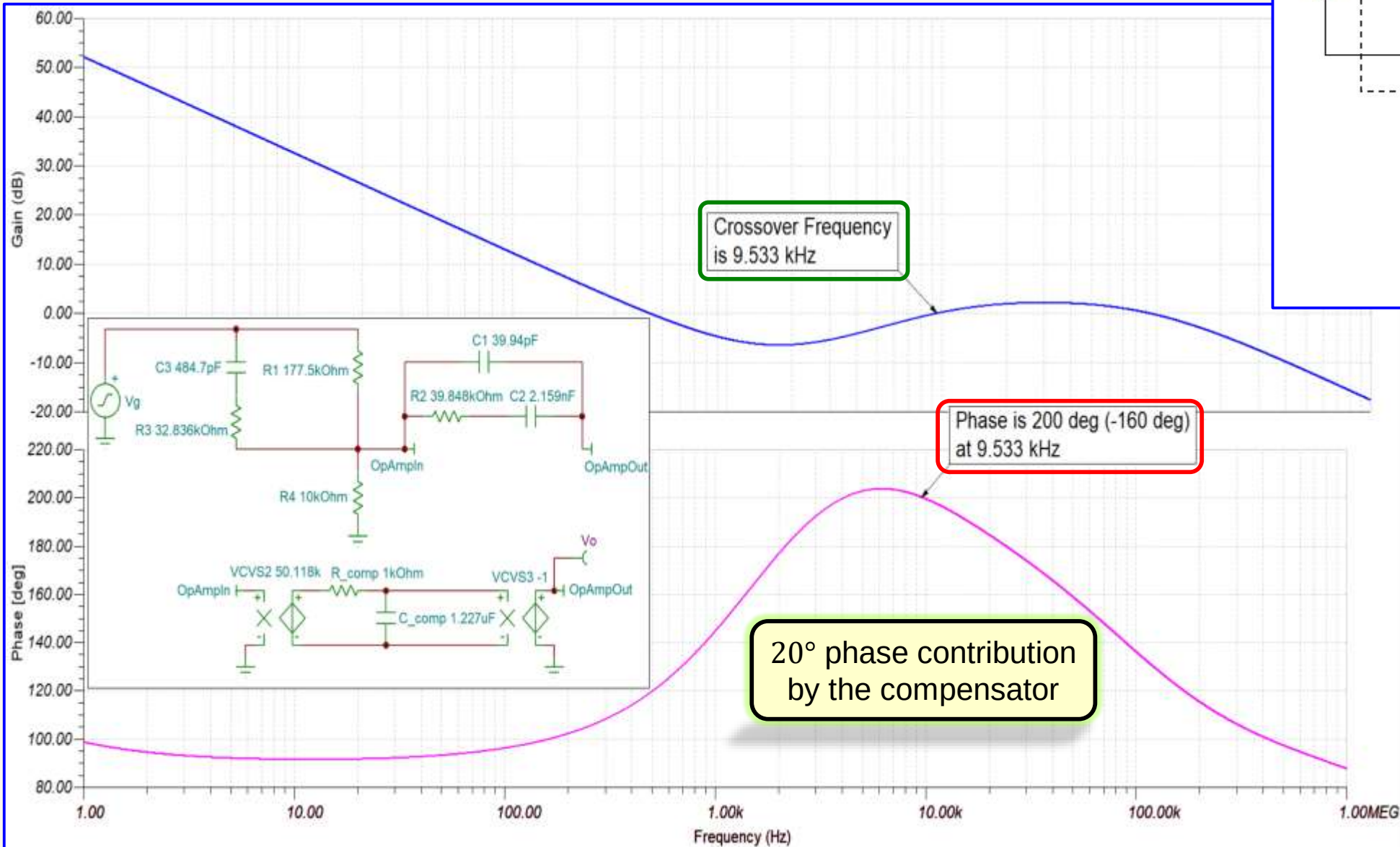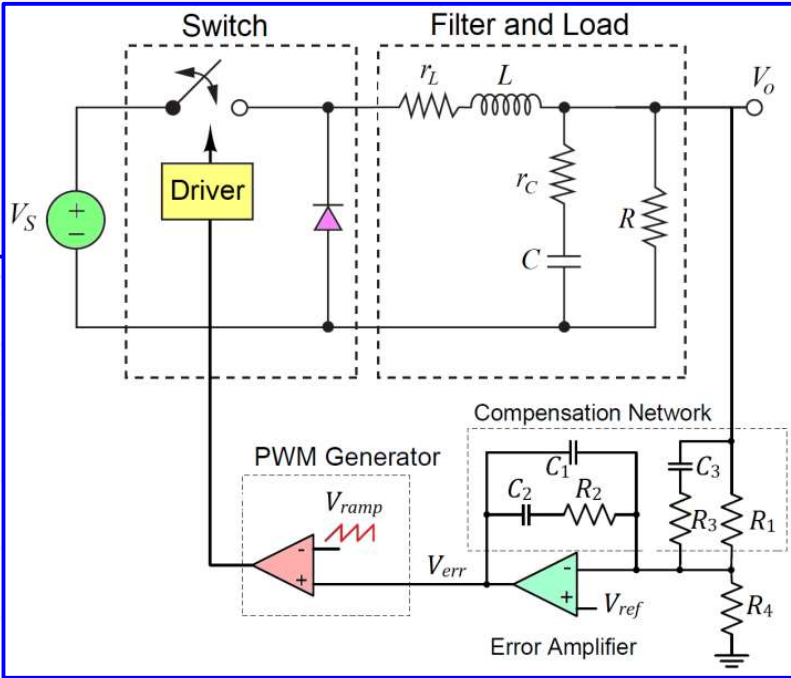Solution: ☐ Simulations – Loop Transfer Function Compensator



Summary:



$V_S = 60\text{ V}$ $R = 7.5\ \Omega$
 $V_{ramp} = 4\text{ V}$ $L = 300\ \mu\text{H}$
 $C = 20\ \mu\text{F}$
 $r_L = 0.025\ \Omega$
 $r_C = 0.400\ \Omega$

$R_1 = 177.5\text{ k}\Omega$ $C_1 = 39.94\text{ pF}$
 $R_2 = 39.85\text{ k}\Omega$ $C_2 = 2.159\text{ nF}$
 $R_3 = 32.84\text{ k}\Omega$ $C_3 = 484.7\text{ pF}$
 $R_4 = 10\text{ k}\Omega$

Objective: Design a buck converter circuit with:

- DC input voltage $V_S = 60\text{ V}$
- Average output voltage $V_o = 15\text{ V}$
- Average output current $I_o = 2\text{ A}$

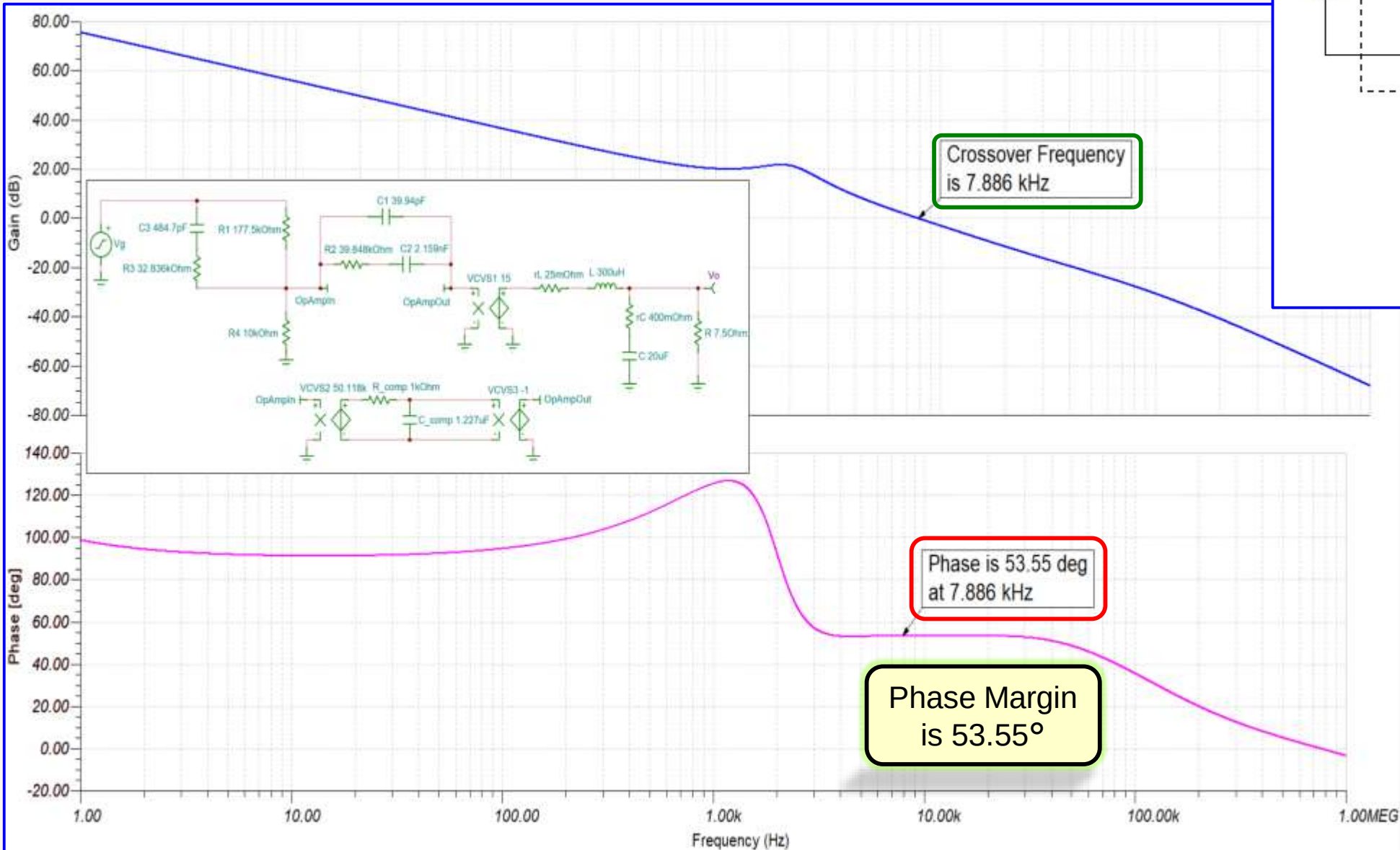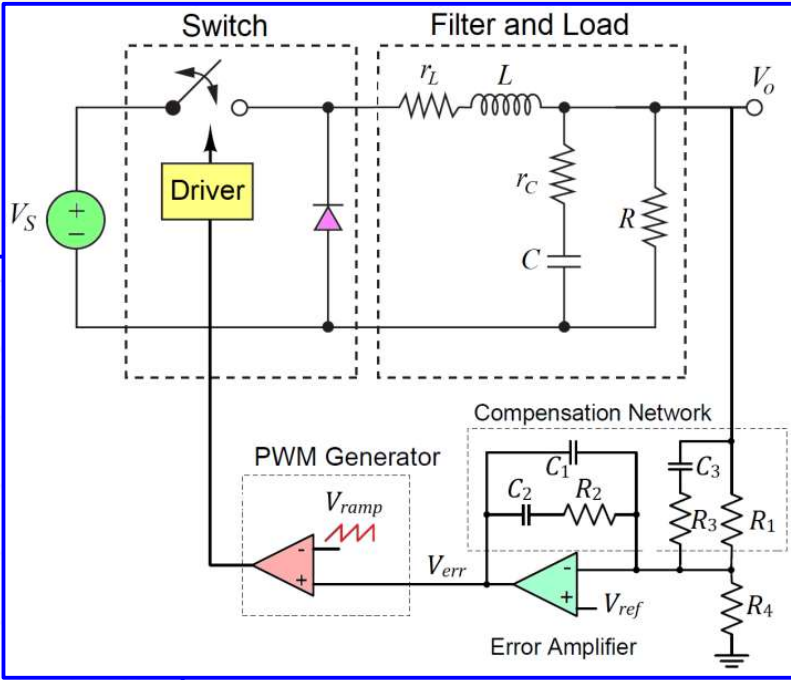Solution: ☐ Simulations – Loop Transfer Function Filter + Modulator + Compensator



Summary:

$V_S = 60\text{ V}$ $R = 7.5\ \Omega$
 $V_{ramp} = 4\text{ V}$ $L = 300\ \mu\text{H}$
 $C = 20\ \mu\text{F}$
 $r_L = 0.025\ \Omega$
 $r_C = 0.400\ \Omega$

$R_1 = 177.5\text{ k}\Omega$ $C_1 = 39.94\text{ pF}$
 $R_2 = 39.85\text{ k}\Omega$ $C_2 = 2.159\text{ nF}$
 $R_3 = 32.84\text{ k}\Omega$ $C_3 = 484.7\text{ pF}$
 $R_4 = 10\text{ k}\Omega$