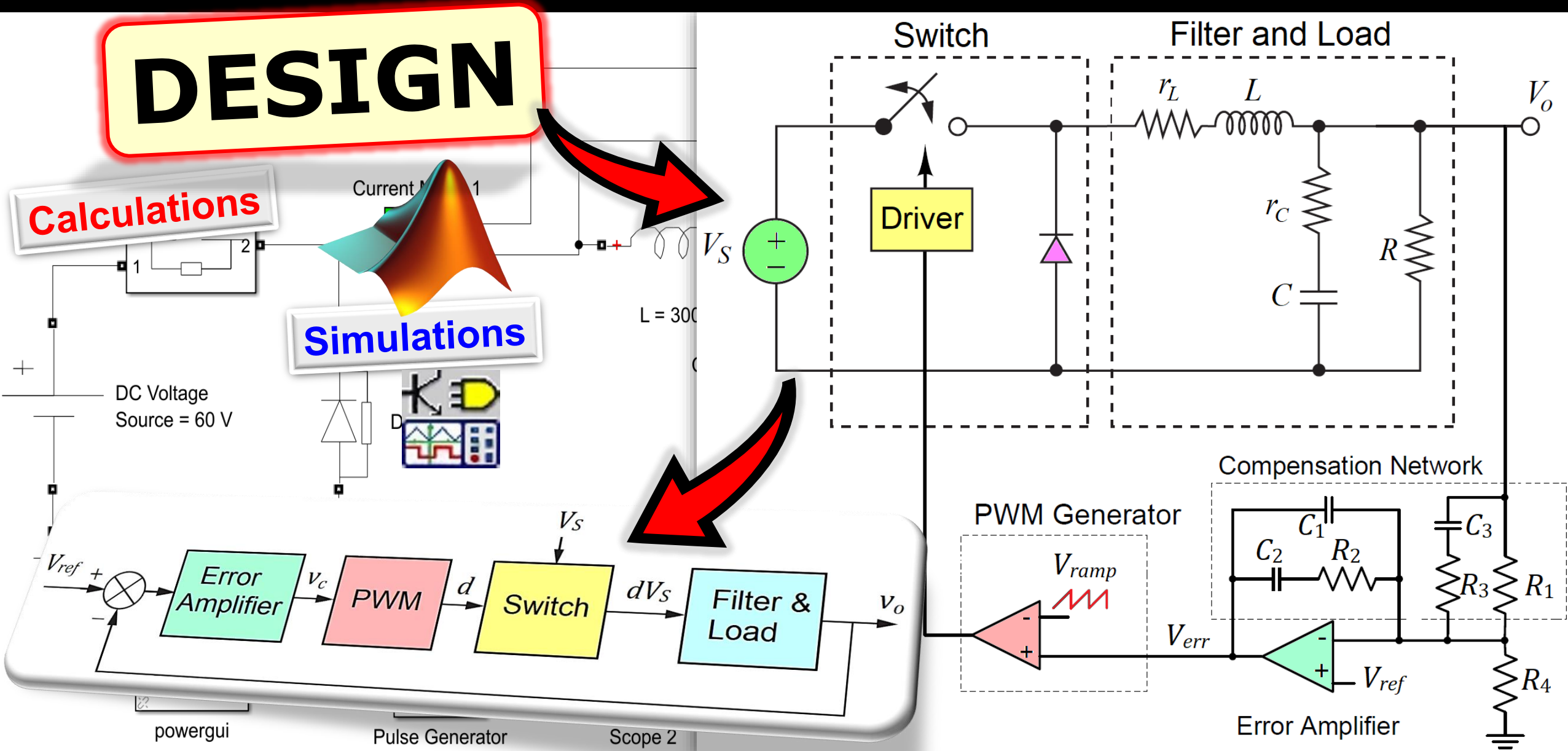


TYPE 3 COMPENSATOR





DESIGN

Calculations

Simulations



Theory

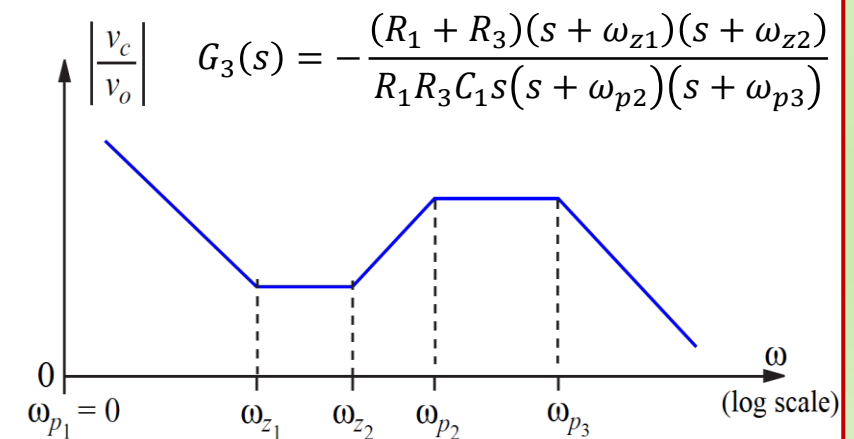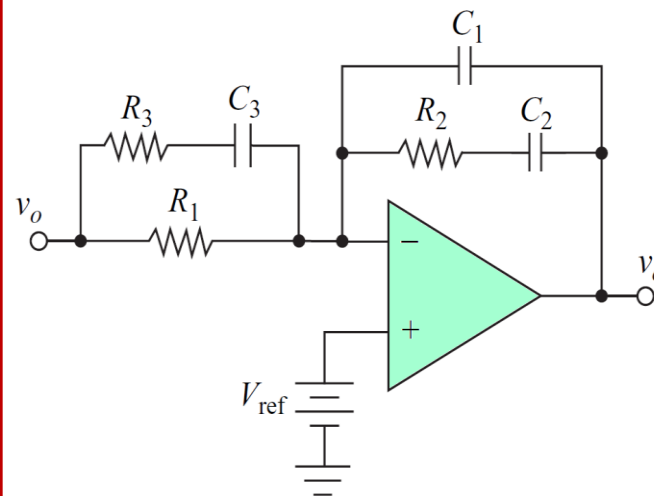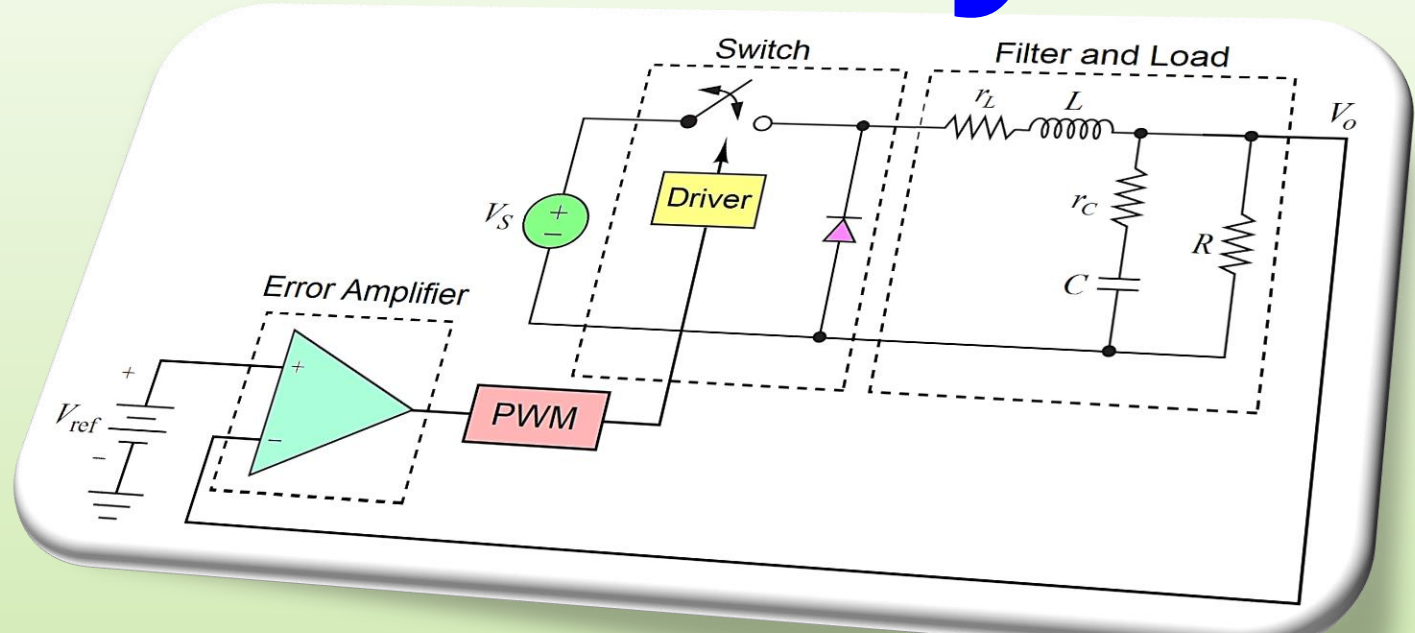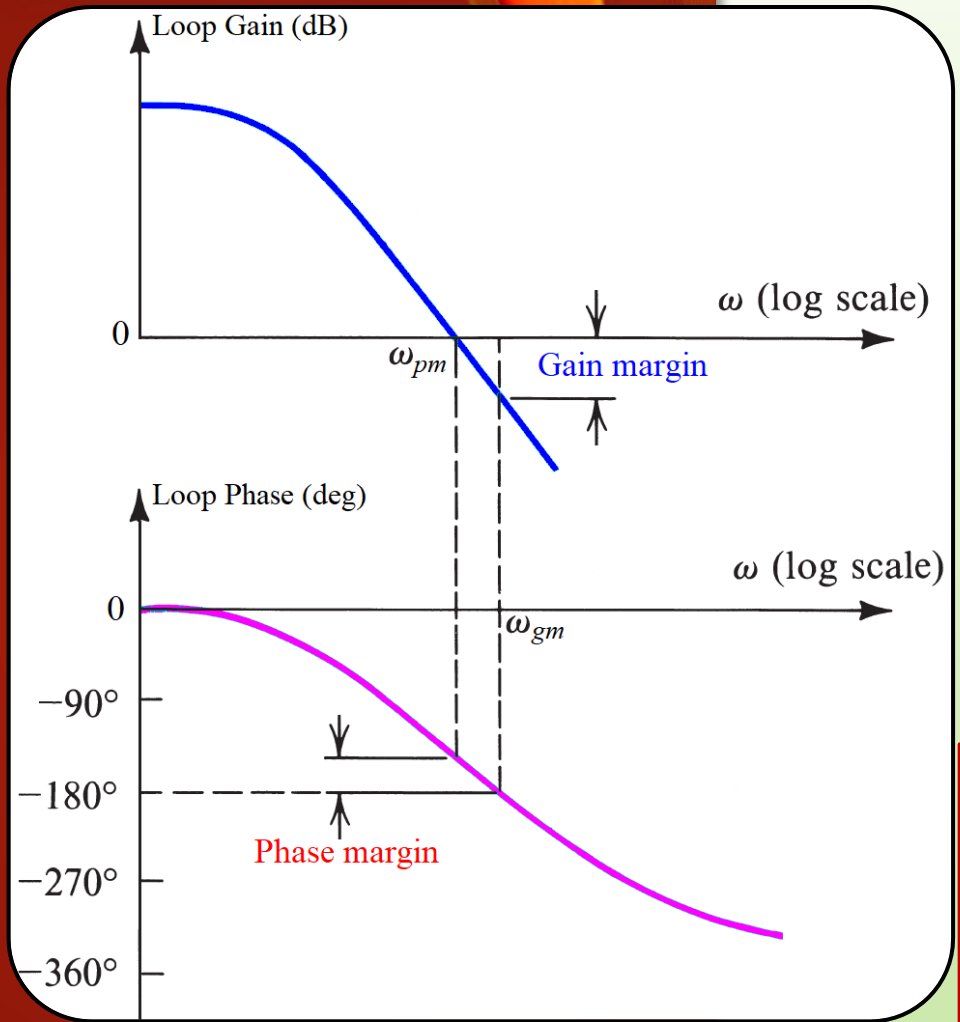

1. Frequency Response Analysis

❖ Stability Margins

▪ Gain Margin:

1. Find the **frequency** where the **loop phase** is -180° . This frequency is called ω_{gm} .
2. Determine the **loop gain** at ω_{gm} .
3. The **gain margin (GM)** is the gain required to **raise** the **magnitude curve** to 0 dB.

▪ Phase Margin:

1. Find the **frequency** where the **loop gain** is 0 dB. This frequency is called ω_{pm} .
2. The **phase margin (PM)** is the **difference** between the **loop phase** at ω_{pm} and -180° .

Example:

Loop transfer function: $L(j\omega) = \frac{1000}{(j\omega + 4)(j\omega + 8)(j\omega + 10)}$

Determine:

- Phase margin (PM)
- Gain margin (GM)

Phase Margin: $|L(j\omega)| = 1 \Rightarrow \frac{1000}{\sqrt{\omega^2 + 4^2}\sqrt{\omega^2 + 8^2}\sqrt{\omega^2 + 10^2}} = 1$

Solving:
 $\omega = 6.79 \text{ rad/s} \equiv \omega_{pm}$

$$\arg(L(j\omega_{pm})) = -\arctan\left(\frac{\omega_{pm}}{4}\right) - \arctan\left(\frac{\omega_{pm}}{8}\right) - \arctan\left(\frac{\omega_{pm}}{10}\right) = -134^\circ$$


$$PM = 180 + \arg(L(j\omega_{pm})) = 46^\circ$$

Gain Margin: $\arg(L(j\omega)) = -\arctan\left(\frac{\omega}{4}\right) - \arctan\left(\frac{\omega}{8}\right) - \arctan\left(\frac{\omega}{10}\right) = -180^\circ$

Solving:
 $\omega = 12.33 \text{ rad/s} \equiv \omega_{gm}$

$$|L(j\omega_{gm})| = \frac{1000}{\sqrt{\omega_{gm}^2 + 4^2}\sqrt{\omega_{gm}^2 + 8^2}\sqrt{\omega_{gm}^2 + 10^2}} = 0.3307 \text{ } (-9.61 \text{ dB})$$

$$GM = \frac{1}{|L(j\omega_{gm})|} = 3.024 \text{ } (9.61 \text{ dB})$$

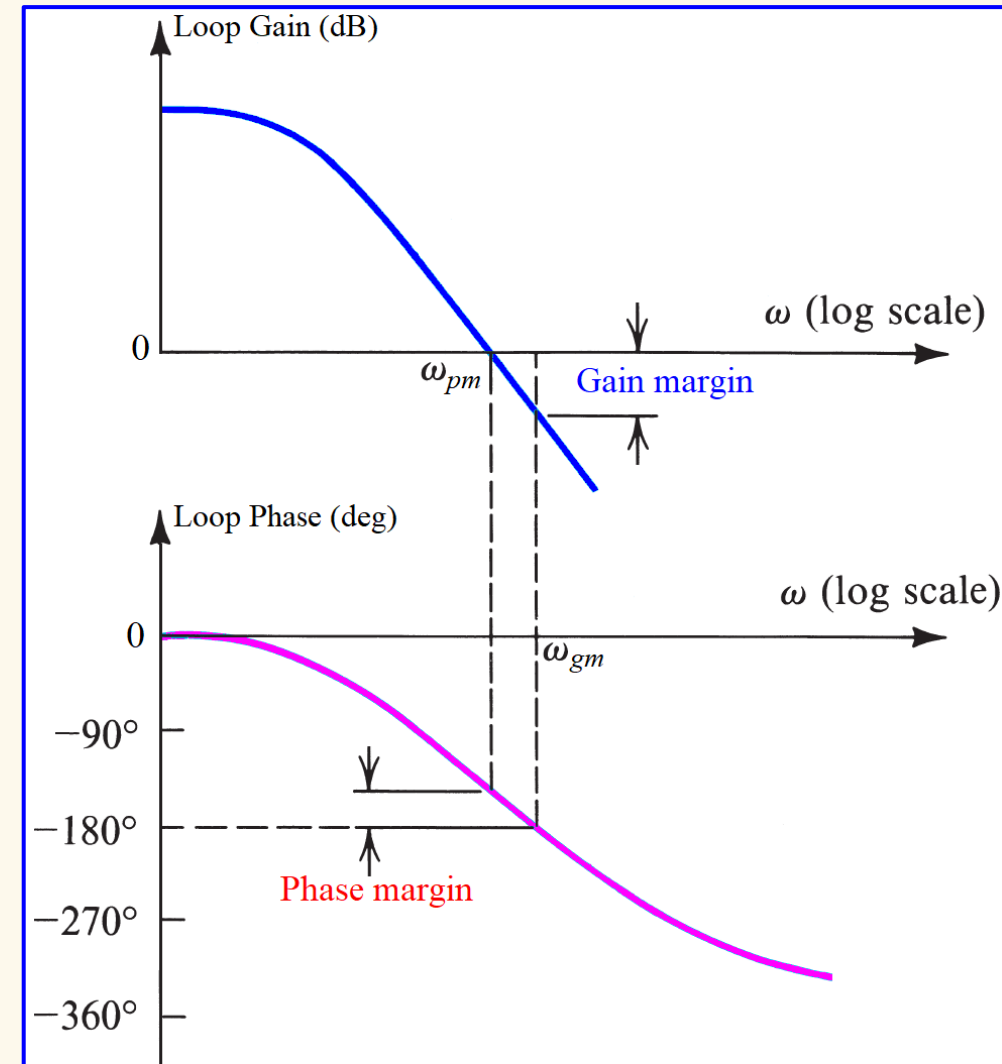

1. Frequency Response Analysis



Example:

Loop transfer function: $L(j\omega) = \frac{1000}{(j\omega + 4)(j\omega + 8)(j\omega + 10)}$

Determine:

- Phase margin (PM)
- Gain margin (GM)

Simulation Results:

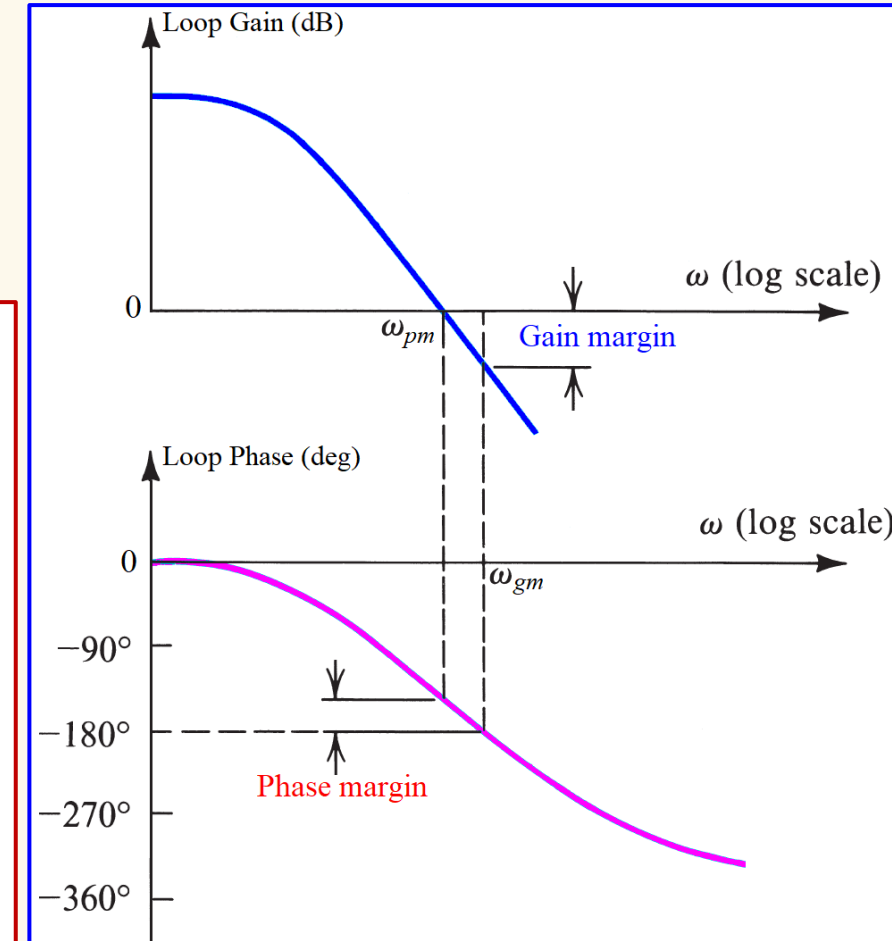
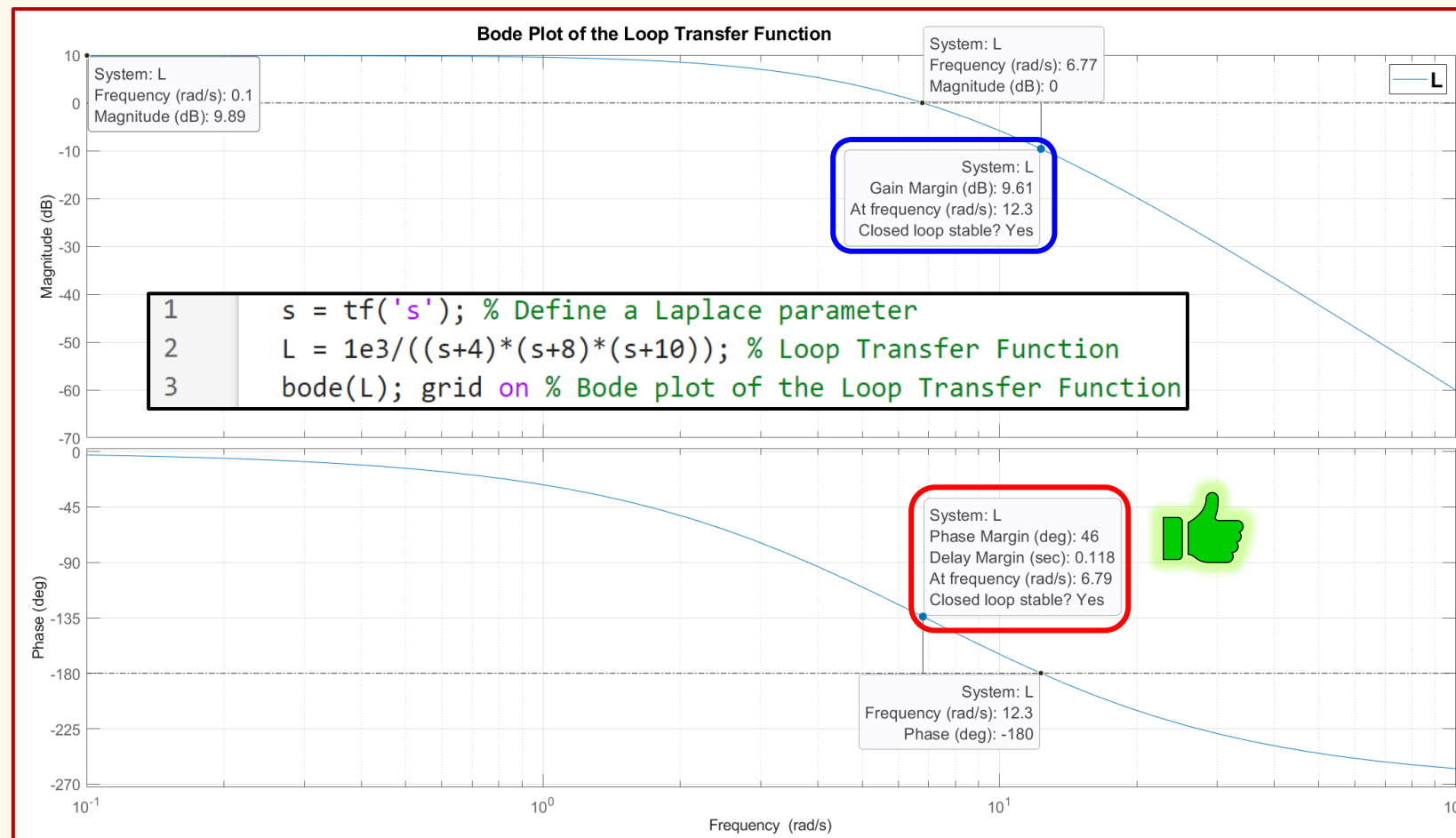


$$\omega_{pm} = 6.79 \text{ rad/s} \quad PM = 180 + \arg(L(j\omega_{pm})) = 46^\circ$$



$$\omega_{gm} = 12.33 \text{ rad/s} \quad GM = \frac{1}{|L(j\omega_{gm})|} = 3.024 \text{ (9.61 dB)}$$

2. Controller Circuits

❖ Type 2 Compensated Error Amplifier

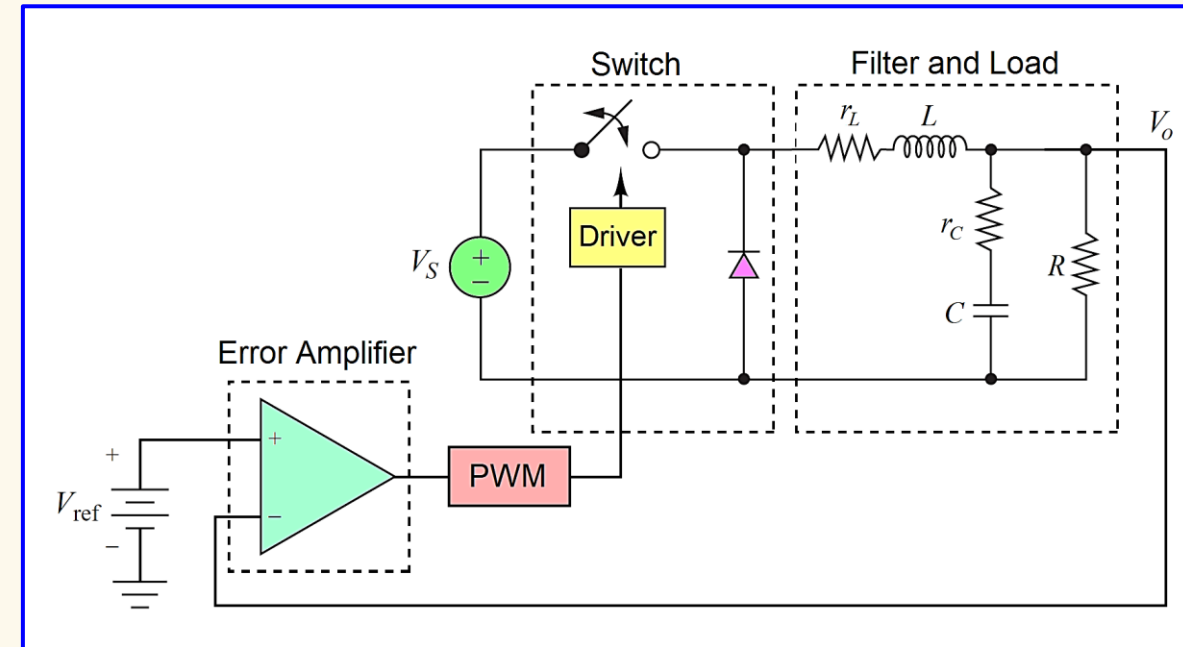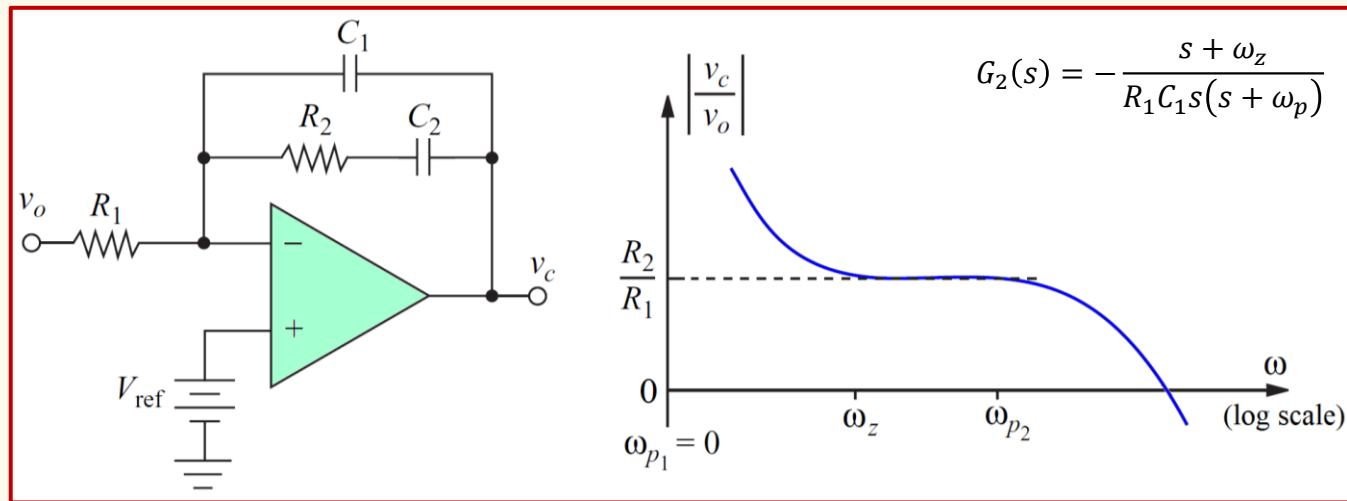


❖ Type 3 Compensated Error Amplifier

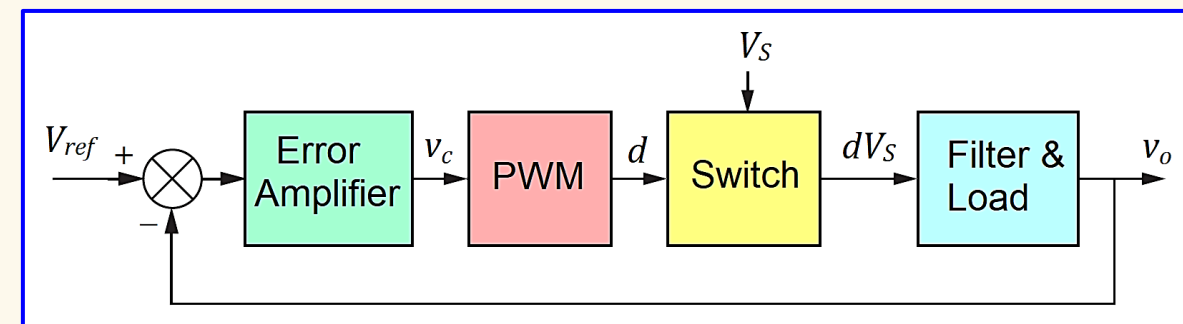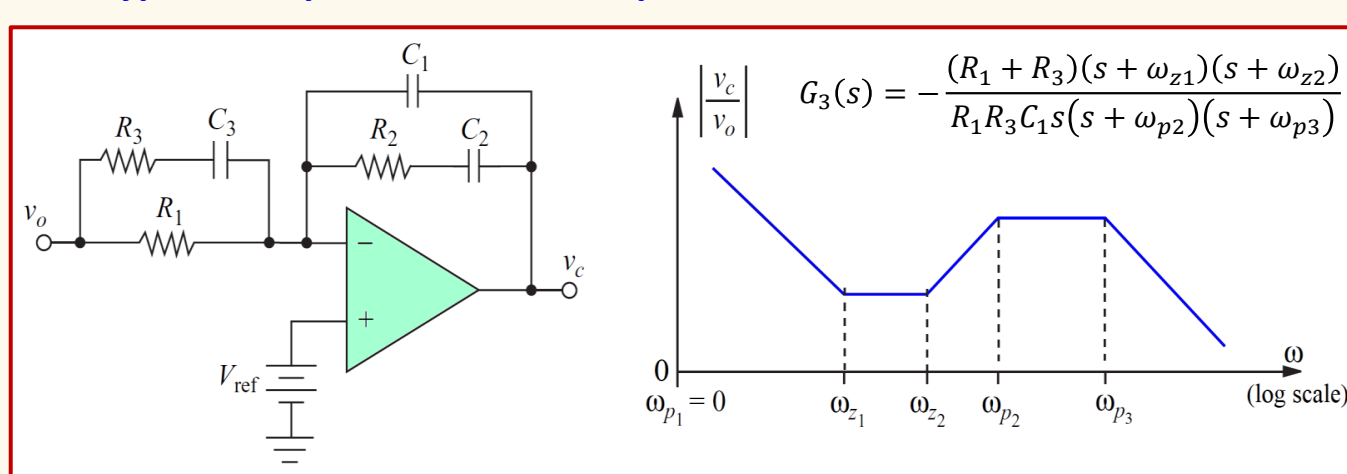

2. Controller Circuits

❖ Modulator:

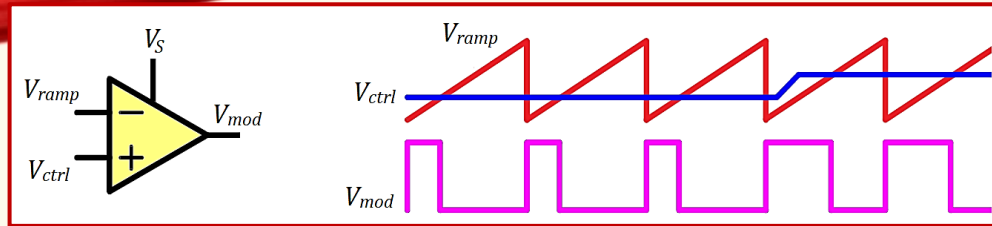

Modulator Average Output Voltage: $V_{mod} = \frac{1}{T} \int_0^T v_{mod}(t) dt = \frac{1}{T} \int_0^{t_{on}} V_S dt$

Modulator Transfer Function: $M(s) = \frac{\Delta V_{mod}}{\Delta V_{ctrl}}$

$$M(s) = \frac{dV_{mod}}{dV_{ctrl}} = \frac{d}{dV_{ctrl}} \left(V_S \frac{V_{ctrl}}{V_{ramp}} \right) \quad \boxed{M(s) = \frac{V_S}{V_{ramp}}}$$

❖ Filter & Load:



Filter & Load Transfer Function: $F(s) = \frac{V_o}{V_D} = \frac{1 + r_c C s}{1 + \frac{r_L}{R} + \left(\frac{L}{R} + (r_L + r_c) C + \frac{r_L r_c C}{R} \right) s + \left(1 + \frac{r_c}{R} \right) L C s^2}$

❖ Compensator:

Compensator Transfer Function: $G(s) = \frac{V_c}{V_o} = \frac{A_{OL}(s)}{1 + A_{OL}(s)\beta(s)} \approx \frac{A_{OL}(s)}{A_{OL}(s)\beta(s)} \approx \frac{1}{\beta(s)}$

Error Amplifier Open-Loop Transfer Function: $A_{OL}(s) = \frac{A_{DC}}{1 + \frac{s}{\omega_{pe}}} \quad A_{OL}(s)\beta(s) \gg 1$

Feedback Transfer Function: $\beta(s)$

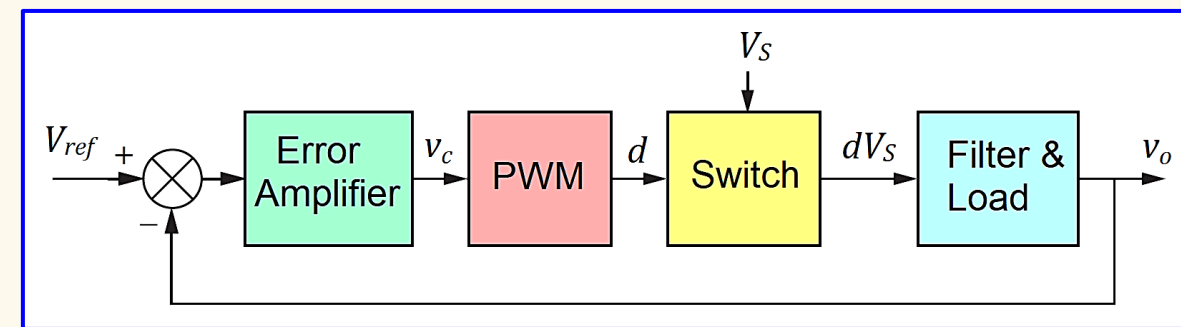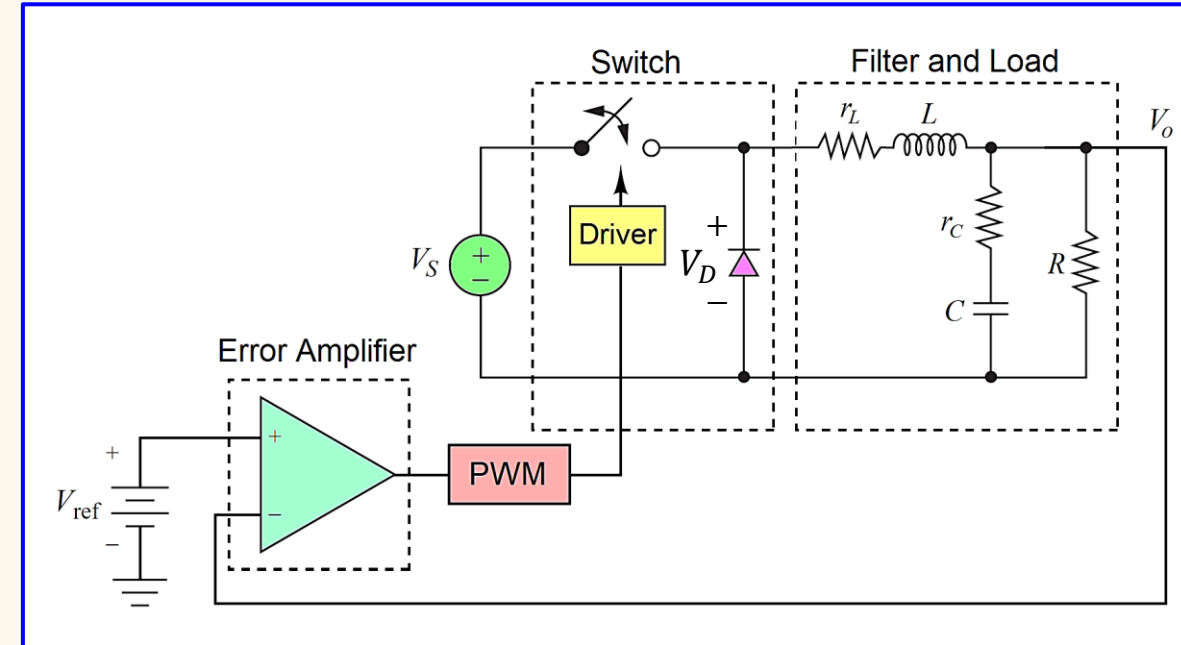

Calculations

- Given:**
- DC input voltage $V_S = 60 \text{ V}$
 - Average output voltage $V_o = 15 \text{ V}$
 - Average output current $I_o = 2 \text{ A}$
 - Maximum percentage peak-peak output ripple voltage $\Delta V_o/V_o = 0.01$ (1%)

Buck Converter Component Values & Selections:

$L = 300 \mu\text{H}$	$r_L = 25 \text{ m}\Omega$	$R = V_o/I_o = 7.5 \Omega$
$C = 20 \mu\text{F}$	$r_C = 400 \text{ m}\Omega$	$f_s = 100 \text{ kHz}$ (selected)

Solution: ☐ Calculations

Filter & Load Transfer Function:

$$F(s) = \frac{1 + r_C C s}{1 + \frac{r_L}{R} + \left(\frac{L}{R} + (r_L + r_C)C + \frac{r_L r_C C}{R}\right)s + \left(1 + \frac{r_C}{R}\right)LCs^2}$$

$$F(j\omega) = \frac{1 + j\omega r_C C}{1 + \frac{r_L}{R} - \left(1 + \frac{r_C}{R}\right)LC\omega^2 + j\omega \left(\frac{L}{R} + (r_L + r_C)C + \frac{r_L r_C C}{R}\right)}$$

Type 3 Compensated Error Amplifier Transfer Function:

$$G_3(s) = -\frac{R_1 + R_3}{R_1 R_3 C_1} \cdot \frac{\left(s + \frac{1}{(R_1 + R_3)C_3}\right)\left(s + \frac{1}{R_2 C_2}\right)}{s\left(s + \frac{1}{R_3 C_3}\right)\left(s + \frac{C_1 + C_2}{C_1 C_2 R_2}\right)}$$

Assuming:
 $R_1 \gg R_3$
 $C_2 \gg C_1$

$$G_3(s) \approx -\frac{1}{R_3 C_1} \cdot \frac{\left(s + \frac{1}{R_1 C_3}\right)\left(s + \frac{1}{R_2 C_2}\right)}{s\left(s + \frac{1}{R_3 C_3}\right)\left(s + \frac{1}{R_2 C_1}\right)}$$

Loop Transfer Function:



$$L(s) = M(s)F(s)G_3(s)$$

$$L(s) = \frac{V_S}{V_{ramp}} \cdot \frac{1 + r_C C s}{1 + \frac{r_L}{R} + \left(\frac{L}{R} + (r_L + r_C)C + \frac{r_L r_C C}{R}\right)s + \left(1 + \frac{r_C}{R}\right)LCs^2} \cdot -\frac{1}{R_3 C_1} \cdot \frac{\left(s + \frac{1}{R_1 C_3}\right)\left(s + \frac{1}{R_2 C_2}\right)}{s\left(s + \frac{1}{R_3 C_3}\right)\left(s + \frac{1}{R_2 C_1}\right)}$$

$$L(j\omega) = \frac{V_S}{V_{ramp}} \cdot \frac{1 + j\omega r_C C}{1 + \frac{r_L}{R} - \left(1 + \frac{r_C}{R}\right)LC\omega^2 + j\omega \left(\frac{L}{R} + (r_L + r_C)C + \frac{r_L r_C C}{R}\right)} \cdot -\frac{1}{R_3 C_1} \cdot \frac{\left(j\omega + \frac{1}{R_1 C_3}\right)\left(j\omega + \frac{1}{R_2 C_2}\right)}{j\omega \left(j\omega + \frac{1}{R_3 C_3}\right)\left(j\omega + \frac{1}{R_2 C_1}\right)}$$

Design Objective:

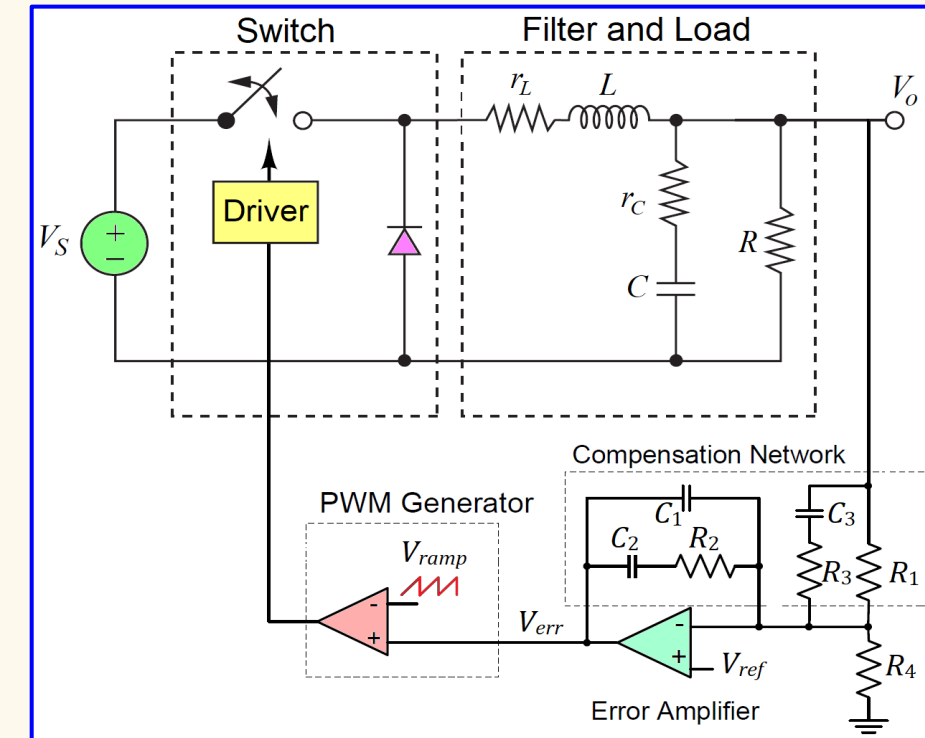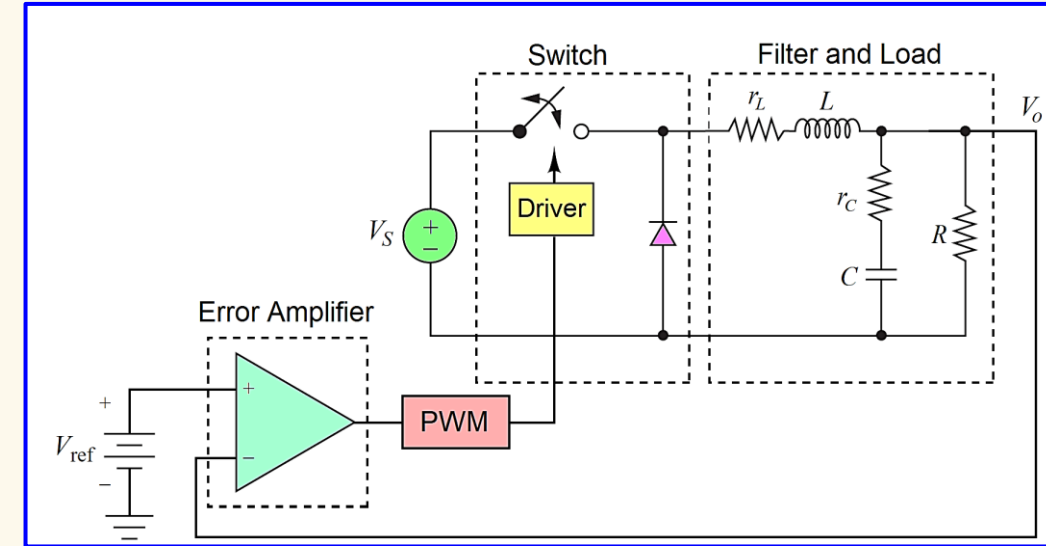- Type 3 Compensated Error Amplifier** for a **stable control system**.
- Design for a **crossover frequency** of **10 kHz** and a **phase margin** of **55°**



- Given:**
- DC input voltage $V_S = 60\text{ V}$
 - Average output voltage $V_o = 15\text{ V}$
 - Average output current $I_o = 2\text{ A}$
 - Maximum percentage peak-peak output ripple voltage $\Delta V_o/V_o = 0.01\text{ (1\%)}$

Buck Converter Component Values & Selections:

$L = 300\text{ }\mu\text{H}$	$r_L = 25\text{ m}\Omega$	$R = V_o/I_o = 7.5\text{ }\Omega$
$C = 20\text{ }\mu\text{F}$	$r_C = 400\text{ m}\Omega$	$f_s = 100\text{ kHz (selected)}$

Solution: ☐ Calculations

Loop Transfer Function:

$$L(j\omega) = \frac{V_S}{V_{ramp}} \cdot \frac{1 + j\omega r_C C}{1 + \frac{r_L}{R} - \left(1 + \frac{r_C}{R}\right) LC\omega^2 + j\omega \left(\frac{L}{R} + (r_L + r_C)C + \frac{r_L r_C C}{R}\right)} \cdot \frac{1}{R_3 C_1} \cdot \frac{\left(j\omega + \frac{1}{R_1 C_3}\right) \left(j\omega + \frac{1}{R_2 C_2}\right)}{j\omega \left(j\omega + \frac{1}{R_3 C_3}\right) \left(j\omega + \frac{1}{R_2 C_1}\right)}$$

Phase: $\arg(L(j\omega)) = \arg(M(j\omega)) + \arg(F(j\omega)) + \arg(G_3(j\omega))$

$$\begin{aligned} \arg(M(j\omega)) &= 0^\circ \\ \arg(F(j\omega)) &= \arctan(\omega r_C C) - \left[\arctan\left(\frac{\omega \left(\frac{L}{R} + (r_L + r_C)C + \frac{r_L r_C C}{R}\right)}{1 + \frac{r_L}{R} - \left(1 + \frac{r_C}{R}\right) LC\omega^2}\right) + 180^\circ \right] \\ \arg(F(j\omega_t)) &= \arctan(\omega_t r_C C) - \left[\arctan\left(\frac{\omega_t \left(\frac{L}{R} + (r_L + r_C)C + \frac{r_L r_C C}{R}\right)}{1 + \frac{r_L}{R} - \left(1 + \frac{r_C}{R}\right) LC\omega_t^2}\right) + 180^\circ \right] = -146^\circ \end{aligned}$$

Crossover Frequency
 $f_t = 10\text{ kHz}$

$$PM = 180^\circ + \arg(L(j\omega_t)) \Rightarrow \arg(L(j\omega_t)) = PM - 180^\circ = 55^\circ - 180^\circ = -125^\circ$$

$$\begin{aligned} -125^\circ &= 0^\circ - 146^\circ + \arg(G_3(j\omega)) \Rightarrow \arg(G_3(j\omega)) = 21^\circ & \phi_{comp} &= 21^\circ + 180^\circ = 201^\circ \\ & & \text{Thus, the compensator needs to provide } &201^\circ. \end{aligned}$$


Magnitude: $|L(j\omega)| = |M(j\omega)| \cdot |F(j\omega)| \cdot |G_3(j\omega)|$

The **loop gain** must be **unity** at the **crossover frequency**.

$$|F(j\omega)| = \frac{\sqrt{1 + (\omega r_C C)^2}}{\sqrt{\left(1 + \frac{r_L}{R} - \left(1 + \frac{r_C}{R}\right) LC\omega^2\right)^2 + \left(\omega \left(\frac{L}{R} + (r_L + r_C)C + \frac{r_L r_C C}{R}\right)\right)^2}} \quad |F(j\omega_t)| = 0.04636 \text{ (-26.68 dB)}$$

Design Objective:

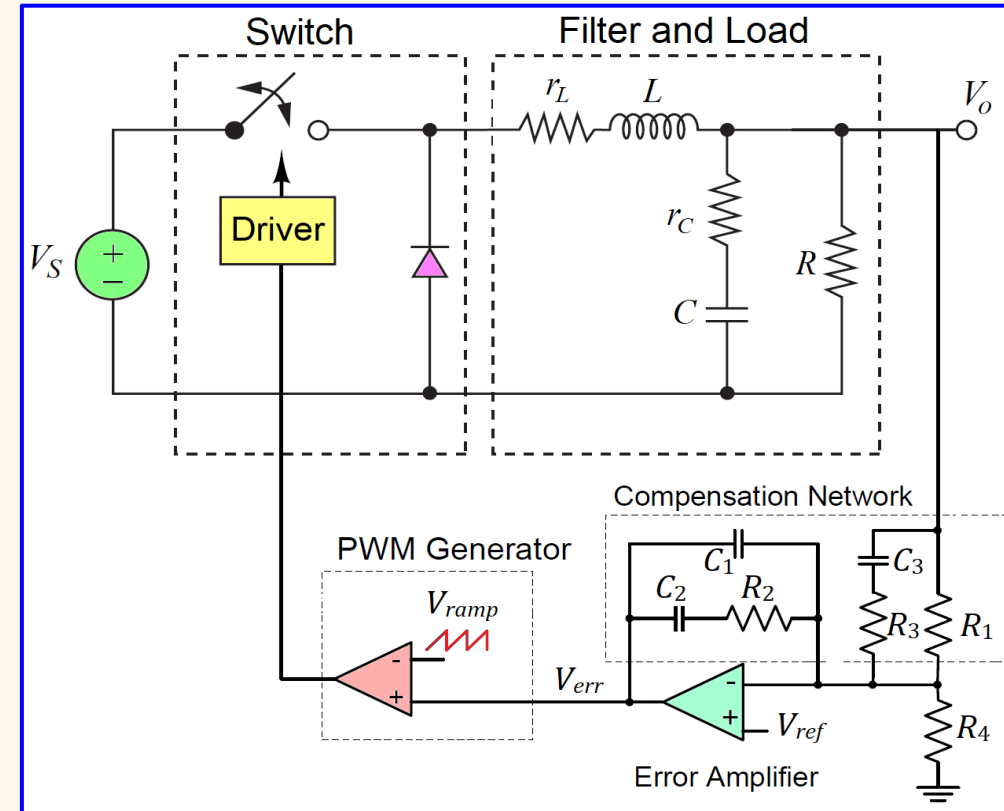- Type 3 Compensated Error Amplifier** for a **stable control system**.
- Design for a **crossover frequency** of **10 kHz** and a **phase margin** of **55°**



$$\text{Modulator gain: } M = \frac{V_S}{V_{ramp}} = 15 \text{ (23.52 dB) for LM5146}$$

At the **crossover frequency**, the compensator needs to provide a gain of

$$|G_3(j\omega_t)| = \frac{1}{|M(j\omega_t)| \cdot |F(j\omega_t)|} = \frac{1}{15 \cdot 0.04636} = 1.438 \text{ (3.155 dB)}$$

- Given:**
- DC input voltage $V_S = 60\text{ V}$
 - Average output voltage $V_o = 15\text{ V}$
 - Average output current $I_o = 2\text{ A}$
 - Maximum percentage peak-peak output ripple voltage $\Delta V_o/V_o = 0.01\text{ (1\%)}$

Buck Converter Component Values & Selections:

$L = 300\text{ }\mu\text{H}$ $r_L = 25\text{ m}\Omega$ $R = V_o/I_o = 7.5\text{ }\Omega$

$C = 20\text{ }\mu\text{F}$ $r_C = 400\text{ m}\Omega$ $f_s = 100\text{ kHz (selected)}$

Solution: ☐ Calculations *Compensator Values – K Factor Method*

- Step 1: Calculate the K Factor**

$$K = \tan^2\left(\frac{\phi_{comp} + 90^\circ}{4}\right) = \tan^2\left(\frac{201^\circ + 90^\circ}{4}\right) = 10.4$$

- Step 2: Calculate Resistor R_2** Let $R_1 = 200\text{ k}\Omega$

$$R_2 = \frac{|G_3(j\omega_t)| \cdot R_1}{\sqrt{K}} = \frac{1.438 \cdot 2 \cdot 10^5}{\sqrt{10.4}} = 89.18\text{ k}\Omega$$

- Step 3: Calculate Capacitor C_1**

$$C_1 = \frac{1}{\omega_t R_2 \sqrt{K}} = \frac{1}{2\pi \cdot 10^4 \cdot 89.18 \cdot 10^3 \cdot \sqrt{10.4}} = 55.34\text{ pF}$$

- Step 4: Calculate Capacitor C_2**

$$C_2 = \frac{\sqrt{K}}{\omega_t R_2} = \frac{\sqrt{10.4}}{2\pi \cdot 10^4 \cdot 89.18 \cdot 10^3} = 575.5\text{ pF}$$

- Step 5: Calculate Capacitor C_3**

$$C_3 = \frac{\sqrt{K}}{\omega_t R_1} = \frac{\sqrt{10.4}}{2\pi \cdot 10^4 \cdot 2 \cdot 10^5} = 256.6\text{ pF}$$

Design Objective:

- Type 3 Compensated Error Amplifier** for a stable control system.
- Design for a **crossover frequency** of **10 kHz** and a **phase margin** of **55°**

$$V_{ref} = 0.8\text{ V}$$

$$\phi_{comp} = 201^\circ$$

$$|G_3(j\omega_t)| = 1.438$$

$$G_3(j\omega) = -\frac{1}{R_3 C_1} \cdot \frac{(j\omega + \omega_z)^2}{j\omega(j\omega + \omega_p)^2}$$

- Step 6: Calculate Resistor R_3**

$$R_3 = \frac{1}{\omega_t C_3 \sqrt{K}} = \frac{1}{2\pi \cdot 10^4 \cdot 256.6 \cdot 10^{-12} \cdot \sqrt{10.4}}$$

$$R_3 = 19.23\text{ k}\Omega$$

- Step 7: Calculate Resistor R_4**

$$\frac{V_{ref}}{V_o} = \frac{R_4}{R_1 + R_4}$$



$$V_{ref}(R_1 + R_4) = V_o R_4$$

$$V_{ref} R_1 = (V_o - V_{ref}) R_4$$

$$R_4 = \frac{V_{ref}}{V_o - V_{ref}} R_1$$


$$R_4 = \frac{0.8}{15 - 0.8} \cdot 2 \cdot 10^5$$

$$R_4 = 11.27\text{ k}\Omega$$

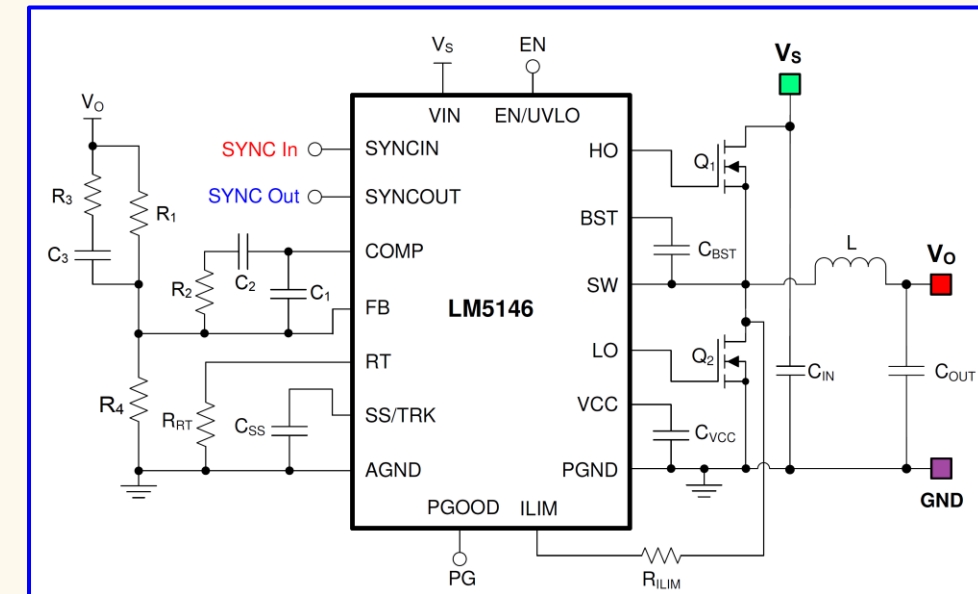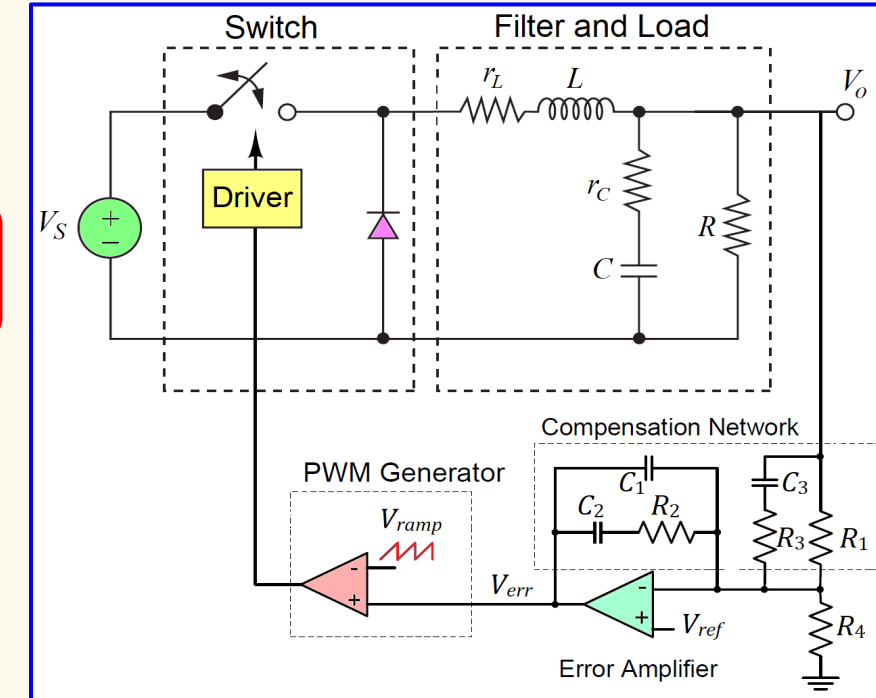

Simulations

MATLAB/Simulink

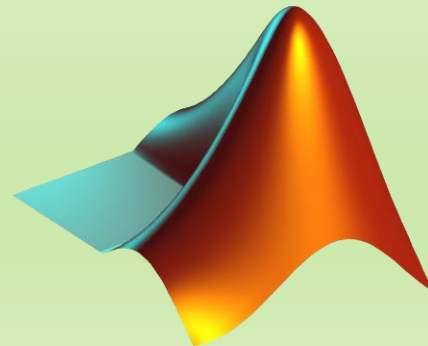

- Given:**
- DC input voltage $V_S = 60\text{ V}$
 - Average output voltage $V_o = 15\text{ V}$
 - Average output current $I_o = 2\text{ A}$
 - Maximum percentage peak-peak output ripple voltage $\Delta V_o/V_o = 0.01\text{ (1\%)}$

Buck Converter Component Values & Selections:

$L = 300\text{ }\mu\text{H}$
 $r_L = 25\text{ m}\Omega$
 $R = V_o/I_o = 7.5\text{ }\Omega$

$C = 20\text{ }\mu\text{F}$
 $r_C = 400\text{ m}\Omega$
 $f_s = 100\text{ kHz (selected)}$

Solution: ☐ Simulations – MATLAB Script

```


1  s = tf('s'); % Define a Laplace parameter
2
3  %**SPECIFICATIONS**
4  Vs = 60; Vo = 15; % Input and output DC voltage values
5
6  %**SELECTIONS**
7  f_s = 1e5; % Switching frequency
8
9  %**BUCK CONTROLLER IC: LM5146**
10 Vref = 0.8; % Reference voltage from Buck Controller LM5146
11 Vramp = Vs/15; %Ramp voltage amplitude from Buck Controller LM5146
12 A_DC = 50119; % Error amplifier open-loop DC gain
13 GBW = 6.5e6; % Error amplifier gain bandwidth product
14 f_pe = GBW/A_DC; % Error amplifier open-loop pole: f_pe = 129.7 Hz.
15
16 %**COMPONENTS**
17 R = 7.5; L = 300e-6; C = 20e-6; % Buck converter output filter values
18 r_C = 400e-3; % ESR of the capacitor C
19 r_L = 25e-3; % ESR of the inductor L
20
21 %**TRANSFER FUNCTIONS**
22 M = Vs/Vramp; % PWM modulator transfer function
23 F = (1+r_C*C*s)/(1+r_L/R + (L/R+(r_C+r_L)*C+r_C*r_L*C/R)*s + (1+r_C/R)*L*C*s^2); % Filter and Load
24
25 %**FREQUENCIES and PARAMETERS**
26 f_t = 0.1*f_s; % Crossover frequency (selected value one decade below f_s)
27 phase_comp = 201*pi/180; % Required compensator phase.
28 K_comp = 1/(M*0.04636); % Required compensator gain at the crossover frequency.
29 K = (tan(0.25*(phase_comp + pi/2)))^2; % K factor value.
30
31 %**CONTROLLER COMPONENT VALUES**
32 R1 = 2e5; % Upper resistor for reference voltage divider (selected).
33 R2 = K_comp*R1/sqrt(K);
34 C1 = 1/(2*pi*f_t*R2*sqrt(K));
35 C2 = sqrt(K)/(2*pi*f_t*R2);
36 C3 = sqrt(K)/(2*pi*f_t*R1);
37 R3 = 1/(2*pi*f_t*C3*sqrt(K));
38 R4 = Vref*R1/(Vo-Vref); % Lower resistor for reference voltage divider.
39
40 %**COMPENSATOR TRANSFER FUNCTION**
41 G_OL = -A_DC/(1+s/(2*pi*f_pe)); % Error amplifier transfer function
42 beta = (R1*R3*C1*s*(s+(C1+C2)/(C1*C2*R2))*(s+1/(R3*C3)))/((R1+R3)*(s+1/(R2*C2))*(s+1/((R1+R3)*C3)));
43 G_comp = G_OL/(1+G_OL*beta); % Compensator transfer function
44 G_loop = M*F*G_comp;
  
```

- Design Objective:**
- Type 3 Compensated Error Amplifier for a stable control system.
 - Design for a **crossover frequency** of **10 kHz** and a **phase margin** of **55°**

$V_{ref} = 0.8\text{ V}$
 $\phi_{comp} = 201^\circ$
 $|G_3(j\omega_t)| = 1.438$

$R_1 = 200\text{ k}\Omega$
 $R_2 = 89.18\text{ k}\Omega$
 $R_3 = 19.23\text{ k}\Omega$
 $R_4 = 11.27\text{ k}\Omega$

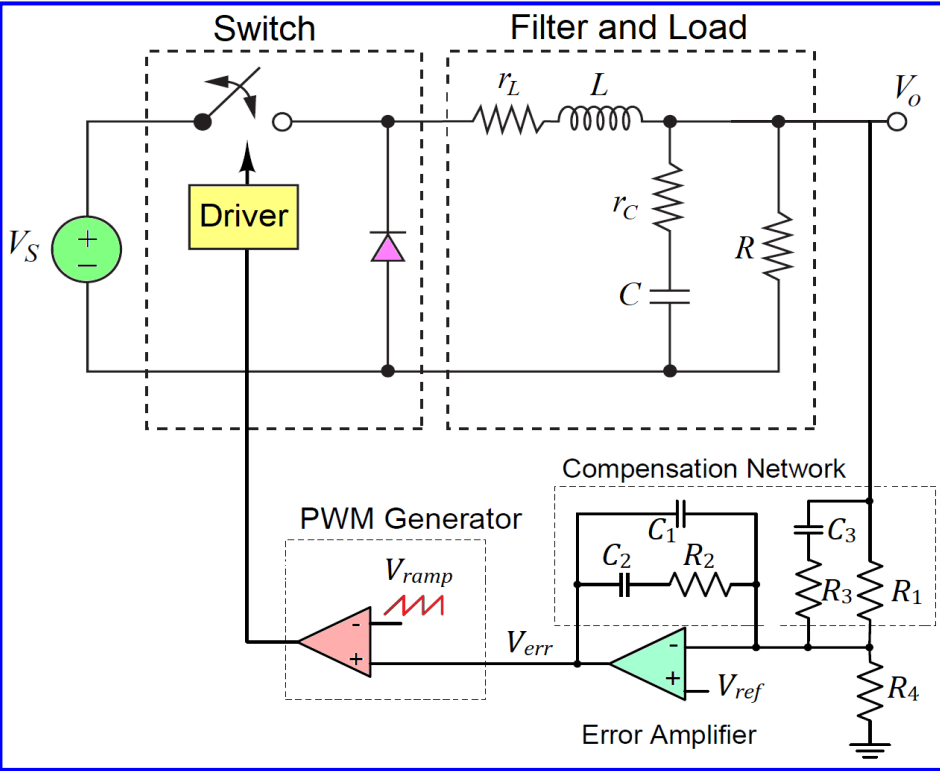$C_1 = 55.34\text{ pF}$
 $C_2 = 575.5\text{ pF}$
 $C_3 = 256.6\text{ pF}$



PARAMETER		TEST CONDITIONS	MIN	TYP	MAX	UNIT
PWM CONTROL						
DC _{100kHz}	Maximum duty cycle	F _{SW} = 100 kHz, 6 V ≤ V _{VIN} ≤ 60 V	98	99		%
DC _{400kHz}		F _{SW} = 400 kHz, 6 V ≤ V _{VIN} ≤ 60 V	90	94		%
V _{RAMP(min)}	RAMP valley voltage (COMP at 0% duty cycle)			300		mV
K _{FF}	PWM feedforward gain (V _{IN} / V _{RAMP})	6 V ≤ V _{VIN} ≤ 100 V		15		V/V
ERROR AMPLIFIER						
V _{REF}	FB reference Voltage	FB connected to COMP	792	800	808	mV
AVOL	DC gain			94		dB
GBW	Unity gain bandwidth			6.5		MHz

- Given:**
- DC input voltage $V_S = 60\text{ V}$
 - Average output voltage $V_o = 15\text{ V}$
 - Average output current $I_o = 2\text{ A}$
 - Maximum percentage peak-peak output ripple voltage $\Delta V_o/V_o = 0.01\text{ (1\%)}$

Buck Converter Component Values & Selections:

$L = 300\text{ }\mu\text{H}$ $r_L = 25\text{ m}\Omega$ $R = V_o/I_o = 7.5\text{ }\Omega$
 $C = 20\text{ }\mu\text{F}$ $r_C = 400\text{ m}\Omega$ $f_s = 100\text{ kHz (selected)}$

Solution: ☐ Simulations – Loop Transfer Functions



Design Objective:

- Type 3 Compensated Error Amplifier** for a **stable control system**.
- Design for a **crossover frequency** of **10 kHz** and a **phase margin** of **55°**

$$V_{ref} = 0.8\text{ V}$$

$$\phi_{comp} = 201^\circ$$

$$|G_3(j\omega_t)| = 1.438$$

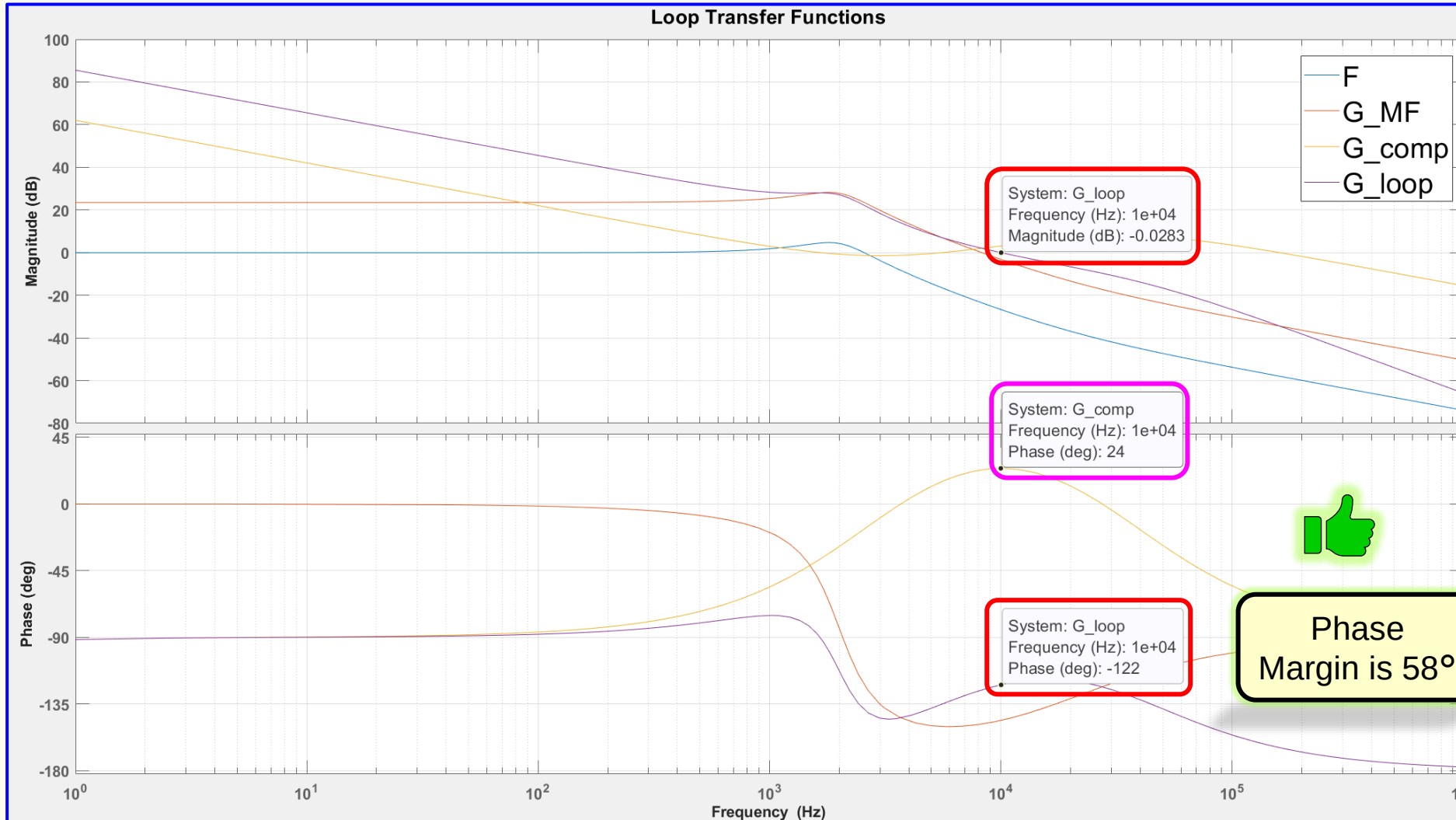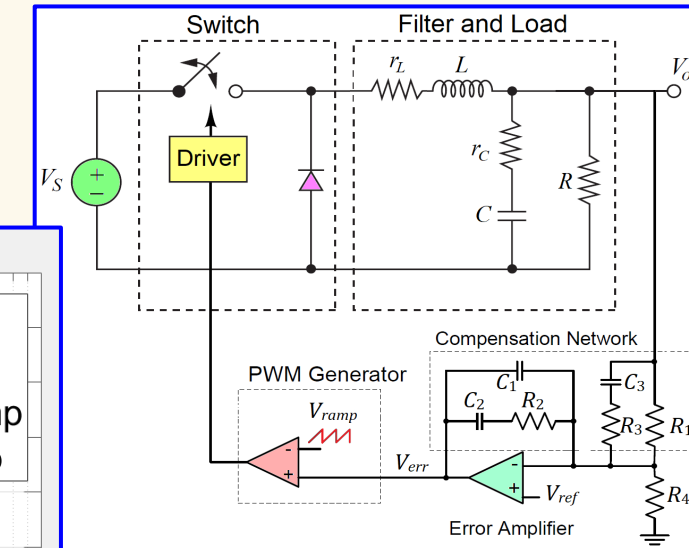

$$\begin{aligned}
 R_1 &= 200\text{ k}\Omega \\
 R_2 &= 89.18\text{ k}\Omega \\
 R_3 &= 19.23\text{ k}\Omega \\
 R_4 &= 11.27\text{ k}\Omega
 \end{aligned}$$

$$\begin{aligned}
 C_1 &= 55.34\text{ pF} \\
 C_2 &= 575.5\text{ pF} \\
 C_3 &= 256.6\text{ pF}
 \end{aligned}$$

Simulations

TINA-TI SPICE




- Given:**
- DC input voltage $V_S = 60\text{ V}$
 - Average output voltage $V_o = 15\text{ V}$
 - Average output current $I_o = 2\text{ A}$
 - Maximum percentage peak-peak output ripple voltage $\Delta V_o/V_o = 0.01\text{ (1\%)}$

Buck Converter Component Values & Selections:


$L = 300\text{ }\mu\text{H}$ $r_L = 25\text{ m}\Omega$ $R = V_o/I_o = 7.5\text{ }\Omega$
 $C = 20\text{ }\mu\text{F}$ $r_C = 400\text{ m}\Omega$ $f_s = 100\text{ kHz (selected)}$

Solution: Simulations – Circuit

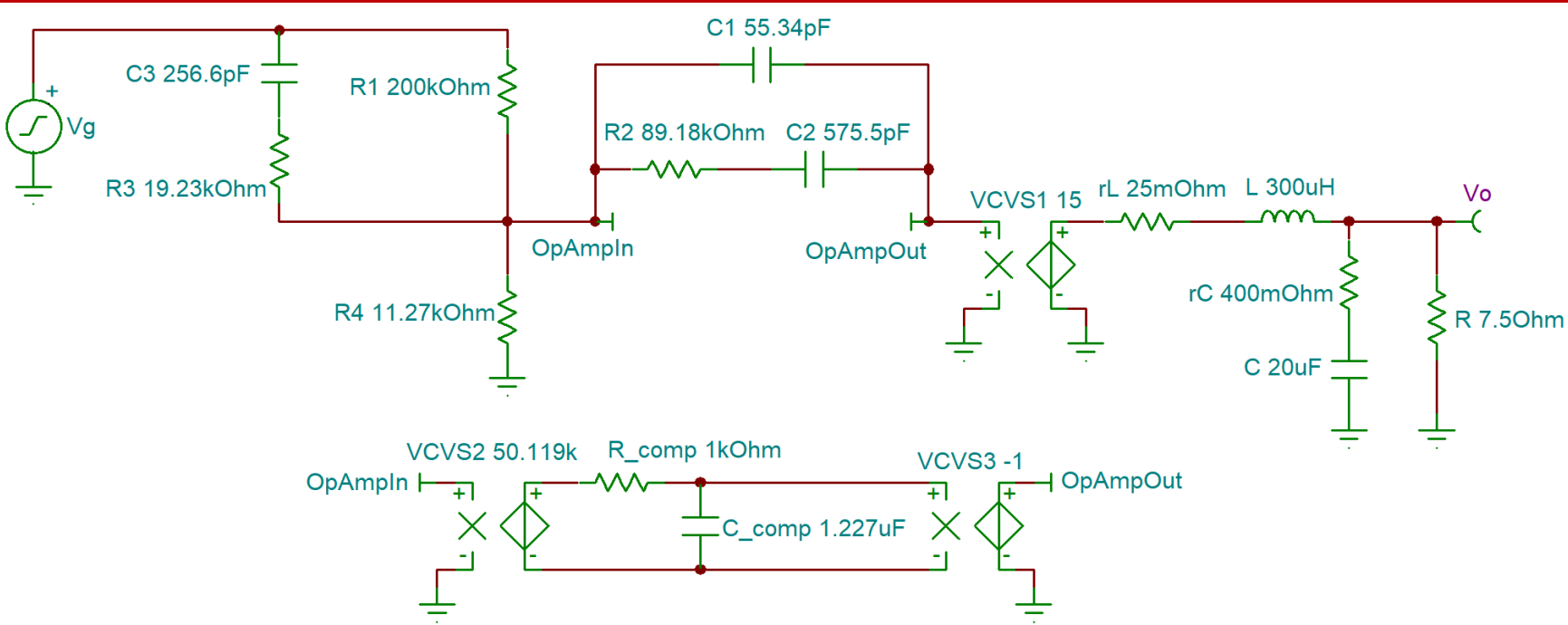

- Design Objective:**
- Type 3 Compensated Error Amplifier** for a **stable control system**.
 - Design for a **crossover frequency** of **10 kHz** and a **phase margin** of **55°**

$V_{ref} = 0.8\text{ V}$
 $\phi_{comp} = 201^\circ$
 $|G_3(j\omega_t)| = 1.438$

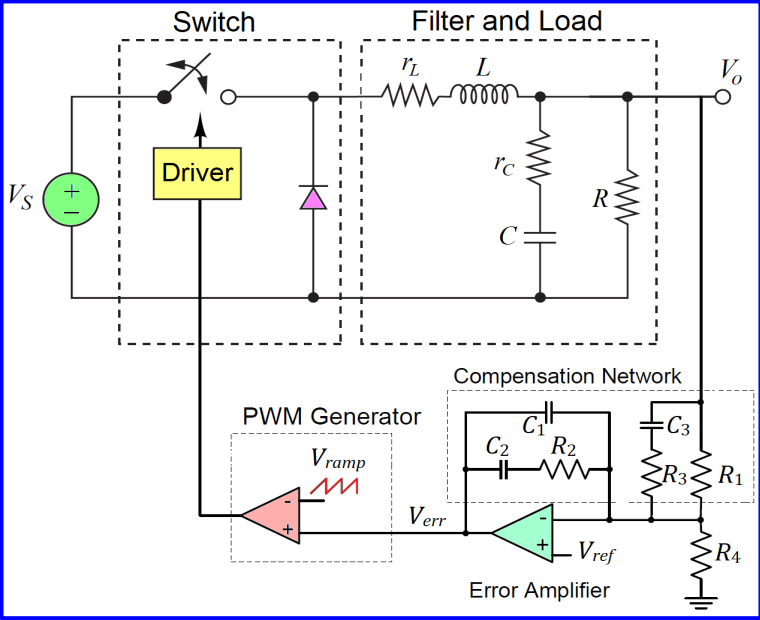

$R_1 = 200\text{ k}\Omega$
 $R_2 = 89.18\text{ k}\Omega$
 $R_3 = 19.23\text{ k}\Omega$
 $R_4 = 11.27\text{ k}\Omega$

$C_1 = 55.34\text{ pF}$
 $C_2 = 575.5\text{ pF}$
 $C_3 = 256.6\text{ pF}$

PARAMETER		TEST CONDITIONS	MIN	TYP	MAX	UNIT
PWM CONTROL						
DC _{100kHz}	Maximum duty cycle	$F_{SW} = 100\text{ kHz}, 6\text{ V} \leq V_{VIN} \leq 60\text{ V}$	98	99		%
DC _{400kHz}		$F_{SW} = 400\text{ kHz}, 6\text{ V} \leq V_{VIN} \leq 60\text{ V}$	90	94		%
$V_{RAMP(min)}$	RAMP valley voltage (COMP at 0% duty cycle)			300		mV
k_{FF}	PWM feedforward gain (V_{IN} / V_{RAMP})	$6\text{ V} \leq V_{VIN} \leq 100\text{ V}$		15		V/V
ERROR AMPLIFIER						
V_{REF}	FB reference Voltage	FB connected to COMP	792	800	808	mV
AVOL	DC gain			94		dB
GBW	Unity gain bandwidth			6.5		MHz

- Given:**
- DC input voltage $V_S = 60\text{ V}$
 - Average output voltage $V_o = 15\text{ V}$
 - Average output current $I_o = 2\text{ A}$
 - Maximum percentage peak-peak output ripple voltage $\Delta V_o/V_o = 0.01\text{ (1\%)}$

Buck Converter Component Values & Selections:

$L = 300\text{ }\mu\text{H}$ $r_L = 25\text{ m}\Omega$ $R = V_o/I_o = 7.5\text{ }\Omega$
 $C = 20\text{ }\mu\text{F}$ $r_C = 400\text{ m}\Omega$ $f_s = 100\text{ kHz (selected)}$

Solution: ☐ Simulations – Loop Transfer Functions



Design Objective:

- Type 3 Compensated Error Amplifier** for a **stable control system**.
- Design for a **crossover frequency** of **10 kHz** and a **phase margin** of **55°**

$$V_{ref} = 0.8\text{ V}$$

$$\phi_{comp} = 201^\circ$$

$$|G_3(j\omega_t)| = 1.438$$

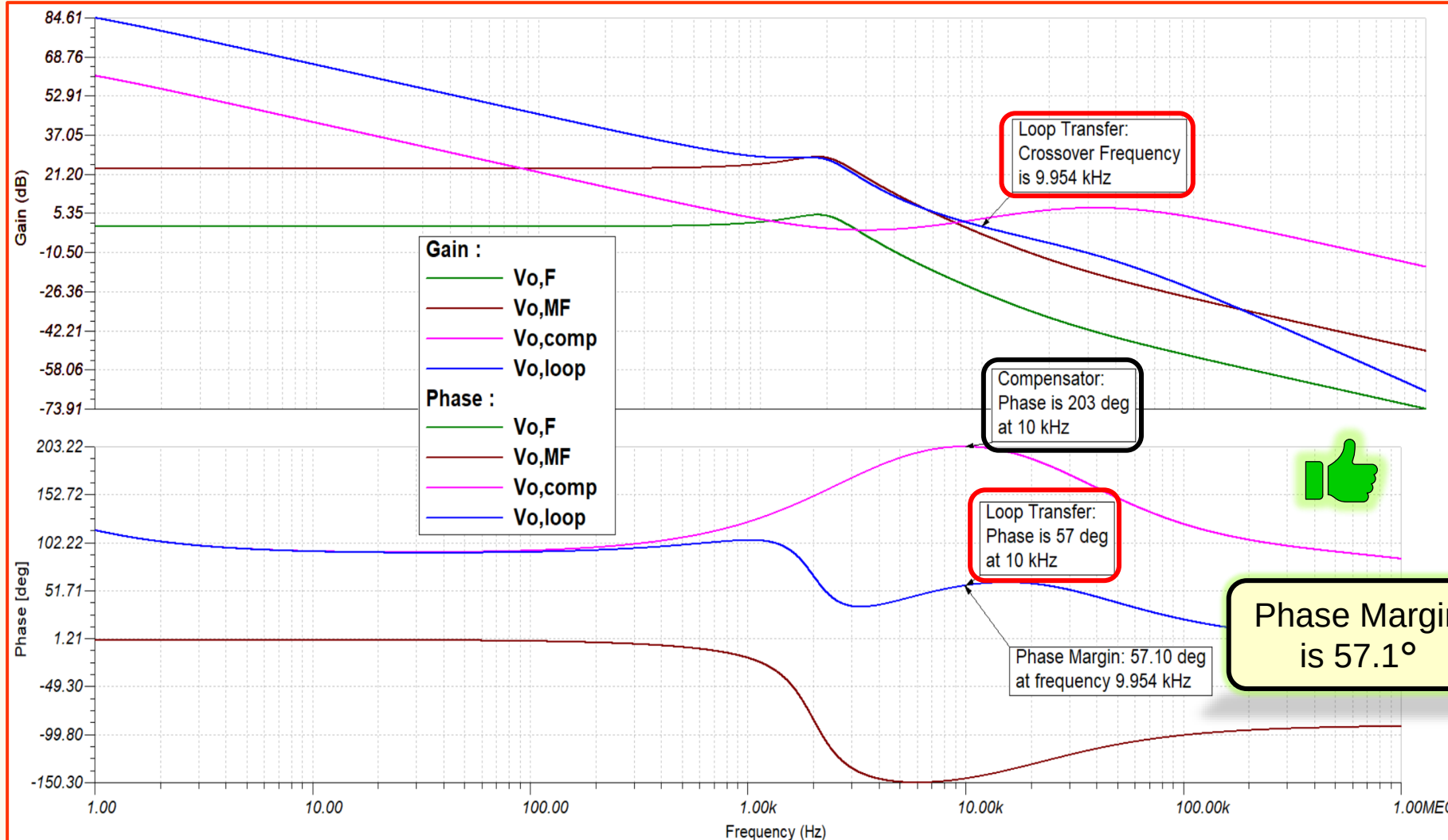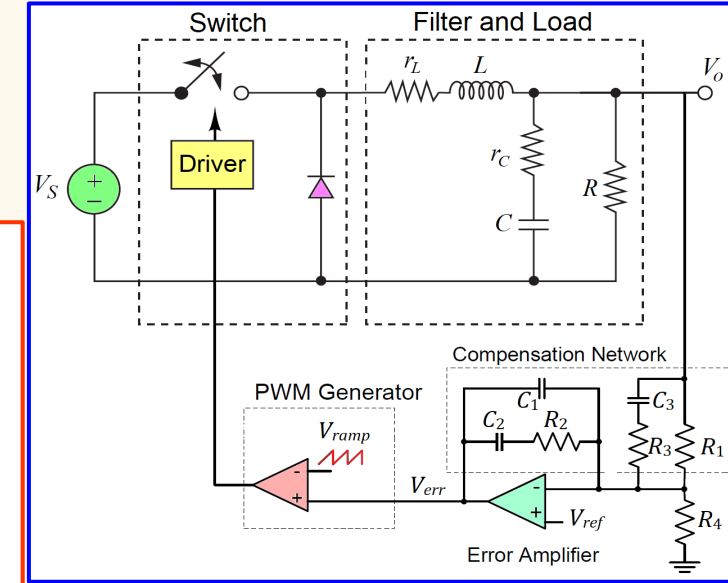

$$\begin{aligned}
 R_1 &= 200\text{ k}\Omega \\
 R_2 &= 89.18\text{ k}\Omega \\
 R_3 &= 19.23\text{ k}\Omega \\
 R_4 &= 11.27\text{ k}\Omega
 \end{aligned}$$

$$\begin{aligned}
 C_1 &= 55.34\text{ pF} \\
 C_2 &= 575.5\text{ pF} \\
 C_3 &= 256.6\text{ pF}
 \end{aligned}$$